

---

## One-button controller issues step, run, and halt commands

by Robert Dougherty  
*Dunedin, Fla.*

---

The logic signals to step, run, and halt a computer or other appropriate digital device or system may be generated by this circuit, which is operated by just a single push button. The only active devices used are a dual one-shot and a dual flip-flop.

The step command is generated each time the push

button is depressed momentarily. The run command occurs if the button is held down for a time exceeding about 180 milliseconds. This time represents an excellent compromise between circuit speed and accuracy. A much shorter duration means the circuit may fail to differentiate between the step and run commands and may generate the run command when the step command is desired, or vice versa. Also, repeatedly pressing the button rapidly to initiate step functions will generate the run command if the duration is set for much more than 180 ms. Finally, the computer will be halted if the push button is depressed momentarily when the circuit is in the run mode.

As shown in the figure,  $A_1$  acts as an effective switch debouncer for the push button. For a step command,


poking the button quickly will cause the Q output of A<sub>1</sub> to go high and fire A<sub>2</sub>, the run-and-stop one-shot. A<sub>1</sub> is also fed to A<sub>3</sub>, the D input of the run-and-idle latch. At the same time, the  $\bar{Q}$  output of A<sub>1</sub>, which moves low, will fire the step one-shot A<sub>4</sub>, yielding the step function.

The sequence of events just discussed also describes the initial portion of the run command, whereby the step pulse is used to manually advance the computer's program counter by one. The run pulse then commands the computer to rapidly execute succeeding steps automatically. The  $\bar{Q}$  output of A<sub>2</sub> moves high 180 ms after the push button is depressed. The positive-going, or trailing, edge of this pulse then clocks the state of the push button (as detected by A<sub>1</sub>) into A<sub>3</sub>.

If the button has been released before time-out, a zero appears at the Q output of A<sub>3</sub>. But if the button is activated, A<sub>3</sub> moves high and the run command is executed by the computer.

A press of the button will cause the circuit to halt the machine if it is in the run mode, by clocking in a logic 0 to the run-and-idle latch. Note that the step pulse generated at the start of the halt sequence, as shown in the timing diagram, is of no consequence, since when the step is received, the machine is already in the run mode and will override that command. □

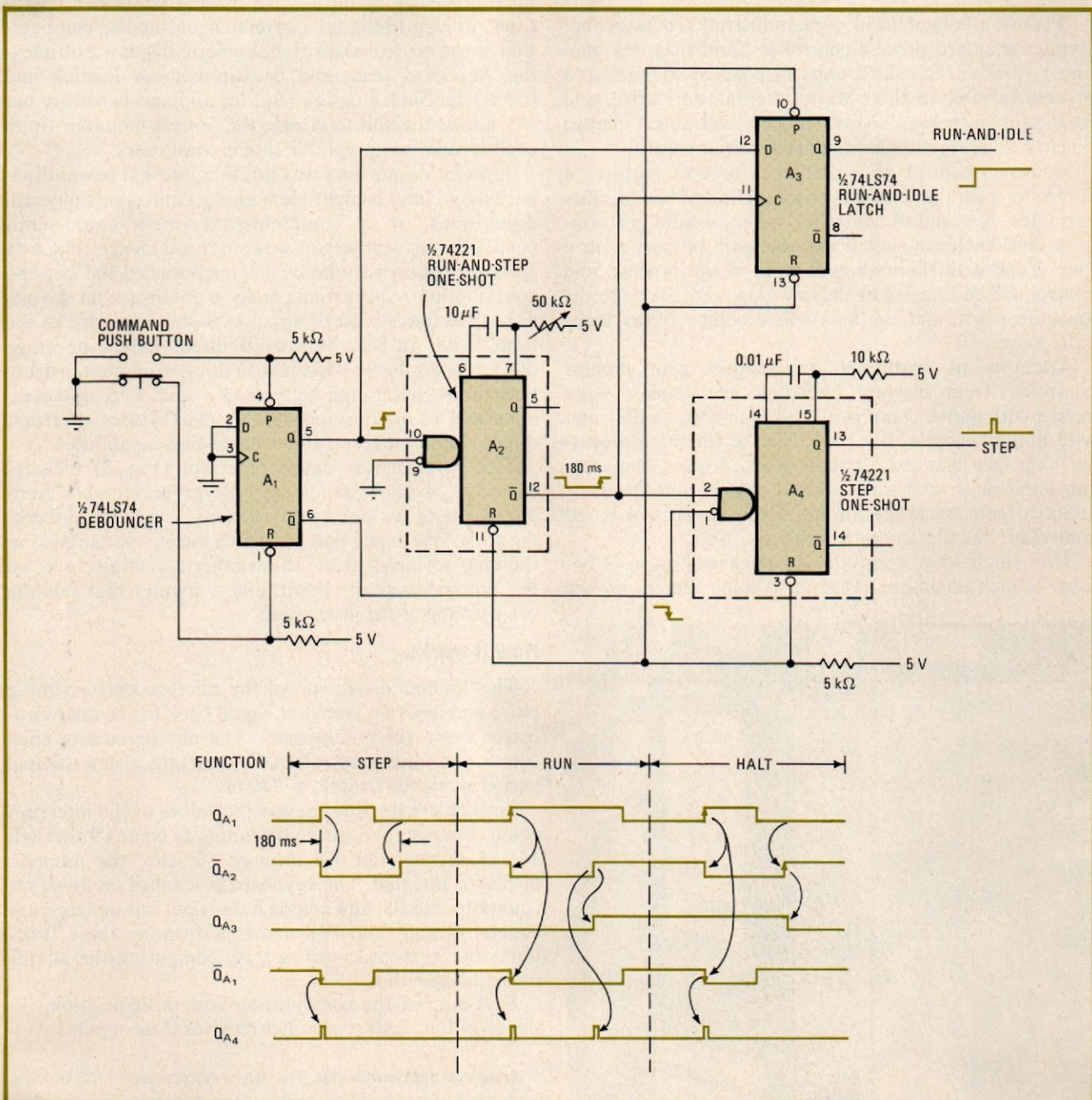Designer's casebook is a regular feature in *Electronics*. We invite readers to submit original and unpublished circuit ideas and solutions to design problems. Explain briefly but thoroughly the circuit's operating principle and purpose. We'll pay \$50 for each item published.



**Touch control.** One push button and two ICs single-step a computer's program counter or control run and halt operations. Button-depression time and present mode of controller determine the command generated. Timing diagram details circuit operation.