


A few added components make a self-contained controller for 100A load

Steve Hageman, AnalogHome.com, Windsor, CA

 The late Jim Williams' last project was a 100A active load (**Reference 1**). That design needed a separate signal generator and other components. This Design Idea makes the load self-contained. It adds potentiometers to control the stepped load levels, a chopper oscillator to switch between the set load levels, and a dual-readout DPM (digital-panel meter) to allow for direct voltage and current readout. In tribute to Williams, it uses three Linear Technology chips.

The heart of the load controller is two potentiometers, Set A and Set B (**Figure 1**). These devices allow you

to set A and B load levels anywhere in the 0 to 100A-load-range capability of Williams' design. For instance, assume that Set A is at $-0.5V$ and Set B is at $-0.75V$. Switching the load between these two levels changes it from 50 to 75A. Timer chip IC_1 controls the stepping rate and duty cycle between the Set A and the Set B levels. This timer IC allows you to control frequency over a decade range. It also allows you to set the duty cycle between 0 and 100%.

The full 0 to 100% duty-cycle control comes in handy when you set up the load. At 100% duty cycle, the voltage between the potentiometers does

not switch, and the Set A control is active alone. This situation allows you to adjust Set A and watch the actual dc level on the dual-readout panel meter. Likewise, setting the duty-cycle control to 0% switches to the Set B potentiometer and allows you to adjust its static or dc level.

**THE FULL 0 TO 100%
DUTY-CYCLE CONTROL
COMES IN
HANDY WHEN YOU
SET UP THE LOAD.**

Setting any duty cycle other than 0 or 100% causes the Set A and Set B levels to alternate. You control the chopping frequency by adjusting the fre-

