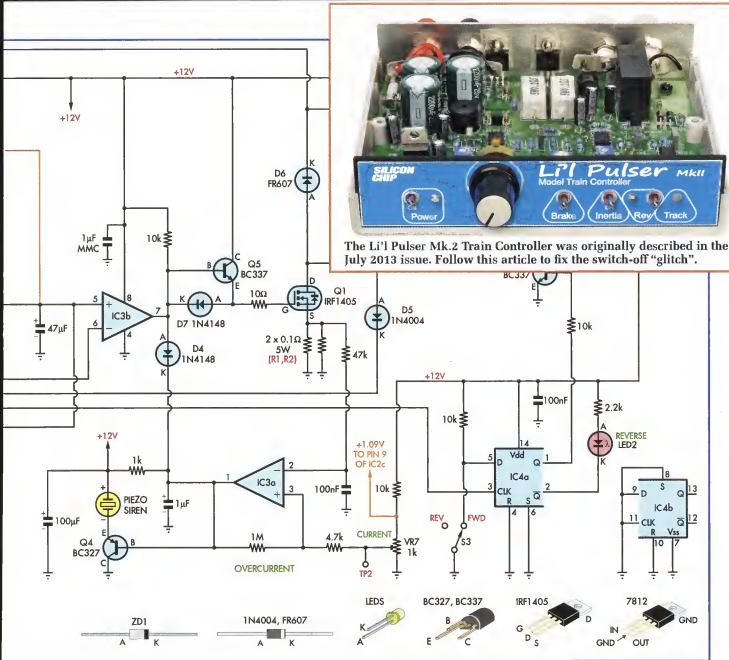




Li'l Pulser Mk2: fixing the switch-off lurch

siliconchip.com.au



The Li'l Pulser Mk.2 Train Controller was originally described in the July 2013 issue. Follow this article to fix the switch-off "glitch".

IF YOU'VE BUILT the Li'l Pulser Mk.2, then you'll want to fix the switch-off flaw. The magnitude of the effect varies, depending on how the unit is switched off (via its front panel controls or the mains power supply), what type of supply is being used, the types of locos involved and so on. It can range from a minor issue to one serious enough to cause derailment.

While this can be solved by taking the locos off the track or disconnecting the controller from the track before switching it off, that's inconvenient. So we set about figuring out why this was happening and how to fix it.

The cause

Take a look now at the circuit of

Fig.1. This shows the relevant sections of the original circuit published in the July 2013 issue but with a number of changes shown in orange.

Ignore the changes for the moment while we discuss the problem and how it occurs. Comparator IC3b generates the PWM waveform to drive Mosfet Q1, which switches the supply voltage to the tracks, controlling how much power the locos receive. This works by comparing a 160Hz triangle waveform to a control voltage, with the control voltage indicating the desired loco speed; the higher the control voltage, the higher the output PWM duty cycle and thus the higher the motor speed.

The control voltage is low-pass filtered by an RC network, to prevent it

from changing too rapidly and also to simulate train inertia. The amount of filtering applied depends on whether or not the inertia switch is on and the position of inertia control pot VR4 but regardless, there is always some filtering of this signal.

When the unit is switched off and its power supply capacitors discharge, the power supply to the op amp generating the triangle signal collapses and so the triangle signal's voltage drops rapidly. But this filtering of the control signal causes the control voltage to drop much more slowly. In other words, the 47µF capacitor at pin 5 of comparator IC3b remains charged for some time after power is removed.

This means that at switch-off, the

Extra Parts For PCB Modifications

- 1 8.2V zener diode (ZD2)
- 1 10nF MKT capacitor
- 1 470kΩ 0.25W resistor
- 1 220kΩ 0.25W resistor
- 1 100Ω 0.25W resistor
- 1 short length light duty hook-up wire

Parts List Changes For Revised PCB

Additional parts

- 1 BC337 NPN transistor (Q6)
- 1 8.2V zener diode (ZD2)
- 1 10nF MKT capacitor
- 1 220kΩ 0.25W resistor
- 1 100kΩ 0.25W resistor
- 1 100Ω 0.25W resistor

Deleted part

- 1 10μF electrolytic capacitor

drops somewhat if the supply is on the low side.

Now since the 10nF capacitor only provides a very short delay (with a time constant of 10ms) and with a threshold of about 11V, once the unit is switched off, the 12V supply doesn't have to drop by much before it enters the reset state which forces Q1 to stay off while the supply voltage decays to zero.

Making the changes

We made these changes to our prototype and it no longer causes any noticeable motor pulse at switch-off. Fig.2 shows what is required. Start by removing the 470kΩ resistor to the right of IC3, the 10kΩ resistor directly below it and the 10μF electrolytic capacitor to the left of S1.

Since it's a double-sided board, it has plated through-holes so the easiest way to remove the resistors is to clip their leads off close to the body, then pull the stubs out with pliers while heating the solder joints. The holes can then be cleared with a solder sucker. The electro can be rocked out while heating the pads and gently pushing on the body and its mounting holes cleared of solder too.

Next, cut the track to pin 9 of IC2, on the underside of the board (shown in Fig.2 with a red 'x'). Fit a fresh 470kΩ resistor and ZD2 to the pads originally used for the 470kΩ resistor,

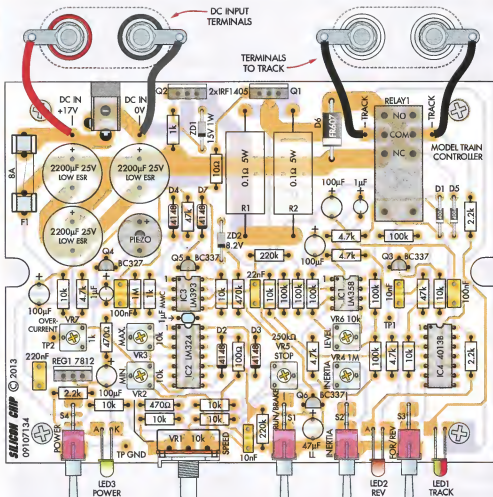


Fig.3: follow this parts layout diagram if you're building a new unit using the revised PCB (09107134). This version also adds transistor Q6 and two associated resistors.

with the cathode of ZD2 to the top of the board and 'air wire' them together. The 100Ω resistor and 10nF capacitor can be fitted as usual, with the added 220kΩ resistor wired across the new capacitor under the board.

Finally, run a short length of insulated wire (eg, Bell wire or Kynar) under the board, from the now-isolated pin 9 of IC2 to the top-most pad of VR7.

When you reassemble and test the unit, you should find that it now operates as before but without the switch-off pulse from the motor(s). If the unit fails to operate, check the voltages at pins 9 & 10 of IC2. Pin 10 should have a slightly higher voltage when power is applied; it's unlikely that it won't but if not, you may need to change ZD2 to the next lowest voltage (eg, 7.5V).

New PCB & further changes

To make it easier for new constructors, we can now supply a revised

PCB for the Li'l Pulser, incorporating all the modifications. This new PCB is coded 09107134 and is available via the SILICON CHIP Online Shop.

Fig.3 shows the overlay diagram for the revised PCB. You will need to refer to the original assembly notes in the July 2013 issue when building it.

In addition to the above changes, we have also added NPN transistor Q6 and two more resistors so that as soon as S4 is switched to the off position, Q6 turns on and rapidly discharges the 47μF control voltage filter capacitor, so there is no possibility of an output pulse regardless of how quickly the under-voltage lock-out circuit kicks in.

This is a bit of a 'belts and braces' approach, ie, it isn't totally necessary but it provides some extra cheap insurance against any sort of output pulse being delivered to the tracks.

With these changes the unit will now behave itself at switch-off but otherwise operate identically. **SC**