

active device (a four-layer diode), two resistors, one capacitor, and a 12-volt relay. Everyone breathed a sigh of relief.

But lo—the villain still lurks in the shadows! It seems that Huber's circuit, while simple, inexpensive, efficient, and reliable, does not work too well on the ever-popular "bug," at least according to Volkswagen owner Richard C. Gabbey (2002½ N. Wisconsin St., Racine, WI 53402). Dick writes that VW's, unlike American cars, use a uni-directional wiper motor controlled by a special conductive timing disk. As a result, Huber's circuit "kicked" the windshield wipers over a mere one-third of their normal travel distance.

Like most of our readers, Dick is inventive by nature. Instead of hanging his head in despair, he promptly modified Huber's design to achieve the arrangement shown in Fig. 6. Huber's original circuit is enclosed by the dotted line, with the only new component being a dpdt "Kick-Normal" switch. Except for the switch, the only other major change is the use of relay *K1*'s NC contact to furnish power to the wiper motor's "down position hot lead."

O.K., Beetle owners?

New Hobby Kits. Two new construction kits have been announced by Motorola HEP through its distributors. They are the HEK-3 Radio Amateur Kits retailing at \$5.95 that contain two r-f/i-f linears IC's and an RTL logic IC, and a project brochure showing how to make transmitters, amplifiers, etc. The other kit is the HEK-4 Home Handyman Hobby Kit at \$4.95 containing an SCR, a UJT, a silicon rectifier, and a silicon npn transistor. The brochure that comes with this kit illustrates 11 different and useful home applications for the semiconductors.

Manufacturers' Circuits. Designed for use as a variable-speed control for low-power universal motors of the type used in sewing machines, mixers, blenders and similar household appliances, the circuit shown in Fig. 7A was abstracted from the specifications brochure for GE's type C106 SCR. According to GE, the design may be used as a direct replacement for carbon-pile or rheostat type controllers and is suitable for any universal (ac/dc) motor requiring up to 1.5 amperes. Unlike many simple SCR control circuits, this version includes a speed-dependent feedback arrangement to insure adequate torque at all speed settings.

In operation, RC network *R1-C1-R2* provides an adjustable ramp-type reference voltage superimposed on the dc voltage developed by diode *D1*. The combined voltages are applied to the SCR's gate as a control signal through diode *D2*, but the reference voltage is balanced within the gate by the

learn electronics at home in spare time



you'll be turning that spare time into extra money very soon!

Learn the skills of electronics and help fill the critical shortage of trained electronics personnel. You can keep your present job and still turn spare time into extra money. The home study program of United Technical Institute has been drawn from a resident course taught in our Milwaukee, Boston, and Los Angeles schools; a course that has produced graduates now earning good pay in the electronics industry from coast to coast. UTI is a division of Career Academy, the world's largest private schooling organization. *Mail coupon today for colorful, free booklet with all the details.*

United Technical Institute

division of Career Academy

135 West Wells St. • Milwaukee, Wis. 53203
Dept. N087225



Please rush me your exciting free booklet with all the details of how I can train in the field of electronics.

Name Age

Address Phone

City/State/Zip

I am interested in Home Study Resident

CIRCLE NO. 34 ON READER SERVICE PAGE

Cut out high speaker costs!

Mail coupon and pay less for latest high-compliance cone-edge speakers for hi-fi stereo. Factory-to-you from CTS, pioneers of air-suspension speakers. Also available—rugged speakers for bass and lead guitar and other musical instrument amps.



CTS of Paducah, Inc.
1565 North 8th Street
Paducah, Ky. 42001

Please send Catalog of CTS speakers at factory-to-me prices. Specify:

- Hi-Fi Stereo Speaker Catalog
 Musical Instrument Amplifier Speaker Catalog

Name _____
Address _____
City _____ State _____ Zip _____

CIRCLE NO. 5 ON READER SERVICE PAGE

CAN YOU QUALIFY
income
FOR MORE RESPONSIBILITY
AS A **CIRCUIT DESIGNER?**



If you have a degree in engineering or formal training in electronics and work in the electronics industry, the Center for Technical Development's DIGITAL DESIGN PROGRAM (DDP-1) can make you more valuable as a trained circuit designer. DDP-1 is a new concept in practical home study courses designed to give you useable know-how fast. YOU CAN'T AFFORD TO WAIT ANOTHER DAY . . . WRITE FOR FULL DETAILS NOW!

We'll also send you information on our IC Logic and Power Supply courses.

Write Director, Dept. PE-031 0051H
THE CENTER FOR TECHNICAL DEVELOPMENT, INC.
517 East Main Street • Louisville, Ohio 40461

970-2

CIRCLE NO. 6 ON READER SERVICE PAGE

SOLID STATE

(Continued from page 89)

motor's residual counter-emf, coupled back through $C2$. If the motor slows down due to heavy loading, its counter-emf drops, permitting the reference ramp voltage to trigger the SCR earlier in the ac cycle, applying more power to compensate for the load and thus speeding the motor back up to its preset speed.

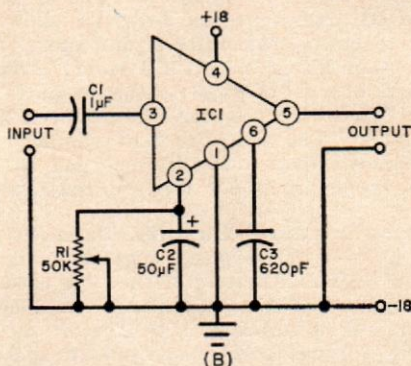
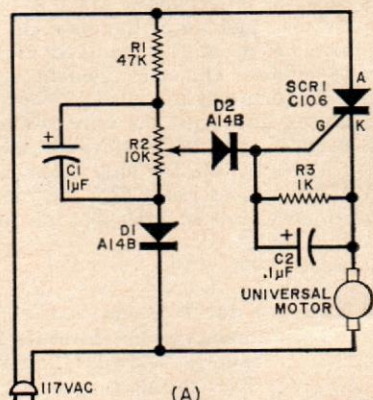


Fig. 7. Circuit at (A) uses SCR to control the speed of low-power universal motors used in appliances. Circuit (B) uses new electronic attenuator IC in remote volume control with 13 dB gain.

Featuring inexpensive components, the speed control circuit can be duplicated at modest cost. Except for linear potentiometer $R2$, the resistors are half-watt types, while both capacitors are 50-volt electrolytics.

With neither layout nor lead dress critical, the control circuit can be assembled on a perf board, small chassis, or etched circuit board. The SCR should be heat-sinked, of course, and all dc polarities must be observed. If adequate space is available within