

## Diodes and integrator brake small motors dynamically

by Stephen Wardlaw

Yale-New Haven Hospital, Dept. of Laboratory Medicine, New Haven, Conn.

Alternating-current motors used in position-sensing circuits must be quickly braked and stopped if the system is to retain its positional accuracy. In the case of a small shaded-pole motor, a dc source connected directly to its field winding brakes it dynamically by rapidly dissipating its kinetic energy. But if not turned off in time, the source will overheat the motor.

A safer way is to derive the dc voltage through a silicon controlled rectifier, a diode, and a resistance-capacitance network. Moreover, such a circuit costs less than an electromechanical switch and is simpler than a thermal-delay or momentary-contact switch.

As shown in the figure, the braking unit (within the dotted lines) must be placed in parallel with a manual electronic switch,  $S_1$ , that is used to trigger the braking of motor  $M$ . With  $S_1$  in the normally closed position, no voltage appears across the braking unit, and  $R_1$  bleeds

off any charge being stored in capacitor  $C_1$ .

When braking is desired,  $S_1$  is activated and thus opened, so that the positive half-cycle of the line voltage will appear across  $D_1$ ,  $C_1$ , and  $R_1$ - $R_3$  and the SCR will be triggered. This action, in addition to enabling a strong pulse of direct current to flow through the motor windings, partly charges  $C_1$ .

When the line current drops through zero and into its negative half-cycle, the SCR turns off and remains in that state until the ac input reaches its positive half-cycle again. The process is repeated until  $C_1$  is charged to near the peak value of the line voltage, at which time direct current will cease to flow. The SCR will not turn on again, because  $D_1$  will be permanently back-biased.

The 150-volt varistor helps to suppress line spikes. The fuse,  $F$ , is included as a safety precaution and will open if for some reason the braking unit continues to enable the power line to feed a relatively high direct current through the motor winding. Using the component values shown, the braking unit will enable the line to supply a pulsating dc to the motor for approximately 1 second—more than enough time to completely brake any small motor with a rating of up to ¼ horsepower or so. □

Designer's casebook is a regular feature in *Electronics*. We invite readers to submit original and unpublished circuit ideas and solutions to design problems. Explain briefly but thoroughly the circuit's operating principle and purpose. We'll pay \$50 for each item published.

**Fast reaction.**  $S_1$  initiates motor braking. Positive half-cycle of input voltage appears across  $D_1$ ,  $C_1$ ,  $R_1$ - $R_3$ , firing SCR and enabling direct current to flow through small shaded-pole motor.  $C_1$  charges to nearly peak value of input voltage during succeeding positive half-cycles, terminating process.

