

# PWM motor control

## With added duty cycle boost

By Rolf Blijleven (Netherlands)

This circuit is designed to allow a small DC motor to run at low rotational speeds. The motor is driven using a PWM signal, in which the duty cycle increases whenever the motor is forced to work harder.

It sometimes happens that you need to run a DC motor at slow speeds. The standard solution is to drive the motor with a squarewave signal having a low duty cycle. But if the motor is overloaded mechanically, the squarewave may deliver inadequate power, causing the motor to stall. A solution to this problem lies in a PWM (pulse width modulation) circuit with a variable duty cycle. Circuits offering a manually adjustable duty cycle are of course plentiful, but I wanted a duty cycle that varied

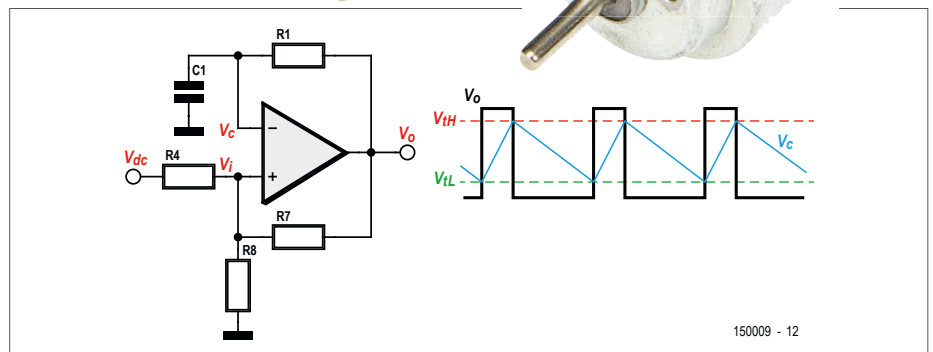


Figure 1. Functional diagram of a pulse generator using a single opamp.

PROJECT-INFORMATION

motor PWM

Duty cycle

entry level

intermediate level

expert level

30 minutes approx.

Soldering iron

Old motor from a CD/DVD drive

€15 / £12.50 / \$16 approx.

automatically. That should not be difficult, I thought. And it should also work without using a microcontroller! You take a PWM generator, use this to control the motor, measure the current through the motor and feed this back to the PWM generator as a control signal. With a couple of opamps, a MOSFET for the motor control, some resistors and capacitors plus a simple, single 5 V USB power supply it ought to succeed. I started out with the classic circuit in **Figure 1**, taken from the datasheet for the LM358 [1]. (The component numbers have been modified to accord with those in the definitive schematic in **Figure 2**.)

### Theory

The basic principle will be familiar to many readers:  $V_{DC}$  is a DC voltage (DC for *direct current*, not to be confused with DC for *Duty Cycle* [2]). At switch-on the

positive opamp input  $V_i$  is always greater than zero, whereas the capacitor voltage  $V_c$  at the negative input is still zero. Opamp output  $V_o$  goes into saturation at its maximum output voltage ( $V_{omax}$ ). The output voltage charges capacitor C1 via R1, until  $V_c$  becomes greater than  $V_i$ . We'll call that state  $V_{th}$ . When this point is reached the output flips back to zero, whereupon the capacitor is discharged via R1 to the point  $V_{tl}$  where  $V_c$  drops below  $V_i$ . Now  $V_o$  goes high again and the cycle repeats. The circuit is a combination of a saw-tooth generator and a Schmitt Trigger.

The great thing now is that you can drop these components into a couple of formulae, with which you can calculate exactly which values you need for a particular cycle. We can also approach this a bit more intuitively. Using any 741-type opamp that you choose,  $V_{omax}$  will

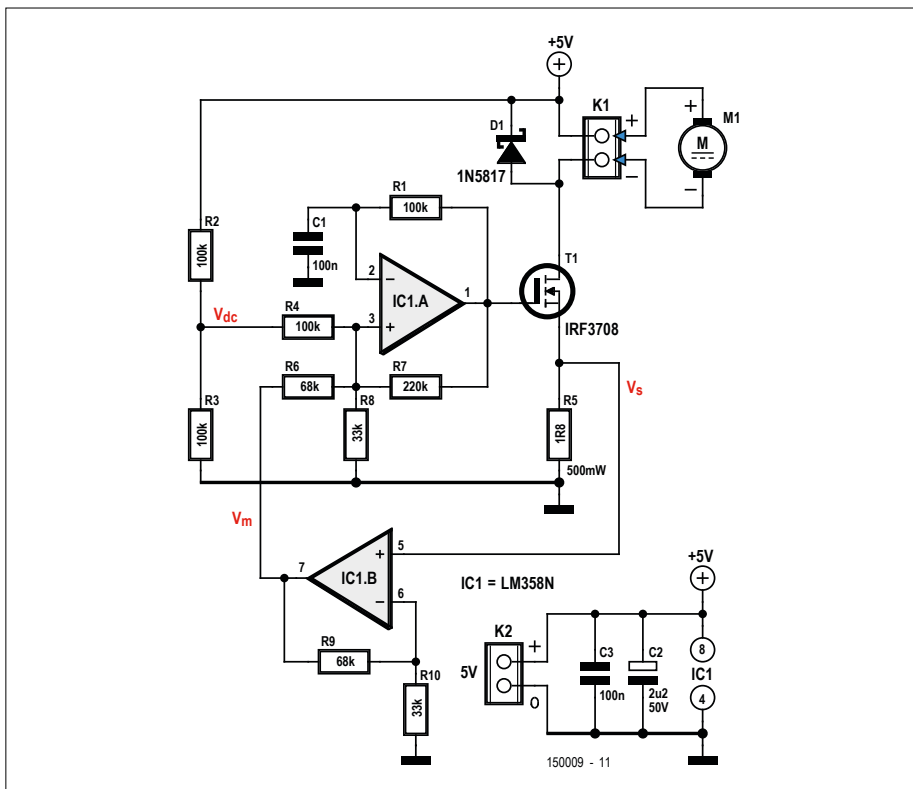


Figure 2. Generator IC1A drives the motor via MOSFET T1, whilst IC1B in conjunction with current sensor R5 assure a degree of positive feedback.

go up to 1.5 V below the supply voltage. If you wish to go all the way up to the supply rail, then take an opamp with an FET output stage, such as the CA3130 or CA3140.

The higher  $V_{DC}$  is, the higher  $V_i$  will be — and the higher the duty cycle. If  $V_i$  is always greater than  $V_c$ , then the duty cycle is 100% (in other words the full DC voltage).  $V_i$  is the determining variable

in the whole affair.

To make this more comprehensible, it may be better to think not in terms of resistance but of conductance. The higher the value of  $R_4$  (the lower the conductance of  $V_{DC}$  through  $R_4$  to  $V_i$ ), the less  $V_{DC}$  contributes to  $V_i$ , thus the lower the duty cycle.

The lower  $R_8$  is, the more the conductance of  $V_i$  to ground (GND) and consequently the lower the duty cycle. The lower  $R_7$  is, the greater the influence of  $V_{omax}$  on  $V_{th}$  and hence the greater the difference between  $V_{th}$  and  $V_{tl}$ . But what matters in duty cycles is the *sum* of  $V_{th}$  and  $V_{tl}$  and this does not change much with  $R_7$ , meaning that  $R_7$  has less influence on the duty cycle than  $R_4$  and  $R_8$ .

At this point you would choose  $R_4$ ,  $R_7$  and  $R_8$  to have a duty cycle that is always high enough to run the motor. But I wanted a duty cycle that was as low as possible and would automatically increase a little when the engine had to work harder.

## Circuitry

You can see the complete schematic in Figure 2 and let me say at the outset that the circuit does not allow itself to be domesticated willingly. More about that more later; the principles of the circuit come first.

### COMPONENT LIST

**Resistors**  
(5%/0.25 W, unless indicated otherwise)  
 $R_1, R_2, R_3, R_4 = 100 \text{ k}\Omega$   
 $R_5 = 1.8 \Omega \text{ } 0.5 \text{ W}$   
 $R_6, R_9 = 68 \text{ k}\Omega$   
 $R_7 = 220 \text{ k}\Omega$   
 $R_8, R_{10} = 33 \text{ k}\Omega$

**Capacitors**  
 $C_1, C_3 = 100 \text{ nF}$   
 $C_2 = 2.2 \mu\text{F}/16 \text{ V}$ , radial, 2 mm pitch

**Semiconductors**  
 $D_1 = 1\text{N}5817$   
 $T_1 = \text{IRF}3708\text{PBF}$   
 $\text{IC}1 = \text{LM}358$

**Miscellaneous**  
 $K_1, K_2 = 2\text{-way screw terminal block}$ ,  
0.2" pitch  
Small DC motor and gearbox (recycled  
from an old PC CD drive)  
PCB # 150009-1 from Elektor Store

$R_2$  and  $R_3$  fix  $V_{DC}$  at half the supply voltage. The PWM signal at the output of IC1A goes to a MOSFET that switches the motor on and off. Using  $R_5$  ( $1.8 \Omega$ ) we measure the current through the motor (nominally around 450 mA). This yields a voltage  $V_s$  of 0.8 V at normal loading, rising to 1.2 V when the motor must work harder. In that instance around 700 mA flows through  $R_5$ . But because the voltage and current are pulsed, the power ( $I^2R = 0.7^2 \times 1.8 = 0.9 \text{ W}$ ) in the resistor is reduced by the duty cycle to around 20%. A 0.5-W resistor for  $R_5$  will not take any notice of this.

$V_s$  is amplified a little using IC1B and the result goes via  $R_6$  to  $V_i$ .  $V_i$  rises slightly in consequence and as the motor becomes still more heavily loaded, it draws more current as appropriate.

This all sounds very straightforward but selecting the correct resistor values is not so easy. There are still some snakes in the grass. To begin, the frequency of the PWM signal decreases as the duty cycle

risers. You can see this in the formula. The charging time  $t_1$  and the discharging time  $t_2$  of C1 are decisive:

$$\text{duty cycle} = \frac{t_1}{t_1 + t_2} \times 100\%$$

The greater the charging period, the higher the duty cycle, but the frequency is  $1/(t_1 + t_2)$  and this then becomes lower. That gives us fewer pulses per second, making the motor speed fall (at a time when you actually want to keep it constant). If you increase the influence of  $V_m$  by using a lower value for R6, then you increase the duty cycle but lower the speed even further.

A shorter time constant ( $R1 \times C1$ ) was not a solution because the DC motor made an ominous sound at PWM frequencies above 75 Hz and above 120 Hz the screeching stopped. Furthermore, the voltage across R5 is a DC voltage with commutation ripple superimposed, caused by switching from one carbon brush to the other while the motor is running. At higher loading, the voltage across R5 is at a maximum and the ripple frequency also increases. This

makes sense, because the motor then turns more slowly.

Finally, the motor current (amplified and converted to voltage  $V_m$ ) was added to the *positive* input of the PWM opamp, achieving positive feedback. According to textbook theory this is a bad idea, in part because the impedance of the voltage source influences the summation. In fact that does not play a major role here. The output impedance of IC1B is very low and much lower than R6. The source impedance of voltage divider R2/R3 here is 50 kΩ, half of R4. I did also experiment with an emitter follower at the voltage divider to reduce the impedance, but that turned out to make hardly any difference to the operation.

If the circuit in Figure 1 using rather simple formulae in a spreadsheet was predictable, then the schematic in Figure 2 displayed some troublesome phenomena trapped in the mathematics. I decided to simply experiment — that is, after all, what breadboards were invented for.

And in this way I got it working. With the values given in the schematic and in the list of components I had a duty cycle of


around 17% at 55 Hz, increasing to 21% at 45 Hz under the toughest mechanical stress. This time I did not need to do anything more.

Elektor Labs have designed a small PCB for the circuit, which can be seen in **Figure 3**. This will always be handy in case you want to experiment but you will still have to adjust some resistor values for each type of motor. Next time, if the speed must be kept constant, I think I would design something with a microcontroller. ◀

(150009)
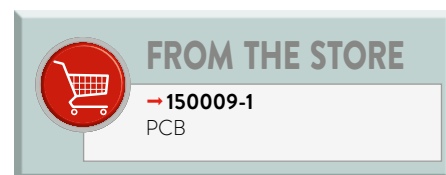
#### Web Links

- [1] LM358 data sheet:  
[www.ti.com/lit/ds/symlink/lm158-n.pdf](http://www.ti.com/lit/ds/symlink/lm158-n.pdf)
- [2] [http://en.wikipedia.org/wiki/Duty\\_cycle](http://en.wikipedia.org/wiki/Duty_cycle)



Advertisement

# Join the Elektor Community

## Take out a GOLD Membership now!




### Also available:

## The all-paperless GREEN Membership!

[www.elektor.com/member](http://www.elektor.com/member)

### GOLD Membership

- ✓ 6x Elektor Magazine (Print)
- ✓ 6x Elektor Magazine (PDF)
- ✓ Access to Elektor Archive
- ✓ Access to over 1,000 Gerber files
- ✓ Elektor Annual DVD
- ✓ 10% Discount in Elektor Store
- ✓ Exclusive Offers

### GREEN Membership

- ✓ 6x Elektor Magazine (PDF)
- ✓ Access to Elektor Archive
- ✓ Access to over 1,000 Gerber files
- ✓ 10% Discount in Elektor Store
- ✓ Exclusive Offers