

Solar heating temperature controller

Differential circuit gives precise control of a pump motor

by A. J. P. Williams Gwent College of Higher Education

This solar heating controller uses a recently introduced sensor to accurately detect the temperatures of a solar panel and a water tank. The circuit allows an electric pump to be controlled at precise selectable temperatures for optimum heat exchanger efficiency. The circuit is easily calibrated, and is not affected by interference from local mains wiring.

In the basic system of Fig. 1, a heat transfer fluid, usually water, is pumped through the solar collector where it gains heat. The fluid then passes through a heat exchanger coil where most of the heat gained previously is transferred to the stored water. The outputs from a temperature sensor attached to the collector output, and a second sensor attached to the storage tank operate a differential temperature controller. This controller switches the pump motor on when sensor 1 is hotter than sensor 2, which transfers heat to the stored water, and off when sensor 1 is cooler than sensor 2, thus preventing the stored water from being cooled during the night or when the weather is dull.

Because solar collectors are more efficient when they are operated at low temperatures, it is beneficial to run the system at the minimum temperature which will allow energy to enter the stored water and justify the pump operating.

For example, if the average rise in

temperature of the stored water is 40 deg C, and the stored water is increased by only a further 2 deg C with precise control, this represents a 5% increase in efficiency, or an extra 348Whr for each 150 litres of water heated.

Circuit details

The complete circuit in Fig. 2 is based on the Analogue Devices AD590K temperature transducer which is a constant current temperature sensor. The current through the device is almost independent of the voltage across it within the range of 4 to 30V. This characteristic ensures that any mains induced voltages in the leads cause negligible 50Hz current through the sensors. Connections to the sensors can be by an un-screened twisted pair of wires of up to 50m in length if required, provided that they are well insulated. It is essential that the connections to the sensors are well insulated and dry so that all of the sensor current is detected by the control unit. The current through each sensor is directly proportional to the absolute temperature of the sensor. Therefore, at 0 deg C or 273 deg K the nominal current is 273 μ A, and at 100 deg C or 373 deg K the current is 373 μ A. This

relationship also makes the device suitable for measuring temperature.


Because IC₂ has a high input resistance, the difference between the currents through the two sensors, $I_1 - I_2$ mainly flows through R₄. When the temperature of the stored water is greater than that of the collector, I_1 is greater than I_2 , and V_1 is positive. This causes pin 2 of IC₂ to become positive and the output at pin 6 to move close to ground. At this point D₅ cannot conduct and Tr₁ switches off the pump motor via the relay. When the temperature of the collector is greater than that of the stored water, I_2 is greater than I_1 , so V_1 is negative which drives pin 6 of IC₂ close to the positive rail. This in turn switches the relay and pump on via Tr₁ and D₅.


With a temperature difference of 1 deg C between S1 and S2, a current of 1 μ A will flow through R₄ which makes V_1 100mV. The value of V₃ is arranged to be approximately 125mV which ensures that V₂ can be varied from 0 to 100mV. As V₂ is increased it tends to switch Tr₁ off therefore, I_2 must be greater than I_1 to make V₁ sufficiently negative before Tr₁ can be switched on. Thus, adjustment of R₁₉ determines the collector temperature that switches the pump on. The range of R₁₉ is at least 10 deg C. At 25 deg C the tolerance of the current through the temperature transducer is $\pm 2\mu$ A, so V₁ could be ± 40 mV when it should be zero. To correct for any such unbalance between the sensors, and any input offset voltage on IC₂, V₄ can be varied from about 0 to 75mV. Varying R₁₉ and R₂₁ only has a small effect on the total resistance between pins 2 and 3 of IC₂ and point C respectively. This ensures that the calibration of different control units will be similar.

Feedback circuit

Positive feedback around IC₂ makes sure that V₁ must be made more positive than V₅ before Tr₁ can be switched off. This switch-off hysteresis enables the pump to be switched on when the collector is, for example, 5 deg C higher than the stored water, and off when the collector is 3 deg C higher than the stored water. The amount of hysteresis is determined by R₂₂ which is a log-potentiometer. This control is wired so that the low resistance end is connected to D₁. The hysteresis control can be calibrated over the range 0.4 to 9 deg C,

Fig. 1. Basic solar heating system. The pump only operates when the collector temperature is above that of the stored water.

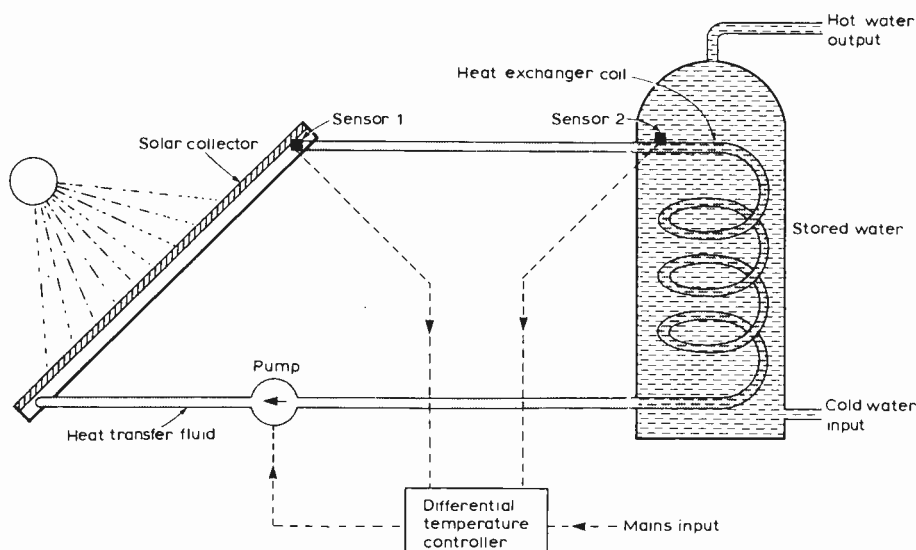

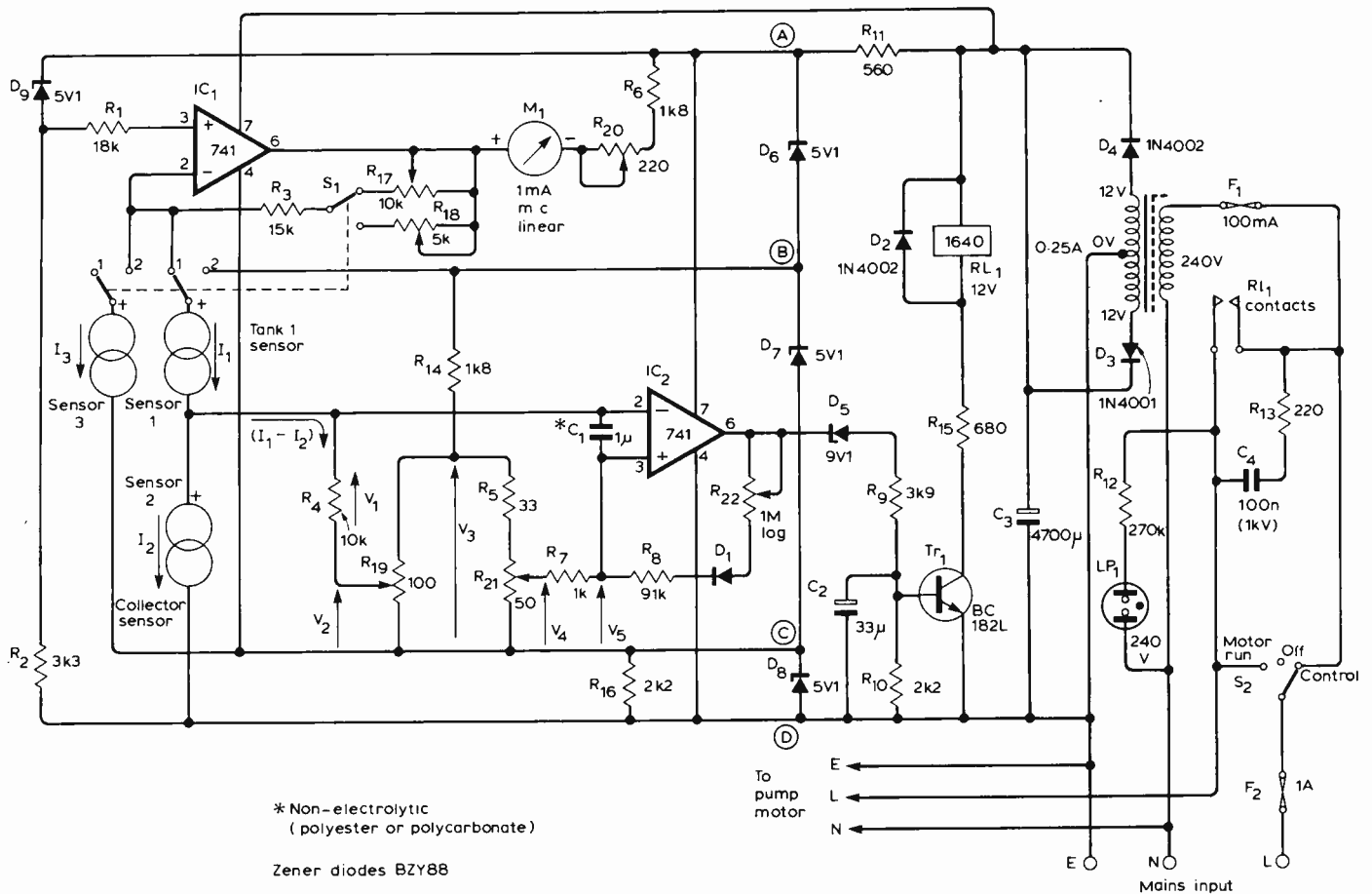

but for a temperature resolution of better than 0.1 deg C, the feedback resistance may be increased to 4.7MΩ.

Measuring circuit

The measuring circuit operates as a current-to-voltage converter where the current from S1 or S3 flows through R₃ and R₁₇ or R₁₈. The voltage at pin 6 of IC₁ moves sufficiently positive to maintain the sensor current through R₃ + R₁₇. The potential at pin 2 of IC₁ is always close to the potential at point B which ensures that S1 has the same internal power dissipation with SW1 in position 1 or 2. When the current through S1 is 273µA, and R₃ + R₁₇ is 18.68k, the p.d. across the two resistors will be 5.1V which holds the positive side of the meter at the same potential as point A. The meter then reads zero which represents 0 deg C. When the current through S1 is 373µA, the p.d. across R₃ + R₁₇ will be 6.97V with respect to point B. Therefore, the positive end of the meter will be 6.97 - 5.1V with respect to point A. The resistance in series with the meter can therefore be set to 1.87kΩ to represent 100 deg C. More sensitive meter movements may be used by changing R₃ + R₁₇ accordingly.

The temperature coefficient of the 5.1V zener diodes is comparatively low so that changes in ambient temperature only have a minor effect. This also applies to sensor S3 which may be used for monitoring any part of the system. A separate control for each sensor is not used because of their high linearity. The circuit may be simplified by omitting the measuring circuit and connecting the top end of S1 to point B.

Fig. 2. Complete circuit for the differential temperature controller. Sensors 1 and 2 are sited as shown in Fig. 1, and sensor 3 can monitor the temperature anywhere in the system.

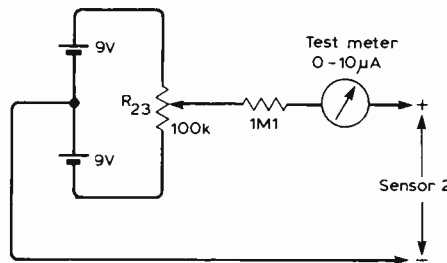


Fig. 3.

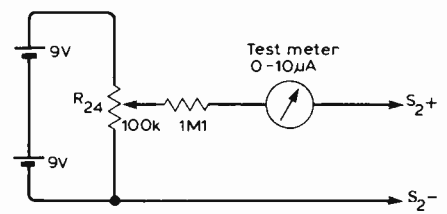


Fig. 4.

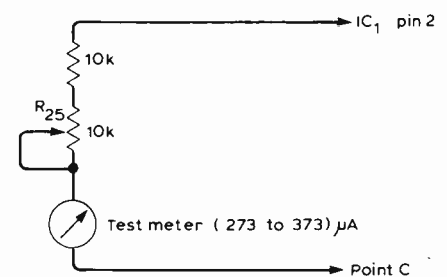


Fig. 5.

Calibration

For the differential temperature, remove S1 and S2, connect the calibration circuit of Fig. 3 in place of S2 and switch SW1 to position 2, or replace S3 by a 15kΩ resistor to prevent the meter reading backwards. Load the pump motor output with a 40W lamp so that LP₁ can turn on. Set the slider of R₁₉ to within a few degrees of point C and mark as zero degrees temperature difference. Set R₂₂ for minimum hysteresis, i.e. maximum resistance, and then set the current on the test meter to zero by adjusting R₂₃. Slowly adjust R₂₁ until LP₁ just lights, and set R₂₃ to give 1µA on the test meter. Adjust R₁₉ until LP₁ goes out, and then return R₁₉ slowly until LP₁ just lights. This position is marked 1 deg C on the dial of R₁₉. Reset R₂₃ for 2µA and re-adjust R₁₉ until LP₁ just lights. The point at which R₁₉ just lights LP₁ is marked as 2 deg C. This procedure is repeated at 1µA steps to calibrate up to 10 deg C.

To calibrate the hysteresis control, connect the circuit in Fig. 4, and set the differential temperature control to zero. Set the hysteresis control to maximum, i.e. minimum resistance. Adjust R₂₄ until LP₁ lights and then set R₂₄ so that the meter indicates the hysteresis required, e.g. 2µA for 2 deg C hysteresis. Slowly move the hysteresis control to the point where LP₁ goes out and mark the calibration point. Repeat the procedure for temperatures from 0.5 to 9 deg C.

For the temperature measuring circuit the following method is suitable if an accuracy of ±3 deg C is sufficient,

or ± 2 deg C if the more expensive AD590L sensor is used. Connect the test circuit in Fig. 5, and set SW1 to position 1. Adjust R_{25} to give $273\mu\text{A}$ on the test meter and set R_{17} so that M1 indicates zero, i.e. 0 deg C. Switch SW1 to position 2 and adjust R_{18} so that M1 indicates zero. Set the test meter to indicate $373\mu\text{A}$ by adjusting R_{25} and adjust R_{20} so that M1 reads full scale, i.e. 100 deg C. If the meter M1 is scaled 0 to 100 in 10 steps, then each step will indicate an increment of 10 deg C.

For maximum accuracy, the sensors are used directly. Keep S1 and S3 at 0 deg C, switch SW1 to position 1 and adjust R_{17} so that M1 indicates zero. Switch SW1 to position 2 and adjust R_{18} so that M1 indicates zero. Keep S1 at 100 deg C, switch SW1 to position 1 and adjust R_{20} until meter M1 indicates full scale, i.e. 100 deg C.

The linearity of the AD590K sensor is better than ± 0.5 deg C over the range -55 to $+150$ deg C, but because all of

the sensors have the same general characteristic they should track within about 0.1 deg C.

It is not easy to check the accuracy of the switching-temperature differences by varying the temperature of the sensors because the control is more precise than most readily available temperature measuring instruments. The overall error for differential temperature and hysteresis is generally less than ± 0.3 deg C.