


Temperature dependent power controller

By using a 723C i.c. regulator as a sense-bridge, a low-cost water temperature controller can be constructed. The base-emitter junction of a BC183B senses the water temperature and gives a base-emitter voltage variation of about 2mV per deg C in the range 0 to +100 deg C. This voltage change is amplified in the collector circuit and applied to the non-inverting input of a comparator within the i.c. A voltage set by R_2 is applied to the inverting input, and determines the sensor temperature at which the comparator switches its output positive. A stable supply for this part of the circuit is provided by V_{ref} . Rectified a.c. is applied to the CL input through a delay network R_4C which allows a positive pulse to pass from the comparator to V_o just after the zero-crossing point of the applied a.c. This pulse drives the triac via a transformer of 36 s.w.g. wound on a $1in \times \frac{3}{8}in$ ferrite rod.

Positive feedback around the comparator is applied through isolating diode V_z which ensures that feedback is only effective when a pulse appears at the output. A 0.5Hz triangular wave, generated by IC_2 , is applied to the input of the comparator and provides proportional pulse width modulation. The amplitude of this waveform defines the proportional bandwidth of the controller, which is 0.5deg C with the values shown.

Control of a three gallon well-stirred water bath at 40 deg C is better than ± 0.05 deg C. A thermistor may be substituted for the transistor to give a wider temperature range and less sensitivity to ambient temperature.

R. L. Hooper
Christchurch
New Zealand

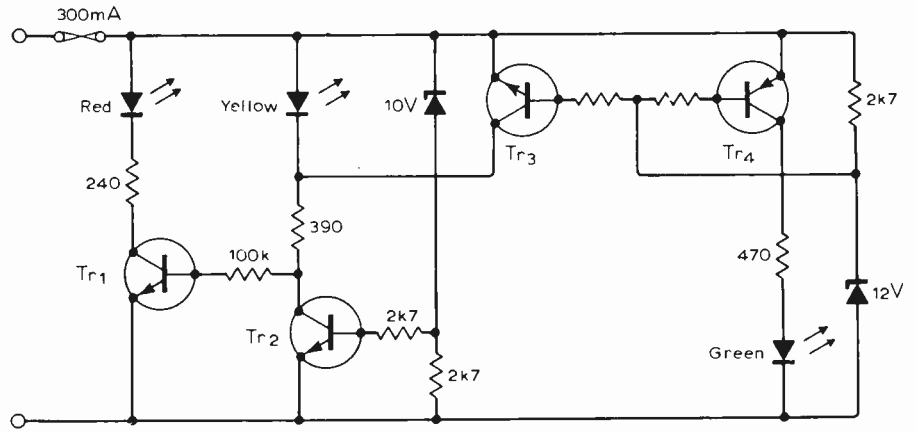

Automotive voltage indicator

An indication of battery voltage is useful to the motorist for monitoring the battery's capacity to deliver current, and as a check on the efficiency of the dynamo or alternator. This circuit is a solid-state alternative to a moving coil meter. The table shows the outputs obtained over the critical range of 10 to 14V.

When the input is below 10V, Tr_2 , Tr_3 , and Tr_4 are off and Tr_1 is turned on. As the voltage rises the 10V zener diode begins to conduct, Tr_2 receives base current and turns Tr_1 off.

At approximately 11V both Tr_1 and Tr_2 are on, but at 12V only Tr_2 is on. Similarly, Tr_4 is turned on as the voltage rises to 14V and the 12V zener conducts.

Transistor Tr_3 takes current from the yellow l.e.d. and turns it off while Tr_2 remains in conduction to keep the red l.e.d. off. The circuit can be easily modified for different voltages by changing the zener diodes.

Red	Yellow	Green	Voltage
1	0	0	$\leq 10V$
1	1	0	11V
0	1	0	12V
0	1	1	13V
0	0	1	$\geq 14V$

S. C. Mathur
Weybridge
Surrey

