

Transformers and optocouplers implement isolation techniques

Maintaining high precision can be a formidable task when you're taking measurements in industrial environments. Fortunately, there are ways to overcome this problem using readily available components.

Jim Williams, National Semiconductor Corp

High electrical-noise levels and excessive common-mode voltages complicate making safe, precise measurements in industrial environments. This article shows how to use transformers and optoisolators to isolate motors, transducers, converters or other real-world interfaces from control circuitry.

The conflicting requirements for high accuracy and total input-to-output isolation call for unusual design techniques. Typically, you use transformers and optoisolators to galvanically isolate the input terminals of a signal-conditioning amplifier from its output terminal.

This technique breaks the common ground connection and eliminates noise and common-mode voltages.

A simple, isolated signal conditioner

Several examples demonstrate how to include these isolation devices in your circuits. In the first, a wide-band audio transformer permits safe, ground-referenced monitoring of a motor powered directly from a 115V ac line (Fig 1a). The floating amplifier's inputs connect across a brush-type motor. The R_1R_2 network and the transformer's turns ratio divide the motor voltage by 100 and simultaneously allow a ground-referenced amplifier output. The neon bulb

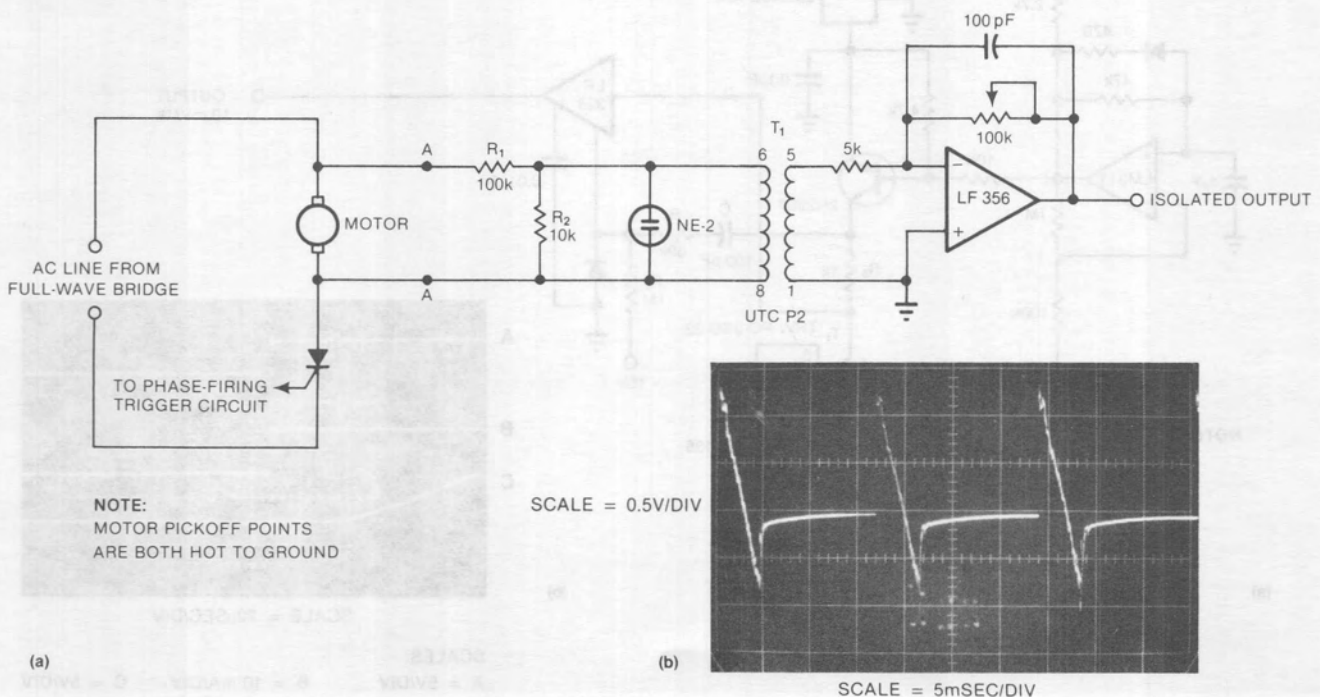


Fig 1—Safe ground-referenced monitoring is possible using a wide-band audio transformer (a). The circuit's fast response (b) permits monitoring of SCR turn-on as well as motor-brush noise.

Isolated pressure transducer uses battery power

to a 0 to 1000-psi input.

Fig 4 diagrams another measurement circuit that uses a transformer to interface to a pressure transducer. Operating from a 1.5V power supply (battery or solar cell) with a current drain of approximately 1 mA, this circuit develops a transformer-isolated frequency output. The pressure transducer's potentiometer output feeds a voltage-to-frequency converter (VFC), in which an LM10 input amplifier makes Q_1 's collector current linearly proportional to V_{IN} over a 0 to 400-mV range. In addition, the LM10's reference amplifier develops a stable and constant Q_2 output current. Transistors Q_3 through Q_{10} form a relaxation oscillator; every time the voltage across C_1 reaches 0.8V, Q_6 resets it to 0V differential.

Normally, this basic circuit isn't very accurate; the

dead time arising while Q_6 is saturated generates a large (1%) nonlinearity in the V/F transfer curve. However, R_X introduces a term in Q_2 's reference current that's linearly proportional to the signal, and this modulation corrects the transfer nonlinearity.

The circuit employs MM74C240 inverters because they're the only uncommitted devices available with a sufficiently low threshold (0.6 to 0.8V) to operate from a supply as low as 1.2V. Because Q_{12} 's V_{BE} acts as a temperature sensor, the 49.9-k Ω resistor in Q_2 's emitter provides a gain-TC trim function: If the output frequency is 100 ppm/ $^{\circ}$ C too high, you can cut the resistor to 20 k Ω ; if it's too low, add resistance in series with the resistor.

Isolating a complete A/D converter

You can use transformers for industrial-isolation tasks other than interfacing to various transducers. Fig 5a, for instance, shows a complete 8-bit A/D converter with all I/O lines fully isolated from system ground. In addition, the converter operates without an external


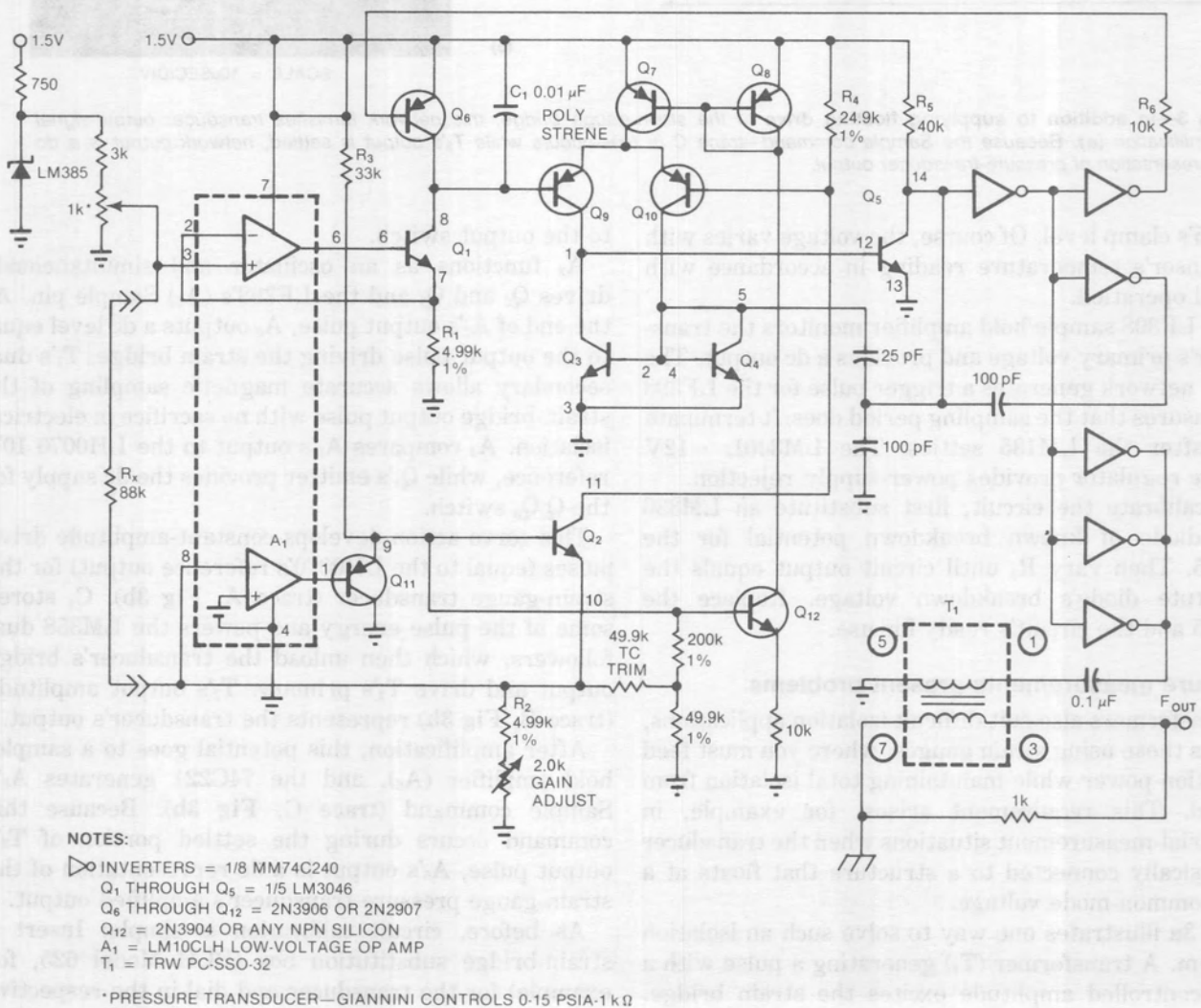


Fig 4—Capable of operating from battery or solar cell, this pressure-measurement circuit has a fully isolated frequency output.

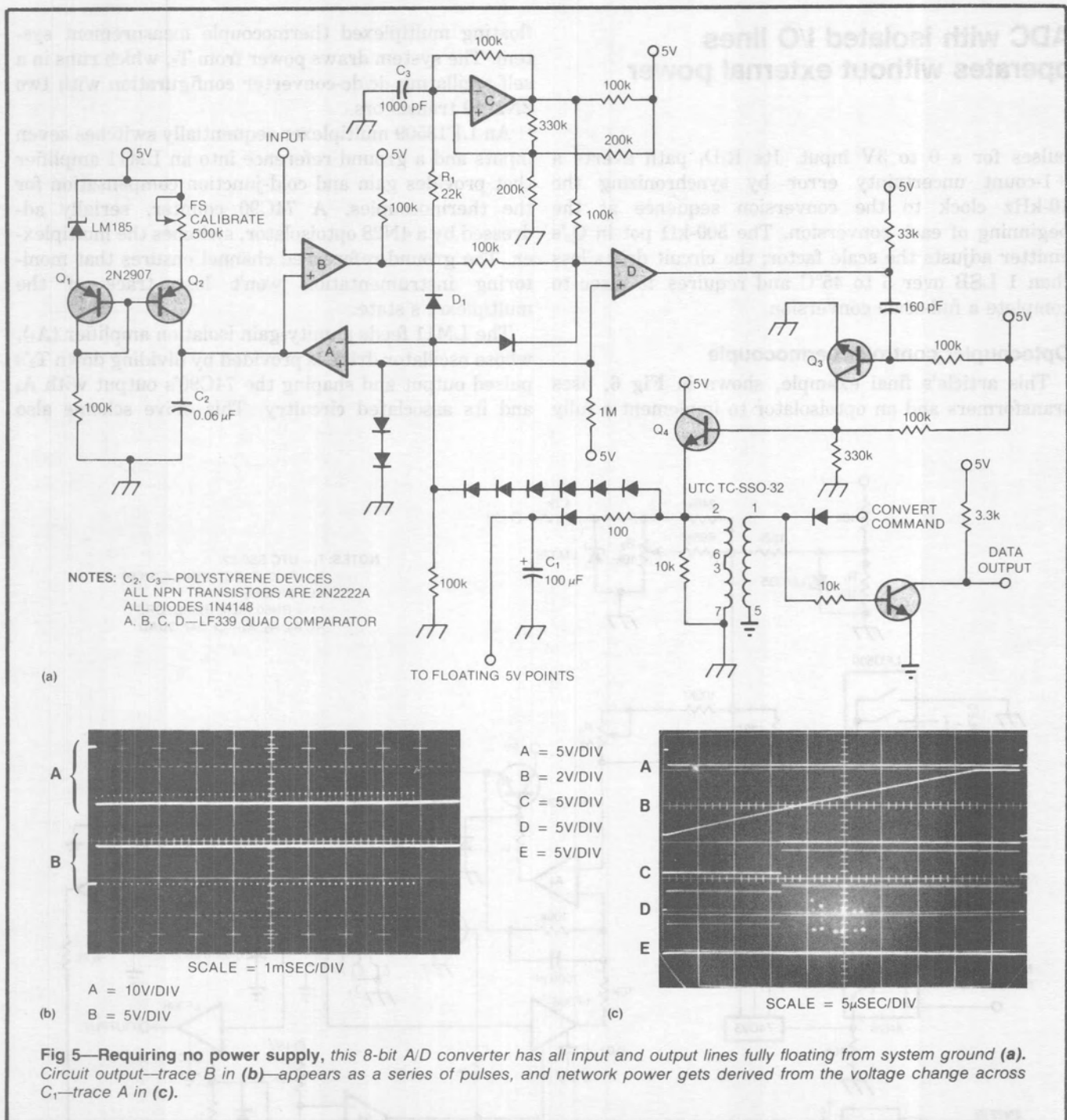

power supply.

To initiate circuit operation, apply a pulse (trace A, Fig 5b) to the transformer's Convert input. This pulse simultaneously forces the Data Output line LOW (trace B, Fig 5b) and propagates across the isolation transformer. The secondary winding charges C₁ to 5V (trace A, Fig 5c)—the supply voltage for the floating ADC. This winding's voltage also starts the A/D conversion by biasing comparator A's inverting input LOW, and the biasing forces comparator A's output LOW, discharging C₂ (trace B, Fig 5c).

Simultaneously, the 100-kHz oscillator (trace D, Fig 5c) formed by comparator D and associated components gets forced LOW (trace E, Fig 5c) by two series resistor/diode combinations. Note the lack of oscillation

while the Convert command pulse is HIGH. When that command goes LOW, the Q₁Q₂ current source charges C₂. During this period, comparator C's oscillator is enabled, and comparator D outputs a stream of 10-kHz clock pulses.

When the ramp voltage across C₂ (trace B, Fig 5c) exceeds the circuit's input, comparator B's output goes HIGH (trace C, Fig 5c), forcing comparator D LOW. The number of pulses that comparator D outputs is directly proportional to the input voltage. Q₃ and Q₄, used to modulate the data pulse stream back across the transformer, amplify these pulses. The diode string ensures that the data doesn't inadvertently trigger comparator A.

The design shown in Fig 5a produces 0 to 300 output

ADC with isolated I/O lines operates without external power

pulses for a 0 to 3V input. Its R_1D_1 path averts a +1-count uncertainty error by synchronizing the 10-kHz clock to the conversion sequence at the beginning of each conversion. The 500-k Ω pot in Q_2 's emitter adjusts the scale factor; the circuit drifts less than 1 LSB over 5 to 45°C and requires 45 msec to complete a full-scale conversion.

Optocoupler controls thermocouple

This article's final example, shown in Fig 6, uses transformers and an optoisolator to implement a fully

floating multiplexed thermocouple measurement system. The system draws power from T_2 , which runs in a self-oscillating dc/dc-converter configuration with two 2N2219 transistors.

An LF13509 multiplexer sequentially switches seven inputs and a ground reference into an LM11 amplifier that provides gain and cold-junction compensation for the thermocouples. A 74C90 counter, serially addressed by a 4N28 optoisolator, switches the multiplexer. The ground-referenced channel ensures that monitoring instrumentation won't lose track of the multiplexer's state.

The LM11 feeds a unity-gain isolation amplifier (A_1), whose oscillator drive is provided by dividing down T_2 's pulsed output and shaping the 74C90's output with A_2 and its associated circuitry. This drive scheme also

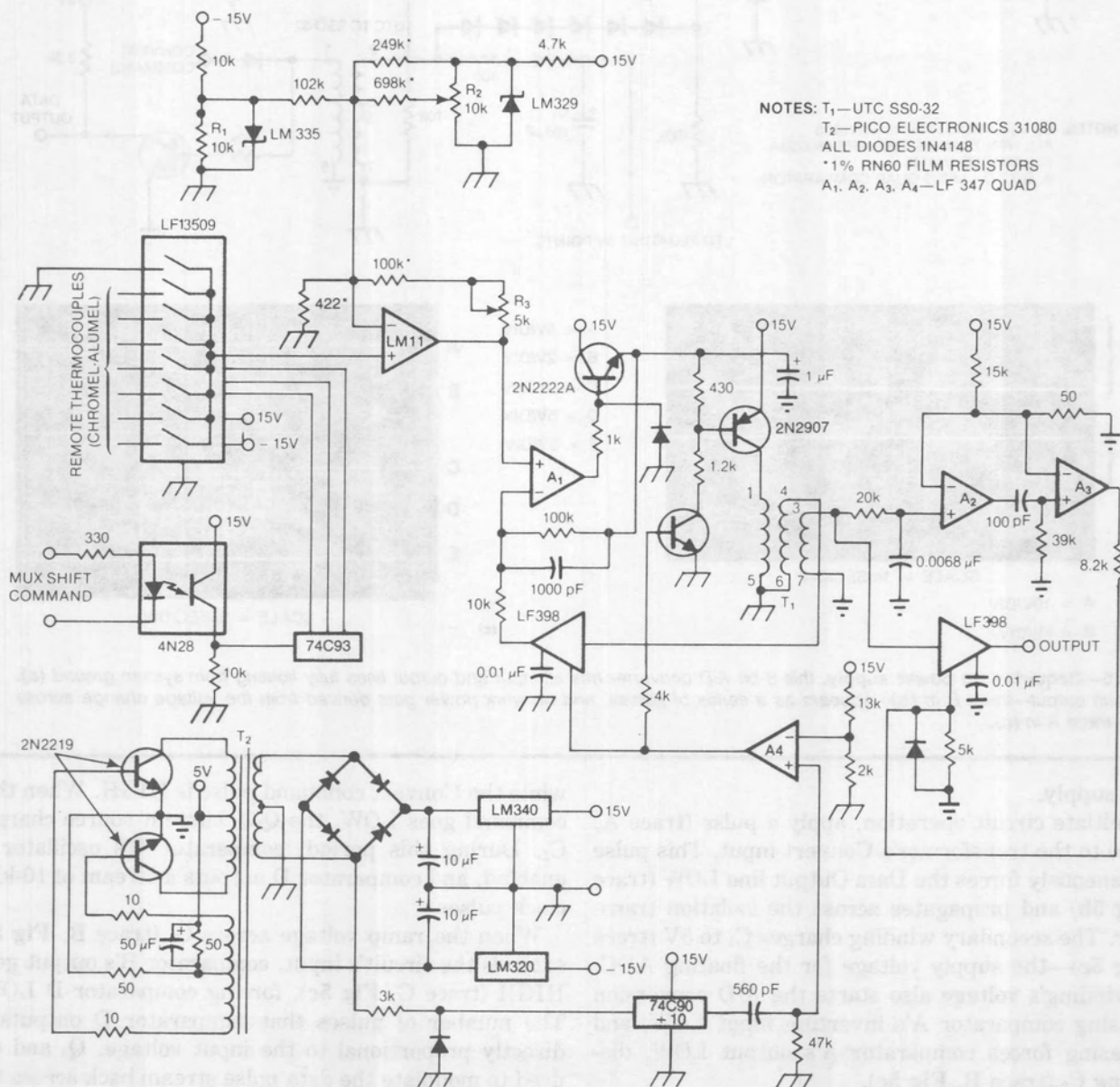


Fig 6—Supplying power to its floating system, this thermocouple measurement system employs a multiplexer that sequentially switches seven inputs and a ground reference.

Transformer, optoisolator combine in multiplexed thermocouple system

prevents unwanted interaction between the dc/dc converter and isolation amplifier.

The network develops a pulse across T_1 's primary—pulse amplitude depends directly on the LM11's output. T_1 's secondary feeds the pulse into an LF398 sample/hold amplifier. The trigger pulse for this amplifier is delayed to ensure that T_1 output sampling occurs well after settling.

Outputs from the LF398 and LM11 are identical. You

can therefore monitor the fully floating thermocouple with grounded test equipment or computers. The most effective cold-junction compensation results when you hold thermocouple leads and LM335 isothermal.

Calibration for the circuit involves a 6-step procedure. First, adjust R_3 to set the LM11's gain at 245.7. Then short the noninverting input of the LM11 and LM329 to floating common, then adjust R_1 for a circuit output of 2.982V at 25°C. Next, remove the short across the LM329, then adjust R_2 for a circuit output of 246 mV at 25°C. Finally, remove the short from the LM11's input and the circuit is ready to use. **EDN**