

Simplifying sum-correction logic for adding two BCD numbers

by Robert D. Guyton
Mississippi State University, Mississippi State, Miss.

To add two numbers in binary-coded decimal form, much less logic hardware is needed if one of the numbers is converted to the excess-6 binary code before the addition is done. The other number remains unchanged.

The block diagram of (a) outlines the approach. One BCD input is converted to the excess-6 code by a second-level logic circuit, which is drawn in (b). This translated number and the unchanged BCD number are then added by a 4-bit binary adder. The resulting output

carry is correct, but the sum must still be corrected—and can be corrected by a simple second-level logic circuit, rather than a multilevel type of logic circuit based on half and full adders.

The BCD-to-excess-6 translator circuit needs four NAND gates and three inverter gates. The rest of the over-all addition circuit is shown in (c): the four-bit binary adder requires four full adders, while the sum-correction circuitry requires 10 NAND gates and three inverter gates.

The complete excess-6 addition circuit, therefore, consists of 14 NAND gates, six inverter gates, and four full adders. As against an addition circuit based on excess-3 code conversion, that's a savings of six NAND gates, three inverter gates, one full adder, and two half adders. □

Conserving logic hardware. The circuit for adding two binary-coded-decimal numbers can be implemented with fewer devices by changing one of the BCD numbers to the excess-6 code format. When this conversion is done, simple logic gates can be used to perform the necessary sum correction. The figure shows the circuit's block diagram (a), the excess-6 code translator (b), and the complete circuit (c).

