

Alternating LED blinker uses four parts


ANDY MENG, CINCINNATI, OH

The circuit in **Figure 1** is an easy-to-make attention-getter and runs for a week or longer on two AA cells. In September, I used this circuit for a school fundraiser, and it helped me generate more than \$100. My dad showed me a circuit in *EDN* that did the same thing, but it uses more parts (see “Alternating LED flasher uses minimal parts,” *EDN*, Nov 20, 1997, pg 104).

The main element of this circuit is LED₁, a Radio Shack 276-036 blinking red LED. D₁ can be almost any silicon diode. The forward bias of D₁ brings the turn-on voltage of LED₂ up to 2.5V. R₁ is a current-limit resistor for LED₁, and this resistor also reduces the current of LED₁ for longer battery life.

LED₂ is a Radio Shack 276-041 red LED. When you apply power, LED₁ turns on and drops the voltage across LED₂ to 1V. When LED₁ turns off, the voltage across LED₂ equals 3V, and LED₂ turns on. (DI #2172) **EDN**

To Vote For This Design, Circle No. 420

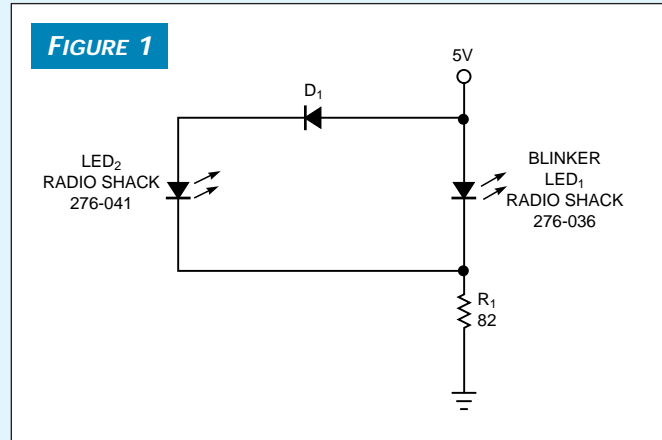

This blinking-LED circuit, designed by a seventh grader, uses only four parts.