

## DC LAMP FAILURE INDICATOR

The very simple circuit here provides an on-if-good function for a lamp. D1 and D2 should be generously rated as they are outside the warning loop. On a car type DO4 is recommended for mechanical support. If all the lights on a car are to be monitored the diodes can be mounted in blocks behind the lamp housing that the wiring harness reaches first. A 'line of light' type LED makes a convenient display.

