Automatic night-light feeds directly from the ac line

Abel Raynus, Armatron International Inc, Malden MA

There are many approaches to the problem of activating a light when it becomes dark, and a recent Design Idea covers this topic (**Reference** 1). Some approaches require a dc power

supply and an electromechanical relay, but a better approach involves feeding the device directly from the ac line, minimizing the number of components (Figure 1).

The heart of the device is a light-sensitive cadmium-sulphide resistor, P_R , with a resistance of approximately 200 $k\Omega$ in the dark and decreasing to a few kilohms in the light. P_R and capacitor C_1 form an ac-voltage divider. In daylight, the voltage across P_R is too low to generate the required gate-trigger current to turn on bidirectional ac switch Q_1 , thus keeping the loadusually a lamp—off. When it becomes dark, P_R 's resistance rises, resulting in an increase in the TRIAC's gate current that triggers the TRIAC and lights the lamp.



The circuit uses inexpensive, offthe-shelf components, including the VT90N1 photoresistor; a 0.1-µF, 275V capacitor; and an L2004F61 TRIAC with a load current of 4A rms, a peak blocking voltage of 200V, and a gatetrigger current of 5 mA. The exact specifications of these components are not critical; you could use others instead.

Editor's note: Attributes worth mentioning include the fact that the

capacitor introduces a phase shift, which places the peak of the gate voltage close to the zero crossing of the load's sine wave for optimum turnon timing. Another benefit is thermal hysteresis, which occurs due to the reduction of the required triggering voltage and current as the TRIAC warms up after the initial turn-on.EDN

REFERENCE

Tran, Chau, "Simple nightlight uses a photoresistor to detect dusk," *EDN*, Dec 15, 2011, pg 49, http://bit.ly/ HPi1GG.