



Bruce Trump Feb 19, 2013

We've included device-level [ESD](#) performance of our ICs in data sheets for many years. But these figures apply to an integrated circuit *before* soldering onto your circuit board. What about ESD tolerance *on your PCB*?

We qualify the ESD performance by zapping each pin multiple times on several devices. It simulates nasty mistreatment that might occur during handling and assembly. Without internal ESD protection circuits, damage could occur with static charges as low as 10V.

OPA314 EDS Ratings

ESD Rating	Human Body Model (HBM)	4000	V
	Charged Device Model (CDM)	1000	V
	Machine Model (MM)	200	V

But you're also concerned (maybe more concerned) with ESD tolerance after PCB assembly and during operation. An IC is generally much more robust after assembly on a circuit board. Power supply connections have bypass capacitors that can absorb sizable discharges. Input and output connections to the board generally have series resistance and PCB trace inductance. Capacitance to ground, even if only from the PCB trace, increases the ability to absorb a static discharge without damage.

You can add additional diode clamps or zener-like protection devices¹ that will greatly improve ESD tolerance of your complete product or equipment. Figure 1 shows a basic approach—and [more information here](#).

 


Figure 1.

This is about *survival* of your circuitry but you should also consider *functional disturbances*. This might include gross overloads of analog circuitry that require a long recovery time. Scrambled bits in digital circuitry or the system processor could be an even bigger problem. You probably cringe as I do when you draw a static spark as you touch your PC. Even though there may be no permanent damage to the hardware, an ESD “hit” can cause a system reset or lost data. You, with analog skills, may be the best person to guide the PCB layout, system layout and grounding to assure your system or product can withstand a zap without lost data or reboot.

Deliberate planning and execution will help achieve good results. Think about where the current flows during a static discharge. Consider both polarities of current flow to assure a safe current path.

It’s best to confine the discharge current path close to entry point. A discharge to the input ground terminal should find an easy path to earth ground without snaking around your circuit board. Keep the current path away from parallel lines that could be disturbed by capacitive or inductive coupling. A discharge to the input terminal must find a current path to ground. The diode clamps shown in figure 1 provide a short path to the power supplies, then through the bypass capacitors to ground.

Consider the same issues for an output terminal or any other likely point of conductive contact with your product or equipment.

With careful design and thoughtful PCB layout, you can improve the ESD tolerance of your system, including *survival and functional tolerance*. If you have big problems, we have an expert available for consultation. Jae Park has helped numerous customers sort out difficulties in their boards and systems. Reach him through our [E2E forums](#) specific to the product type relating to your issues.

Have you solved a tricky ESD sensitivity problem? Tell us how, below.

Bruce email: thesignal@list.ti.com (Email for direct communications.)

Check out other interesting topics... [Table of Contents](#) for all *The Signal* blogs

- Note 1) In a prior [blog on EOS protection](#), I lamented that many protection devices had too much leakage current for many precision circuits. These [new 5V protection devices](#) have lower leakage.

4 comments 0 members are here



[Antenna Head](#) *over 12 years ago*

Bruce- You have completely ignored Spark Gaps. Where ESD is concerned, nothing is more fun and exciting than Spark Gaps. They take up very little board space, can easily be located on the bottom side of the board, and generally cost nothing. The ionization potential is easily adjusted by the gap length and geometry, and are pretty much a mandate when really serious voltages are present. A spark gap at the connection to the outside world, following by a small resistance (like 30-100 Ohms) and then the diode clamps you suggest make for a very fine suppression network.



[Bruce Trump](#) *over 12 years ago*

Thanks for the excellent comment. How appropriate that you, "Antennahead" would mention the spark gap. Erecting conductors in the sky gives you a special appreciation for their value. It's a great way to dissipate a large share of a major ESD event. The semiconductor protection then deals with the remaining energy. Discharge tubes are also useful. The ubiquitous NE-2 neon lamp breaks down about about 65V, or so, and is sometimes used to help deal with ESD on inputs. Both the spark gap and neon lamp have very high impedance up to the discharge voltage. -- Bruce



[Dorian Barladeanu](#) *over 11 years ago*

The ESD problem becomes tricky on isolation amplifiers as AMC1100 (AMC1200) if the isolation have to be kept at levels of 1000V. I am facing such a problem when one side of the amplifier is earthed and the second is zapped with 15kv air discharge. If there is any suggestion it will be warmly welcomed. Thanks

Dorian



[Bruce Trump](#) *over 11 years ago*

Dorian-- I would think that an ESD event at the input of an isolation amplifier would be applied and referenced to the input side ground of that device. In this case, the advice of this blog would still apply. If an ESD event is applied between the input and output side grounds, other parasitic and component capacitance (such as from the isolated power source) would help dissipate the ESD pulse. I doubt that a 15kV test event would produce anywhere near 15kV across the isolation barrier in a complete system application circuit board. I see that you have posted question on the TI forums. This is probably the best place to handle the specifics of your case. Regards-- Bruce.