

40 SHOOT-OUT

□ The object of "Shoot-Out" is to test your reaction time against your opponent's. A third person acts as referee and begins the duel by pressing S1, which lights LED1. Upon seeing LED1 lit, you try to outdraw your opponent by moving S2 (or S3) from "holster" to "draw" before he does. If you do, D2 (or D3 if you use S3) will light first and will automatically prevent the other LED from lighting. A clear winner every time. This is a great party game for children.

PARTS LIST FOR SHOOT-OUT

IC1—4011 NAND gate

LED1-LED3—Light-emitting diode

R1—2,000-ohm, ½-watt resistor

R2, R3—1,000-ohm, ½-watt resistor

S1—Pushbutton (doorbell) SPST switch

S2—Toggle-type SPDT switch

S3—Toggle-type SPDT switch

