

## HEADLIGHT OPERATED GARAGE DOOR OR LIGHT SWITCH

- FEATURES:
- Relay contact will close when light hits photodiode.
  - Sensitivity adjustment to prevent false triggering.
  - Low battery drain

### PARTS LIST:

- 1 HEP 312
- 1 HEP 320
- 1 HEP 156
- 1 Resistor, 680 ohms, 1/2 Watt
- 1 Potentiometer, 25K
- 1 Push Switch, Normally Closed
- 1 Relay, Potter-Brumfield RS5D, 6VDC
- 1 Battery, 9VDC

