

Fig. 2. Curve shows how thermostat setting is affected by R4.

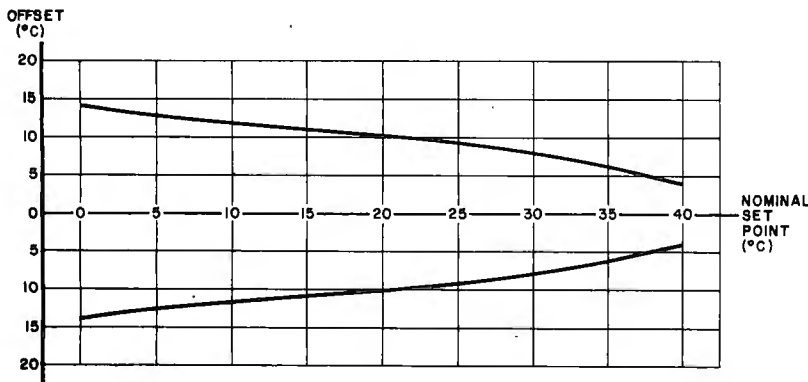


Fig. 3. Worst-case recalibration curve for a non-typical D5.

R4 is set properly, then the diac D5 (also called a silicon bilateral switch, or SBS) will turn on and latch. Capacitor C1 is sufficiently large to hold D5 in its on state from the firing point of TDR1 (less than 90°) to at least 180°. Of course, if TDR1 fires at a sufficiently low voltage (sensor hot), then there will not be enough voltage to fire diode D5.

But if D5 does fire, it will do so prior to 90° and remain in this state through 180°. Therefore, SCR1 has positive gate current at 180°. Prior to this phase angle, SCR1 remains off since its anode is negative with respect to its cathode. As soon as the phase angle passes 180°, SCR1 conducts current into the gate of the triac Q1. The current through SCR1 is limited to the minimum turn-on current of Q1, as it serves as a shunt around SCR1.

So, the triac is on from 180° to 360°, when the current through it falls below its holding point. The slaving circuit consisting of D3, D4, C2, and R6 serves to store the peak voltage across the load on C2. This stored voltage provides the triac with gate current between 270° and 450°, insuring zero-cross firing at 360°.

In this way, the load will be ener-

gized for at least two half cycles when heat is required. If still more heat is needed, two more half cycles will follow to keep the load energized.

Construction. Since the circuit is fairly simple, either pc or perforated-board techniques can be used. In any event, the circuit should be mounted in a suitable enclosure, observing the safety practices that are necessary when dealing with line-powered equipment. Thermal sensor TDR1 should be mounted so that it samples the average temperature of the room, not that of any heat-generating com-

ponent in the circuit. For example, it could be mounted in one corner of the enclosure away from triac Q1, with numerous holes drilled around it for unimpeded air flow. Alternatively, it could be mounted in a small metal box a short distance away from the rest of the circuit, with short interconnecting leads between the two. Thermal paste could then be used to keep sensor and enclosure at the same temperature.

Calibration and Use. Potentiometer R4 acts as the thermostat's sensitivity control. Figure 2 shows how the thermostat's set point varies as R4 is rotated. This curve is valid when all components are at their "typical" values. Of course, solid-state and thin-film devices are subject to some variations. Figure 3 shows the worst-case recalibration required with a "non-typical" D5. Worst-case variations of the thermal sensor will affect the calibration curve as well, and the resulting recalibration is shown in Fig. 4. All thermostats can be calibrated to within 2° C of Fig. 2 by trimming R3 and R8.

You will most probably want to make a calibrated dial for adjusting R4 to the desired room temperature. This is best done empirically. Thermally couple a good-quality thermometer to R1 and adjust R4 until the neon indicator I1 flickers or glows. At that point current is flowing through the heating element (LOAD), and the temperature of the sensor can be read off the thermometer. For temperatures higher than the room temperature, R1 can be gently heated.

One final note—the triac specified for Q1 (HEP R1722) is rated at 10 amperes forward current. If your heating element draws more current, simply use a higher-power triac. Of course, adequate heat-sinking is necessary for any thyristor. ♦

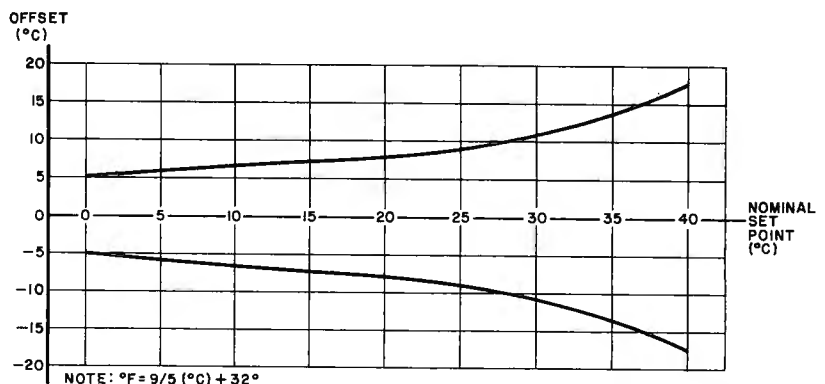


Fig. 4. Variations in R1 can be corrected using these curves.