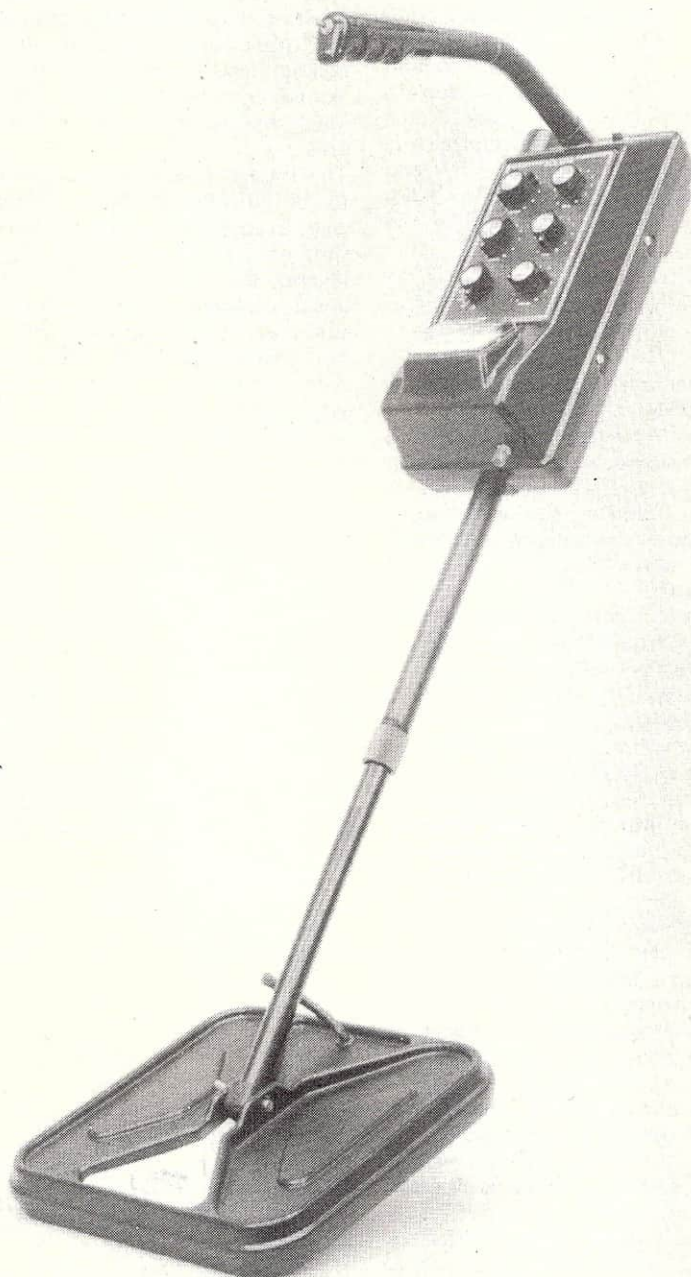


metal detector

high performance and simple construction

One of the problems that govern the fast growing hobby of treasure hunting is that economical metal detectors are notoriously unstable and suffer from a lack of sensitivity while the good ones are very expensive. The design featured in this article is both highly stable and sensitive and presents no problems in construction. It is professional in appearance and operation and performs better than many high-priced commercial detectors.



One of the projects near the top of the 'most requested projects' list has, some time, been a metal detector. The reason for the delay in publishing an article on the subject is due to the fact that construction of a good detector (and not one that just detects something) is a very difficult proposition. The very first major problem that the search head is that of stability since this is dependent on a number of aspects. To achieve a stable circuit design is not easy when cost is taken into consideration. The design and construction of the search head is also a formidable obstruction to obtaining a high performance while still remaining within the capabilities of the average enthusiast. Furthermore, the search head must be robust and remain stable after the very critical setting-up procedure it requires. In other words, it must not be prone to 'headaches' when knocked. Even the difficulties of waterproofing and resistance to temperature changes are problems enough in themselves if others are not enough.


What of the circuit itself? There are, of course, a number of methods by which metals can be detected with the use of electronics but stability is the governing factor in performance. It is possible to design a circuit using microprocessors and the like that will work wonders but will require a find of gold sovereigns every day for a week to cover its cost. Overall, the difficulties will appear now to be unsurmountable and you may well be asking how we managed to do it at all. It took a little time but, reassured, it has been done and the results have been well worth waiting for. The Elektor metal detector performs very well and is easy to construct due to the fact that the ultimate horror — the search head — does not have to be constructed by the reader. A complete hardware assembly, including the head, is available to readers, ready-made. How has it all been done? Before reading on to find out, a note of warning. Firstly, reading the article carefully and paying attention to details during construction are essential to produce a high performance metal detector. Secondly, and not quite so obvious, treasure hunting with a metal detector is much like horse riding; it takes time and practice to become proficient at it. Don't expect it to happen in one day!

Surveying the field

Various methods are used in the design of metal detectors and they all have their various advantages and disadvantages.

BFO — beat frequency oscillator

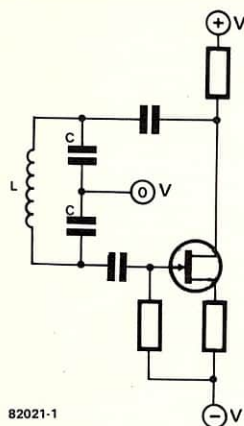These units are cheap, easy to build, but suffer due to the high frequencies used (for economic reasons). They are very sensitive to metals, suffering badly from instability and ground effect as they do not discriminate between different



82021-1

Figure 1. A simplified diagram of a conventional oscillator circuit. No form compensation is included to allow changes in the value of capacitor C to temperature variations.

materials. They work on the heterodyne principle of beating two frequencies together and obtaining an audio tone relative to the difference between the two signals. The basic trick is that the oscillator has the search head as its frequency determining component. Inducing a metal object into its vicinity will increase or decrease the search frequency so producing a change in audio tone.

B — transmit-receive/induction-balance

These metal detectors are much better than BFO types as regards general sensitivity but still suffer from stability problems and do not discriminate between metals. This type requires very accurate relative positioning of the coils which can be extremely difficult to set up. Another disadvantage is the fact that a 'knock on the head' can cause false signals.

— very low frequency


The most expensive metal detectors are usually of this type. Various circuits (a) make the unit sensitive to all metals, (b) discriminate between metals, (c) provide ground effect control overcoming a lot of shortcomings present in cheaper detectors. However, due to the low frequencies used, these still suffer from instability. The disadvantages are cost (which can be high) and difficulty in setting up the assembly.

pulse induction

Pulse induction is used in professional industrial metal detecting systems. Good design can be extremely costly and construction and calibration is beyond the realms of the average electronics enthusiast.

The Elektor metal detector to be described is a high performance VLF metal utilising phase locked loop techniques for stability, good discrimination between metals and elimination of ground effect. It features a better

2

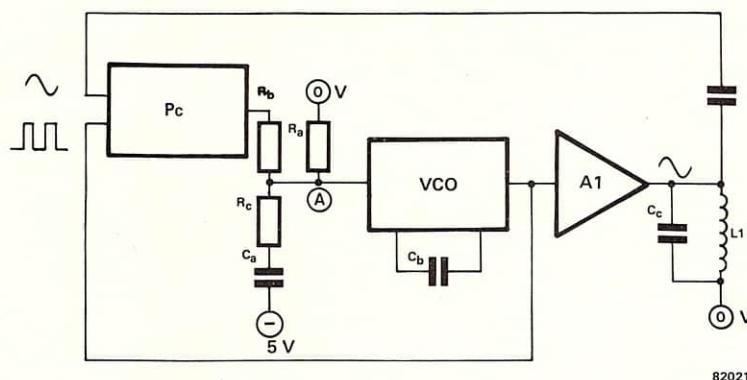

82021-2

Figure 2. The Elektor metal detector employs a phase locked loop design to provide the basis of a highly stable oscillator with immunity to drift.

detection range than BFO and TR/IB types and does not suffer from instability problems. To achieve all this 'icing on the cake' it will be obvious that the circuit must therefore be more complex. However, a glance at the circuit diagram in figure 4 will show that it is not as complicated as some readers may have expected, and furthermore calibration is extremely simple.

Instability and PLL

As previously mentioned the major disadvantage of cheaper metal detectors is that of instability. In cases of severe instability, the process of detecting metal can be hampered to the degree that it becomes impossible to differentiate between the detector itself being 'off tune' and a 'find'.

Why is the Elektor VLF circuit more stable than others? The simplified circuit diagram in figure 1 is that of the more conventional VLF design. The problem is that the low frequencies used with a VLF design require a large number of turns in the search head coil. This also necessitates that the value of C in the circuit is relatively large. This is the point in the circuit where instability will occur since any capacitor will change value when exposed to heat. If it happens that the capacitor is included in the tuned circuit of an oscillator, it follows that the oscillator frequency will therefore be prone to drift.

In this type of oscillator the drift cannot be compensated for and the problem is further aggravated by the susceptibility of the circuit to voltage fluctuations in the power supply (creating more instability). As if this were not bad enough, the oscillator has a fairly high current-consumption and therefore batteries have a very short life.

To overcome these shortcomings the Elektor phase locked loop design was developed. This effectively compensates for any drift in the oscillator frequency due to changes in the value

of the capacitor. This design is slightly more complex but with the help of figure 2 is fairly easily understood.

The centre frequency of the VCO (Voltage Controlled Oscillator) is initially set by R_a , R_b , R_c and C_a , C_b . This produces a square wave, which is converted into a sine wave by the amplifier A1 and is fed to the search head L1. A proportion of this signal is capacitively coupled back to the input of the phase comparator PC, the output of which is passed to the control input of the VCO via the low pass filter consisting of R_c and C_a . The output of the VCO is also fed back to the other input of the phase comparator. These two feedback loops provide an immunity to drift and form the basis of this highly stable oscillator.

The Elektor metal detector

It has already been stated that the circuit of the metal detector is fairly complex. However, the diagram in figure 3 shows the details of the circuit in block form and it will be understood more easily if each block is treated separately, bearing in mind that each one refers to a section of the main circuit in figure 4.

Since the first block of the diagram, the PLL oscillator, has already been described, we can move on to the phase locked loop discriminator. A discriminator enables the user to reject unwanted materials, for example metal paper foil. This part of the circuit has again been designed with high stability in mind and for this reason a second PLL is used. The adjustment of the phase relationship between the transmit oscillator and the received signal, provides a method of sampling a proportion of the received signal. This provides the phase sensitive detector with its gate input.

The phase sensitive detector 'chops up' the input signal from the receive head and, after filtering, the DC voltage output is used by the meter and audio

circuits.

The auto tune is another special feature of the Elektor metal detector. Briefly the principle is to achieve an offset voltage, by storing it in a capacitor across an FET opamp which is used as a slow/fast integrator. By feeding this voltage level back to the phase sensitive detector we can reset the output voltage of the PSD, in order to zero the meter at the flick of a switch. This means that manual retuning is not necessary when changing modes or altering the sensitivity of the detector.

The meter circuit is straightforward and incorporates a battery status check, as well as indicating the accepted and rejected finds.

The final section of the block diagram is the audio stage, but this does not consist solely of an ordinary amplifier. A gated chopper circuit is also included which takes the search oscillator frequency and divides it down to approximately 270 Hz. This is used to chop the DC voltage output of the PSD before feeding it to the audio output amplifier thus providing an audio tone when metal is received.

This covers the basic building blocks of the metal detector and we can now move on to discuss the finer points of the circuit in detail.

The circuit diagram

The PLL oscillator is formed around IC1 in the circuit diagram shown in figure 4. The frequency is set by the components C3, R12, L1 (the search head), C2 and R10. The value of R10 is chosen to set the VCO initially at mid frequency. The square wave output of the VCO (pin 4) is coupled via R7 to the search amplifier which is formed by transistors T1...T4. A portion of the sine wave is fed back via C1 and R11 to the signal input of the phase comparator (pin 14) where it is compared to the signal at pins 3 and 4. The resultant output at pin 2 is used to adjust the VCO to its resonant frequency thus forming a stable oscillator.

The VCO output at pin 4 of IC1 is also fed to the input of the phase locked loop discriminator IC2. The configuration of this IC provides a convenient method of adjusting the phase relationship by simply changing the value of a resistor at pin 11. The actual 'resistor' value is selected by S1, P4 and P5 and the resistor networks connected to pin 11 of ES5 and pin 8 of ES6. The level at pin 11 of IC2 selects either ground effect or reject mode with the aid of the CMOS switches ES5 and ES6. The phase shifted square wave output of the discriminator IC2 is the gate signal for the phase sensitive detector formed by IC4 and A2. The receive signal from the search head is passed through an impedance converter T12 and then amplified (by a factor of 50) by the opamp A1 before being passed to the phase sensitive detector. It is this signal

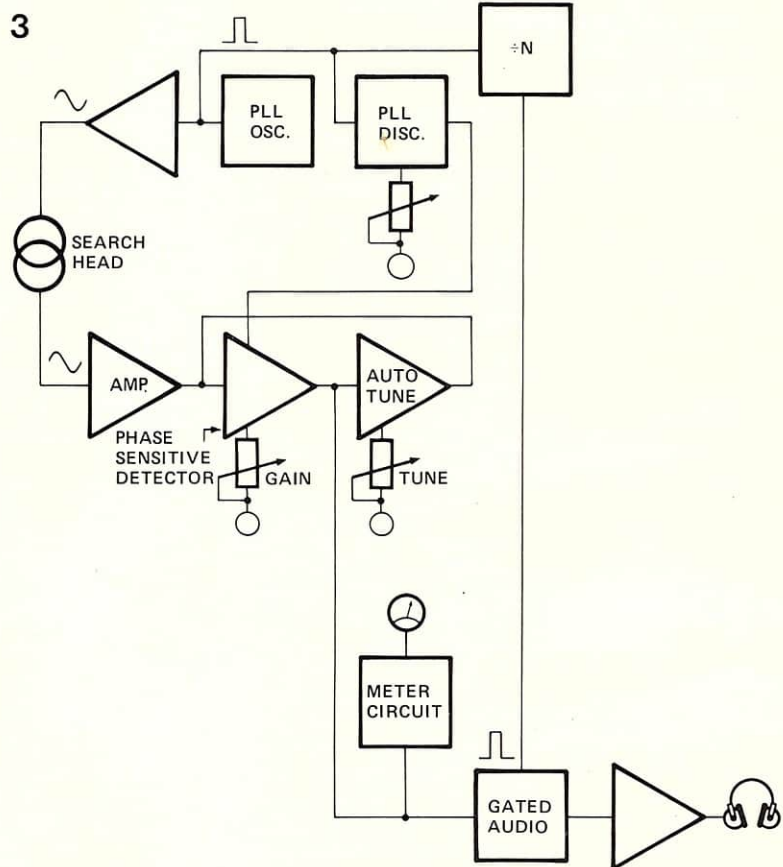


Figure 3. The block diagram of the Elektor metal detector. Each block corresponds to a part of the circuit diagram in figure 4.

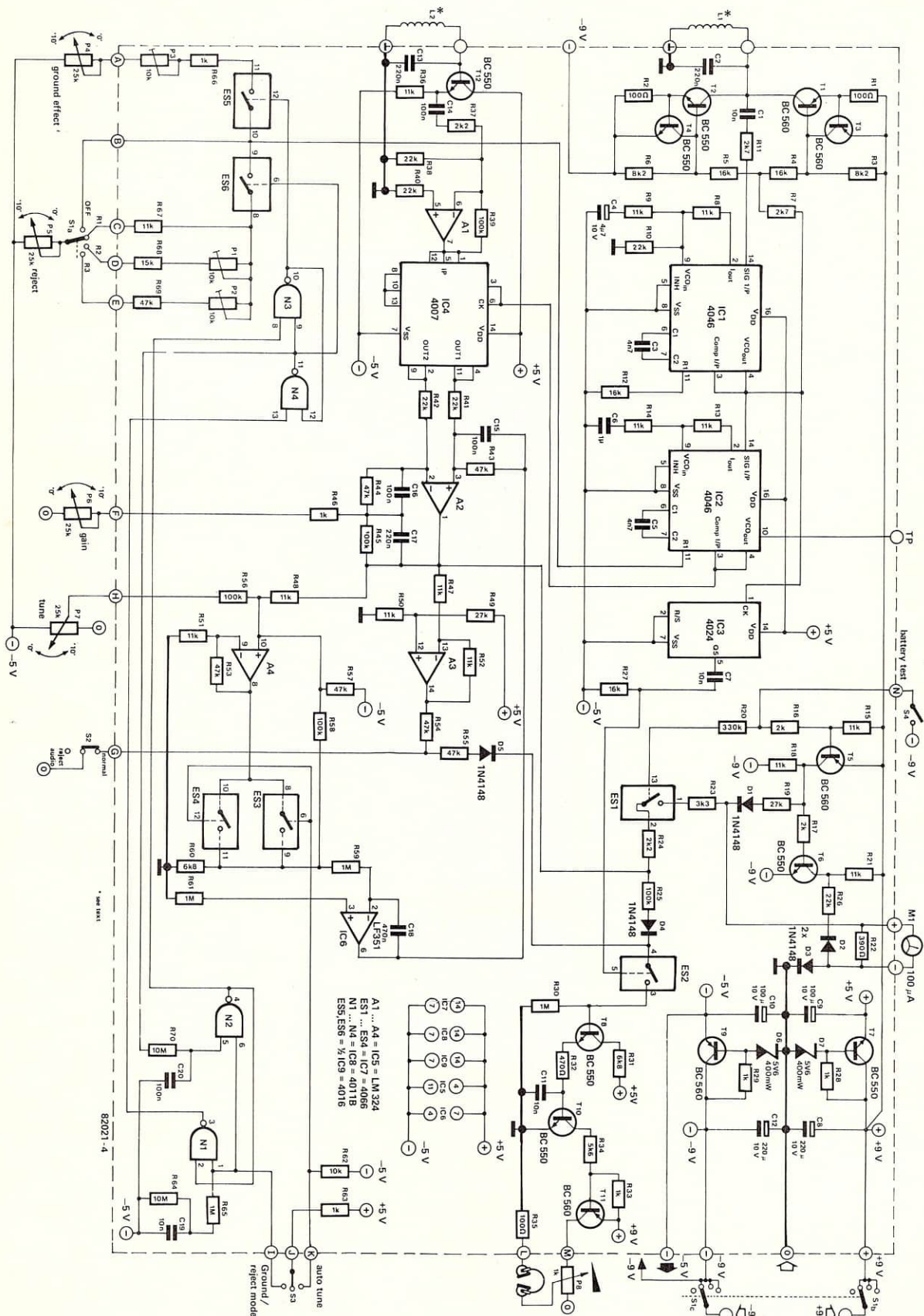


Photo 1. The handle and case assembly of the metal detector showing the high standard of the finished project.

that is then chopped and sampled by IC4 and converted to a DC voltage level by opamp A2. The gain of this stage is variable by means of potentiometer P7. The output of A2 is a voltage level that varies in relation to the size and content of any metal object in the proximity of the search head. This signal is provided with a variable offset by the tune control P7 in order to allow the meter to be zeroed.

Manual tuning can become tedious and is required after every change of mode and therefore an auto tune is a desirable feature of the circuit. This is carried out by storing a voltage level in C18. This voltage is the sum or difference of the output of A2 and the position of the tune control. A4 together with IC6 forms the basis of the auto tune circuit with the following functions. When the CMOS switches S3 and S4 close, the output of A4, an opamp with a gain of 4, will be fed directly to the input of IC6 and cause this opamp to act as a fast integrator. Since its output is fed back to the non-inverting input of the original voltage level on the output of this opamp will be restored. Auto tune is brought into operation by flicking the handle switch S3 momentarily. This action will turn on CMOS switches ES3 and ES4 thus increasing the voltage level on pin 2 of IC6 by a factor of 4.

S3 also serves as the mode change switch when operated in the other



ure 4. The complete circuit diagram for the metal detector. This drawing can also be used for wiring information for the tches and potentiometers.

direction, changing from ground effect to reject mode or vice versa. It will be apparent then that S3 is effectively a three-way switch. Mode change is achieved by the gates N1...N4 which are configured as a flipflop (although they may not appear to be so in the circuit diagram!). The complementary outputs of the flipflop control the two CMOS switches ES5 and ES6.

Many readers may find the going a little tedious by now, but take heart: we are almost at the end, in fact only the meter and audio sections of the circuit are left. The two functions of the meter are selected by the CMOS switch ES1. This is 'normally closed' and the meter will be connected to the detector circuit. Pressing the battery check switch S4 will open ES1 and at the same time, cause T5 and T6 to conduct. The meter will now be connected across the batteries via R19/D1 and R26/D2.

The remaining part of the circuit is the audio stage. It is slightly unusual but fairly straightforward. The output from the PLL oscillator (IC1) is fed to IC3 where it is divided by 32 to produce a 270 Hz square wave. This is then 'sharpened' by C7 and R27 to provide a control pulse for the CMOS switch ES2. In the normal modes an audio signal will only be heard when the meter moves to the right, indicating the presence of a wanted 'find'. This is when a rising positive voltage appears at the output of A2 and is fed via R25 and D4, through the CMOS switch to the output stage via T8.

It is also possible to use an audible signal for rejected finds. This may not be obvious at first but after some experience with the metal detector this feature will be found to be a useful extra. When S2 is switched off, the output of A3 is allowed to pass, via R55/D5 and again ES2, to the output stage. The audio amplifier consists of transistors T8, T10 and T11 with T10 acting as a level converter.

Construction

Readers will be in no doubt by now that the Elektor metal detector has a very professional appearance and in no way suffers from the usual nuts, volts and tobacco tin look that usually grace home construction projects of this type. The good news is that, yes, your metal detector can look exactly the same as that shown in the photograph here. Even more important, the major problem that prevents construction of a really good metal detector, that of winding and setting the coils in the search head, is completely taken care of. The entire case and hardware assembly, together with the potted, waterproofed and tested search head, has been made available to readers via Crestway Electronics Limited and it can be purchased with or without electronics. The overall design is to fully professional standards and the finished metal detector will out-

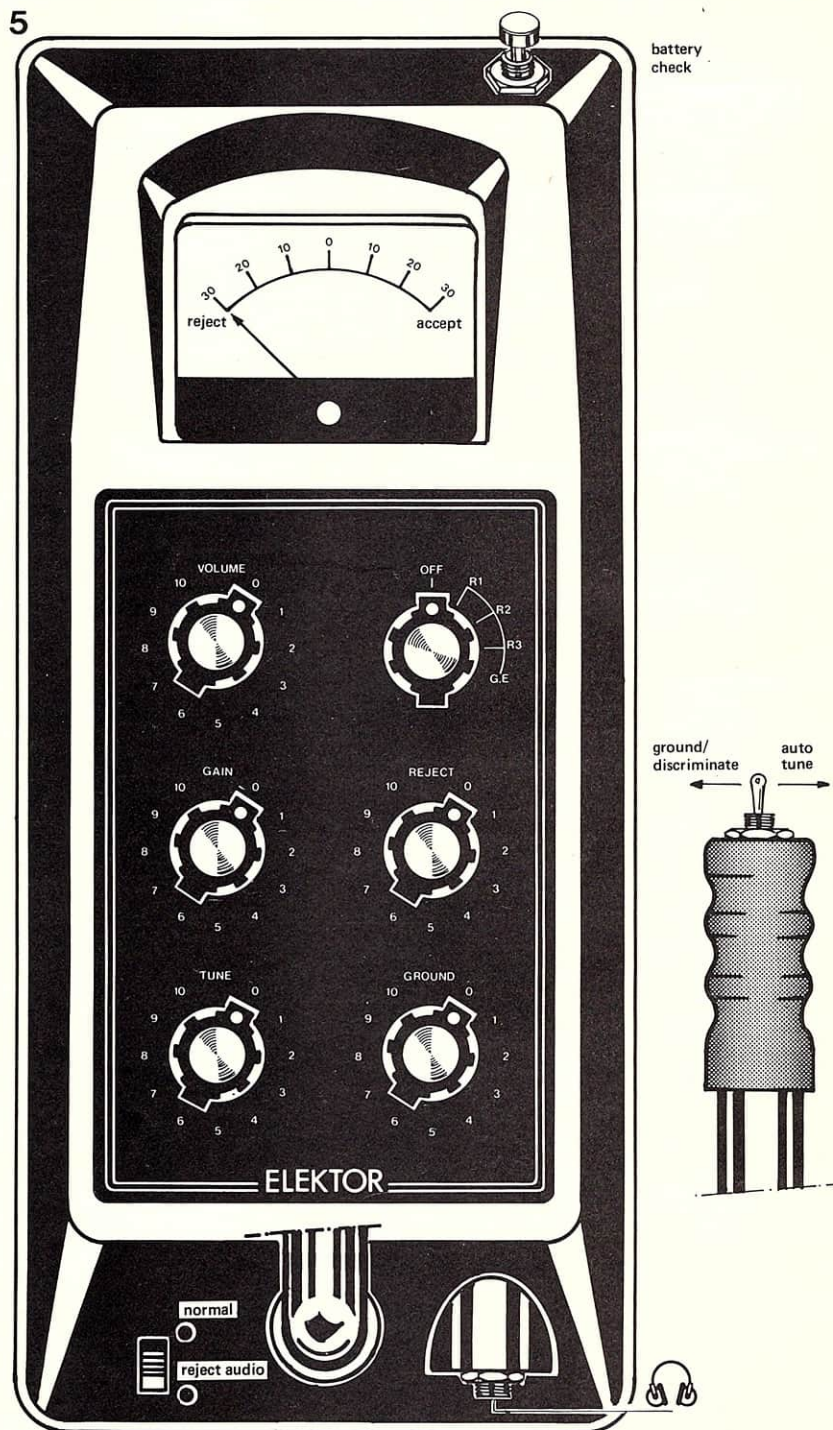


Figure 5. The front panel layout and controls for the metal detector. It is important that the switches and potentiometers are wired correctly. This diagram can be used with the operating instructions.

perform many high quality commercial units.

Should any reader wish to produce his own search head it is just possible although not very practical, since the setting of the coils is extremely critical and their position makes the difference between a very good detector and no detector. However, for those interested the head consists of two 10" coils with 80 turns each of 29 swg enamelled copper wire slightly flattened (to form a D) and overlapped by approximately 1". The critical setting is then found by

trial and error.

The electronics of the metal detector surprisingly easy to construct. In fact, the printed circuit board is used, it presents no problems at all. Assembly the board is carried out in the usual manner after which the point to point wiring is completed, using figure 4 as a guide.

Particular attention should be paid to the wiring of the potentiometers or the direction of the rotation may be incorrect. If one of them does appear to be the wrong way round, exchanging it

ring at each end of the track (the out-le tags) will provide a solution.

The handle switch S3 (ground effect/reject mode and auto tune) is a momentary two-way switch with a biased centre off position. This must be wired correctly to avoid confusion in use. The switch should be fitted so that auto tune is operated when the switch is flicked to the right. The contact that is made in this position (usually the left-hand one) should be the one connected to K on the printed circuit board.

Note on the printed circuit board, there are two points marked —9, these have to be wired together externally. If stereo headphones are used they should be converted to mono by shorting the left and right leads together (not the common lead).

It will be wise to ensure that all connections are correct before connecting the batteries.

Calibration

Any electronic device will only be as good as its calibration and for this reason the setting of the three preset potentiometers P1, P2 and P3 should be carried out with care. Some readers tend to get a little alarmed at this point but I can dispel any worries right away. The metal detector has been specifically designed to allow the calibration to be carried out — with nothing more sophisticated than an ordinary multimeter with reasonably accurate 1 V and 10 V ranges.

Initially all controls must be turned fully clockwise. The unit can now be switched on by turning S1 to the R2 position. The first check is the positive supply rail and this is carried out by connecting the meter (switched to V DC) across C9 — taking note of the polarity. The reading should be between 7 V and 5.3 V. The negative supply can be checked across C10, again with attention to polarity, and in this case a reading between —4.7 V and —5.3 V will be fine. If either reading is outside these limits the components in the supply regulators must be checked before going on.

If the supply voltages are correct the meter can now be connected between the test point (TP, pin 10 of IC2) and V (negative lead). With the meter switched to the 1 V range adjust P1 for a reading of 0.55 V. Switch S1 to the R3 position and adjust P2 for a reading of 0.15 V. After flicking the handle switch to select ground effect mode, P3 can be adjusted for a reading of 0.82 V. And that's all — the calibration has been completed!

Operating instructions

1. Switch S1 to the R3 position.
2. Press handle switch S3 to right and hold.
3. Rotate tune control until meter reads zero.
4. Rotate gain control to position 8.
5. Release handle switch.

2



Photo 2. Possibly the most important part of the metal detector, the search head, is supplied as a complete and finished assembly.

6. Adjust volume control to 1/2 way position.
7. Using a gentle sweeping motion sweep the ground in front of you with a left-right-left movement while walking slowly forward. The maximum sweep should be about 18".
8. Practice for a while using this procedure and try to receive signals from all types of metal. Once you are confident in the use of the basic procedures of the machine then move on to the following: using steps 1-6 set up the machine in basic operation mode and carry on with the following steps.
9. Flick handle switch to the left and release.
10. Rotate the reject mode control and check that the mode is correctly selected by a swing on the meter, if not return to step 9 and repeat.
11. Switch S1 to the R2 position and set the reject mode control to 1/2 way.
12. Flick the handle switch to the right (auto tune) momentarily and release.
13. At this point you should be rejecting tinfoil silver paper etc. but accepting coins (cupronickel) bronze, brass, silver and hopefully gold.
14. Rotation of the reject control towards zero will decrease the amount

of rejection, and towards 10 will increase rejection.

15. Practice using the above until you are familiar with the machine, then try the following.

16. The coarse settings of positions R1, R2, R3 on S1 works as follows:

R1 will give the maximum rejection of metals:

R2 will give average rejection and is the most used position.

R3 will give a minimum metal rejection, in other words, receives most metals.

17. Ground effect control

On some soil the so-called ground effect may be experienced, due to mineralised soil. The same effect will appear when using the detector on beaches. This phenomenon produces the effect of an almost continual and apparently haphazard series of finds. The indication of ground effect can be verified by a drop in audio output when lifting the search head away from the ground. It must be noted that ground effect is a phenomenon that all metal detectors have to overcome. The Elektor metal detector is able to eliminate this problem when the procedure described here is followed:

18. Depress handle switch to the left momentarily and release.
19. Rotate the ground effect control whereupon the meter should move.
20. Adjusting this control from zero to 10 will increase or decrease the compensation for ground effect and the best setting is when you can lift the head away from the ground, with no change of signal.
21. **Gain control**, this control sets the sensitivity of the machine and is normally turned up towards position 10 for most of the time. However, if a beach is being searched for coins, which will usually be just on the surface, then turning the gain down will make the detector sensitive to coins on or just below the surface and anything buried deeper will be ignored.

22. Auto tune switch

At any time in use, if changing mode or resetting of the gain, reject and ground controls, then momentarily operation the handle switch to the right will reset the tune position back to zero

3

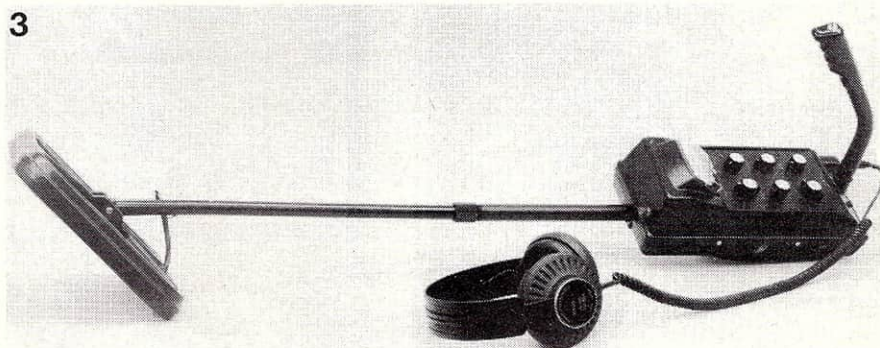


Photo 3. The distance between the head and the handle is fully adjustable.

Parts list

6

Resistors:

R1,R2,R35 = 100 Ω
 R3,R6 = 8k2
 R4,R5,R12,R27 = 16 k
 R7,R11 = 2k7
 R8,R9,R13 ... R15,R18,R21,R36,R47,
 R48,R50 ... R52,R67 = 11 k
 R10,R26,R38,R40 ... R42 = 22 k
 R16,R17 = 2 k
 R19,R49 = 27 k
 R20 = 330 k
 R22 = 390 Ω
 R23 = 3k3
 R24,R37 = 2k2
 R25,R39,R45,R56,R58 = 100 k
 R28,R29,R33,R46,R63,R66 = 1 k
 R30,R59,R61,R65 = 1 M
 R31,R60 = 6k8
 R32 = 470 Ω
 R34 = 5k6
 R43,R44,R53 ... R55,R57,R69 = 47 k
 R62 = 10 k
 R64,R70 = 10 M
 R68 = 15 k
 P1 ... P3 = 10 k preset potentiometer
 P4 ... P7 = 25 k lin. potentiometer
 P8 = 1 k lin. potentiometer

Capacitors:

C1,C7,C11,C19 = 10 n MKM
 C2,C13,C17 = 220 n MKM
 C3,C5 = 4n7 ceramic
 C4 = 4 μ 7/10 V
 C6 = 1 μ MKM
 C8,C12 = 220 μ /10 V
 C9,C10 = 100 μ /10 V
 C14 ... C16,C20 = 100 n MKM
 C18 = 470 n MKM

Semiconductors:

D1 ... D5 = 1N4148, 1N914
 D6,D7 = 5V6 400 mW zener diode
 T1,T3,T5,T9,T11 = 2N4126, BC 560
 T2,T4,T6,T7,T8,T10,T12 = 2N4124, BC 550
 IC1,IC2 = 4046
 IC3 = 4024
 IC4 = 4007
 IC5 = LM 324
 IC6 = LF 351, 3140, or equ.
 IC7 = 4066
 IC8 = 4011 B
 IC9 = 4016

Miscellaneous:

S1 = three-pole four-way switch
 S3 = SPDT biased centre off switch
 S4 = single pole push to make switch
 S2 = SPST slide switch } included in complete
 L1,L2 = search head } casework kit from
 M1 = 100 μ A meter } Crestway Electronics Ltd.
 headphones = 8 Ω
 batteries = 2 x PP6

A complete kit of parts including all metal
 work is available from
 Crestway Electronics Limited.


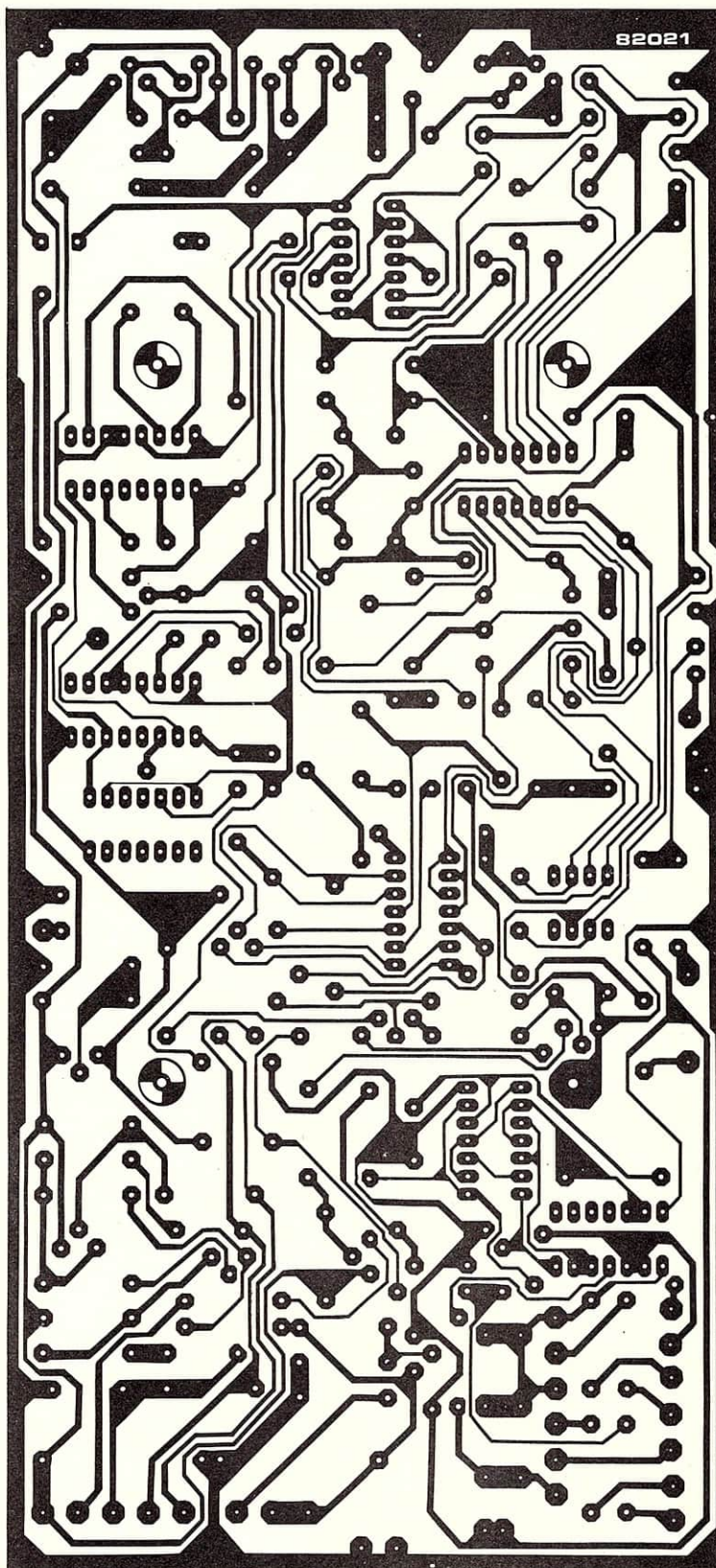



Figure 6. The printed circuit board and components layout for the metal detector.
 The two points marked —9 are wired together externally.

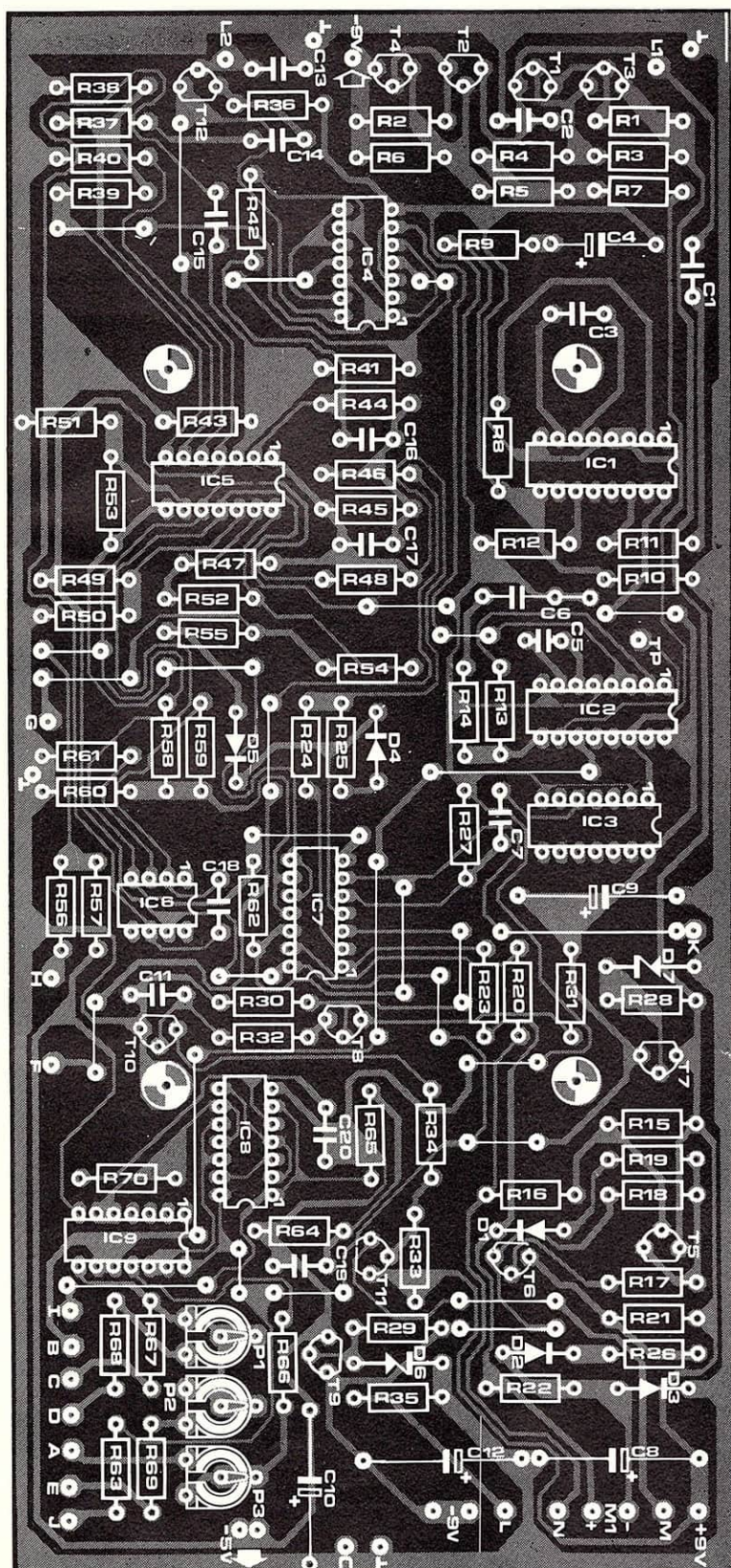

on the meter, but note: do not hold this switch over while actually searching for metal as the fast integrator circuit will be constantly in use.

23. The slide switch S2, at the left hand rear of the case, is normally in the nearest position to the front panel. This corresponds to an audible indication when the meter moves towards the right. If the switch is in the other position then an audio signal will be present at all times whether the meter is moving towards the right or the left, but a change in tone will be heard as metal is detected. This mode is useful for general searching, since you do not need to look at the meter all of the time.

24. Battery test button

Pushing this will give a meter reading indicating the state of the batteries. The batteries should be replaced when the meter reading falls below 10 on the right hand half of the scale. 

Notes for treasure hunters

Successful treasure hunting with any metal detector requires plenty of luck and experience. We are of the opinion that the former is somewhat unreliable but the latter can be gained with practice. After a period of use and time in which to become familiar with the metal detector, you will get to know little tricks like telling the difference between ferrous and non-ferrous materials from indications given by the detector alone. Steel is indicated by a more rapid movement of the meter. It is not really understood why, but bronze tends to give a warbling note in the headphones. Small coins and rings lying on edge in the ground will produce a very sharp on/off signal. It is also useful to know that the larger the size of a buried object, the more area the signal will be on for. We are also reliably informed that gold actually gives a double pulse in the form of an echo.

For consistent results, do not move too fast (neither sweeping nor walking) and keep the head within 1/2 to 1 inch above the ground. This becomes a lot easier with practise. After use always clean the search head with a damp cloth.

Above all, respect other people's property, and request permission before searching an area of land, it is almost always granted. The Elektor metal detector head is perfectly water-proof and can therefore be used in rivers which can prove quite fruitful.

We are given to understand that growing a beard and rising at unheard of hours does bring a measure of success but we have no documentary evidence to prove this. The seasoned treasure hunter can be recognised by this downcast, glazed expression and constant mumbling. His hand never leaves the shovel that travels everywhere at his side and he wears headphones in bed!

Treasure hunting can be rewarding, frustrating and damaging to your social life but it will never be boring.