

## APPLICATION NOTE 1831

## Low-Noise APD Bias Circuit

*Abstract: This circuit generates and controls a low-noise bias voltage for avalanche photodiodes (APDs) used in optical communications. The variable voltage controls the avalanche gain of the APD to optimize sensitivity in a fiber-optic receiver. The circuit employs a low-noise fixed-frequency PWM boost converter with an inductor operating in discontinuous-current mode. Slow switching of the internal MOSFET reduces high-frequency spikes for low-noise performance. A complete circuit is provided, and an extended circuit is suggested. The latter employs an ADC for digital control allowing a microcontroller to read a thermistor to provide temperature compensation by referring to a lookup table.*

Avalanche photodiodes (APDs) are used as receiving detectors in optical communications. The APD's high sensitivity and wide bandwidth make it popular with designers. APDs operate with a reverse voltage across the junction that enables the creation of electron-hole pairs in response to incident radiation. The electron-hole pairs are then swept by the applied field and converted to a current that is proportional to the radiation intensity.

Applying a variable reverse-bias voltage across the device junction creates a variable avalanche gain during APD operation. In turn, varying the avalanche gain optimizes sensitivity in the fiber-optic receiver. To achieve satisfactory levels of avalanche gain, however, many APDs require high reverse-bias voltages in the 40V to 60V range, and some require voltages as high as 80V.

A disadvantage of the APD is that avalanche gain depends on temperature and varies with the manufacturing process. Thus, for typical systems in which the APD must operate at constant gain, the high-voltage bias must vary to compensate for the effects of the temperature and manufacturing process on the avalanche gain. To achieve constant gain in a typical APD supply, the temperature coefficient must be maintained at approximately  $+0.2\%/^{\circ}\text{C}$ , which corresponds to  $100\text{mV}/^{\circ}\text{C}$ .

### APD Power Supply

Many methods exist for adjusting the output voltage of a power supply to compensate for temperature-induced gain variations of the APD. APD modules contain temperature-measuring devices such as thermistors, which can be connected directly to the power supply for output-voltage adjustment. In some systems, a microcontroller ( $\mu\text{C}$ ) reads the resistance value and then issues necessary bias-adjustment commands to the power supply.

The schematic of an APD bias power supply (**Figure 1**) is based on a low-noise, fixed-frequency PWM boost converter (U1) with an inductor that operates in discontinuous-current mode. Switching times have been intentionally slowed to reduce the high-frequency spikes that are otherwise present in most cases. Slower switching times reduce the high-frequency  $di/dt$  and  $dv/dt$  rates, which minimize radiated and coupled noise to surrounding circuits through current loops and capacitances between PC board traces or component pins.



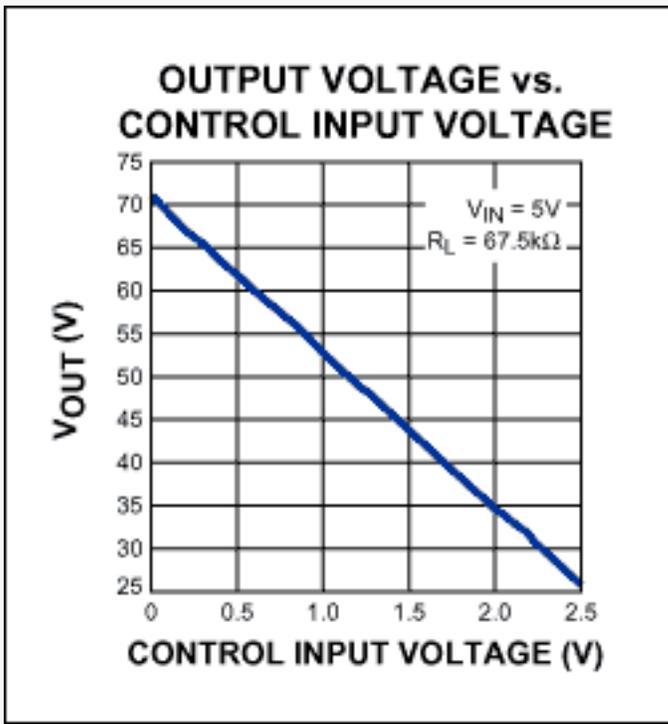


Figure 2. This graph demonstrates measured output voltage vs. control input voltage for Figure 1's circuit.

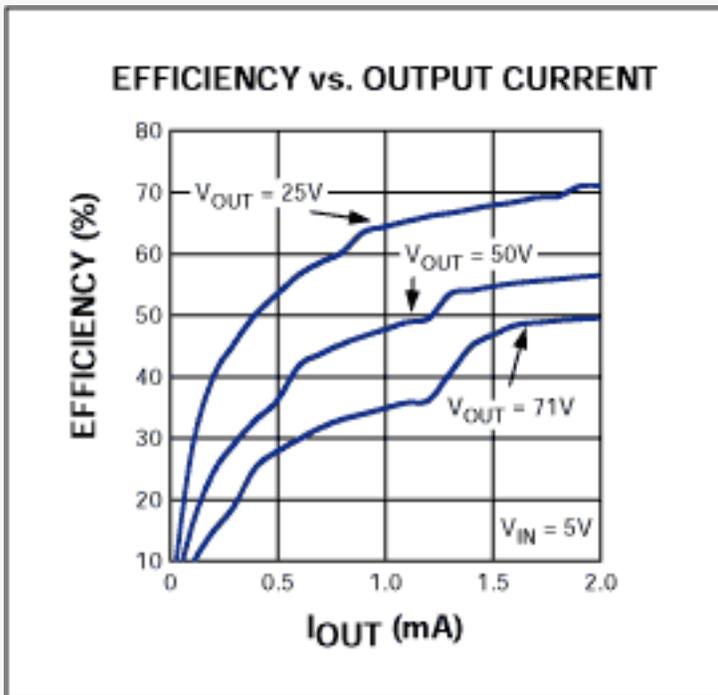


Figure 3. This graph shows the efficiency curves vs. output current of Figure 1's circuit.

Set the circuit's output voltage as follows:

$$V_{OUT} = [V_{REF} \times (R_2 \times R_3 + R_1 \times R_2 + R_1 \times R_3) - V_C \times R_2 \times R_3] / R_1 \times R_3$$

where V<sub>REF</sub> = 1.25V and V<sub>C</sub> is the control input voltage.

Figure 1's circuit has an output ripple of about 100mV<sub>P-P</sub> at 71V with a 1mA load current. That level can be improved to less than 20mV by placing a low-cost electrolytic capacitor (10μF, 100V Nichicon VX-series) in parallel with a 1μF ceramic capacitor (**Figure 4**). Additional filtering may be required to reduce the noise to lower levels. The typical noise level for an APD power supply is approximately 2mV. That level is easily achieved with a simple LC filter, given the MAX5026's fixed 500kHz switching frequency.

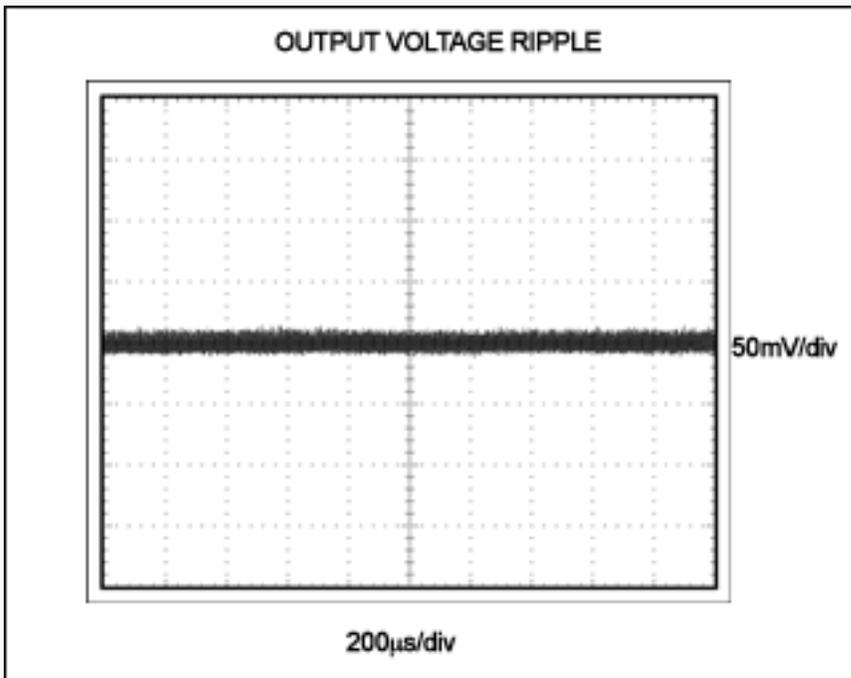


Figure 4. This graph demonstrates the output voltage ripple for Figure 1's circuit with  $V_{OUT} = 71V$ ,  $I_{OUT} = 1mA$ , and a  $10\mu F$  electrolytic capacitor in parallel with the  $1\mu F$  output capacitor. The vertical axis is  $50mV/div$  and the horizontal axis is  $200\mu s/div$ .

**Figure 5's** schematic is an APD power supply with digitally adjustable output voltage. A  $\mu C$  in the control loop reads the thermistor value, provides temperature compensation, corrects the thermistor curvature through lookup tables, and compensates for gain variations due to APD manufacturing. In this application circuit, the 10-bit DAC (U2) provides approximately 45mV resolution when varying the output voltage from 25V to 71V.

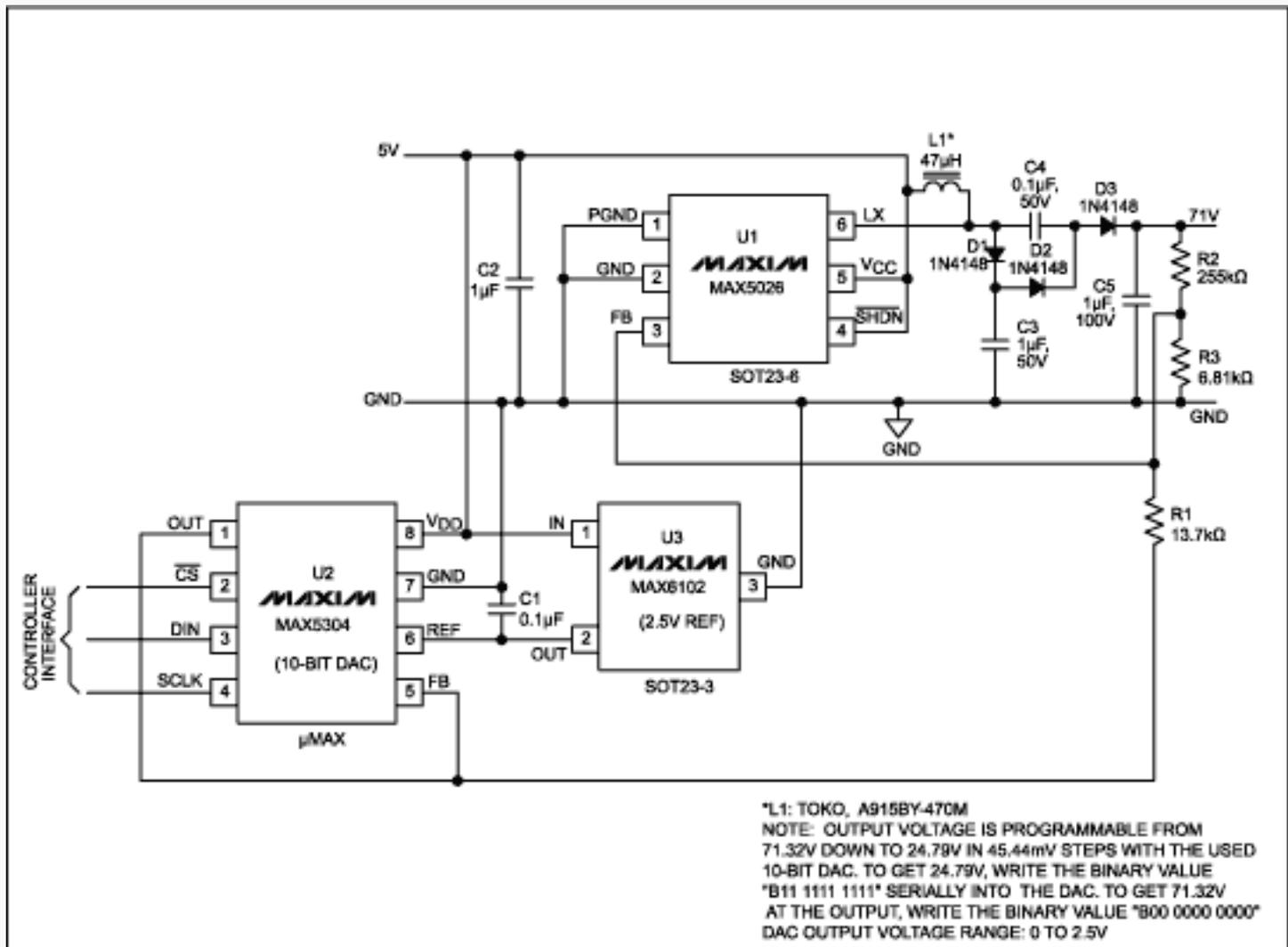


Figure 5. The output voltage in this low-noise APD bias power supply is digitally programmable from 25V to 71V in 45mV increments.

Application note 1831: [www.maxim-ic.com/an1831](http://www.maxim-ic.com/an1831)

### More Information

For technical support: [www.maxim-ic.com/support](http://www.maxim-ic.com/support)

For samples: [www.maxim-ic.com/samples](http://www.maxim-ic.com/samples)

Other questions and comments: [www.maxim-ic.com/contact](http://www.maxim-ic.com/contact)

### Automatic Updates

Would you like to be automatically notified when new application notes are published in your areas of interest?

[Sign up for EE-Mail™.](#)

### Related Parts

MAX5026: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

MAX5304: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)

MAX6102: [QuickView](#) -- [Full \(PDF\) Data Sheet](#) -- [Free Samples](#)



# Photodiode amplifier exhibits one-third the output noise of conventional transimpedance amp

Glen Brisebois, Linear Technology Corp, Milpitas, CA

➤ A conventional 1-M $\Omega$  transimpedance amplifier has at least 130 nV/ $\sqrt{\text{Hz}}$  of output-noise density at room temperature (Figure 1). You can consider the 130 nV as the theoretical noise floor limit of the amplifier because that is the noise density of the 1-M $\Omega$  resistor itself. Any noise in the op amp can only make things worse. Cooling the resistor to 77.2K, the temperature of liquid nitrogen, quiets it to 65 nV/ $\sqrt{\text{Hz}}$ , provided that it survives, but is that the only option? Can you beat the 130-nV theoretical noise floor without cooling?

Figure 2 shows one way. IC<sub>1</sub>, a Linear Technology (www.linear.com) LTC6240, provides an overall transimpedance gain of 1 M $\Omega$ , but it has an output-noise density of only 43 nV/ $\sqrt{\text{Hz}}$ , about one-third of a conventional 1-M $\Omega$  transimpedance amplifier at room temperature. It achieves this figure by taking an initial transimpedance gain of 10 M $\Omega$  and then attenuating by a factor of 10. The transistor section provides voltage gain and works on a 54V supply voltage to guarantee adequate output swing. By achieving an output swing of 50V before attenuation, the circuit maintains an output swing to 5V after attenuation. The 10-M $\Omega$  resistor sets the gain of the transimpedance-amplifier stage and has a noise density of 400 nV/ $\sqrt{\text{Hz}}$ . After attenuation, the amplifier's effective gain drops to 1 M $\Omega$ , and the noise floor drops to 40 nV/ $\sqrt{\text{Hz}}$ , which dominates the observed 43 nV/ $\sqrt{\text{Hz}}$ . To achieve this noise performance by cooling requires a temperature of 33K, much colder than liquid nitrogen. Note also that the additional benefit of this method is that it divides the offset voltage of the op amp by 10. The worst-case output offset for this circuit is 105  $\mu\text{V}$  over temperature. Bandwidth is 28 kHz. EDM

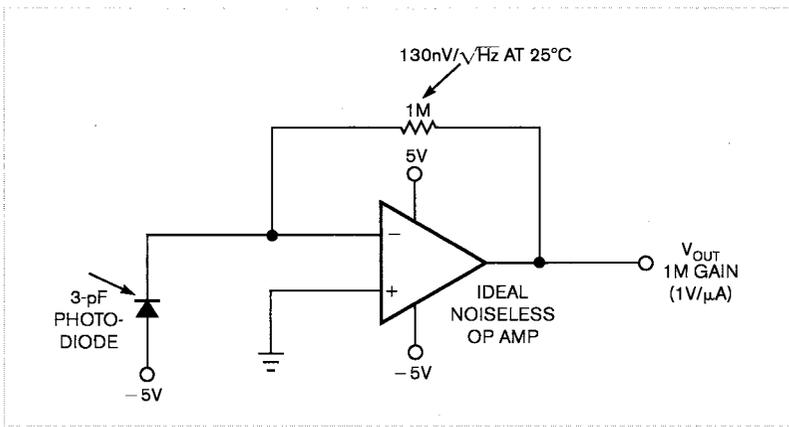


Figure 1 A conventional 1-M $\Omega$  transimpedance amplifier exhibits 130 nV/ $\sqrt{\text{Hz}}$  of output noise, even with a noiseless op amp. Cooling the resistor reduces the noise, but can you do better without cooling?

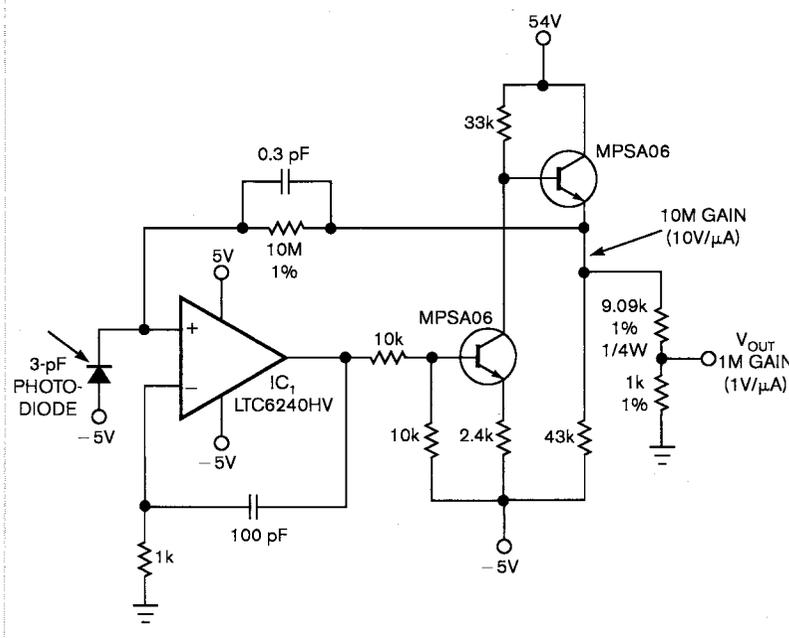


Figure 2 This effective 1-M $\Omega$  transimpedance amplifier has only 43 nV/ $\sqrt{\text{Hz}}$  of output noise. The circuit takes 10 times the high amplifier gain and then attenuates by a factor of 10. The LTC6240 has low current and voltage noise. The discrettes allow for high output swing at the 10-M $\Omega$  gain node, so that a 0 to 5V output swing remains after attenuation.