



then be connected and S1 opened.

In addition to the zener regulator, the main rail is further regulated by the action of comparator IC2a. This limits the pulse width so that the load cannot drag the main rail below 10V.

The third control circuit is based on IC2b and IC2c, and provides adjustable current limiting. Differential amplifier IC2b monitors the voltage across R10 and R11. When its output voltage at pin

7 exceeds the voltage preset by VR1, pin 8 of IC2c goes low and pulls pin 2 of IC1 low via D9.

In the absence of a control signal, the SG3525 (IC1) has its control pin (pin 2) pulled high via R4 so that it can provide the maximum pulse width to drive Q2 and Q1. Note that LEDs can be used in place of the diodes to give a status display. Note also that only one of the control circuits will pull pin 2 of IC1

low at any given time.

The supply to the main switching transistor (Q1) is prefiltered by L1 and C3 to prevent noise from affecting the control circuitry. Q1 dumps current into L2 which free wheels via D2 when Q1 is off. C4 provides filtering for the output. To ensure stability of the current loop (the primary control loop), the error amplifier (IC2c) is compensated by R14 and C8.