

Relay driver saves substantial power

TIM HERKLOTS, MAXIM INTEGRATED PRODUCTS, SOUTHAMPTON, UK

It is common practice to operate relays and solenoids at a reduced holding power once the mechanical actuation takes place. Relays are usually specified to pull in within 3 msec at 80% of the rated voltage and to release at 30% of the rated voltage. The circuit in **Figure 1** drives as many as eight 12V (120 Ω coil) power relays, which memory-map into an 8-bit μ P bus. An octal latch stores the relay status, where each bit of the 8-bit word serves a separate relay (0=off, 1=on). The latch's Select line latches data on the rising edge. Whenever the relay's status data changes, the relay's drive voltage rises to the full 12V for 140 msec to ensure that the relay pulls in. A series zener diode then reduces the relay's drive voltage by 50% to reduce dissipation.


A ULN2803, an octal Darlington array with base resistors for direct logic interface, drives the relays. A useful feature

is the inclusion of eight inductive-load clamping diodes, internally connected between the Outx pins and the Com pin. Com thus connects to the relay-supply rail. The power-saving timing comes from IC₁, a micropower MAX810 processor supervisor powered by the normally high Select line. When the system processor writes to the IC₂ latch, the supply to IC₁ toggles for 200 nsec, causing IC₁ to take its RST output high for 140 to 560 msec. Q₁ operates as a gated current source, dragging current from Q₂, thereby shorting out D₁, a 5.6V zener diode. Hence, the relays receive full bus power during the switching phase. After this period, Q₂ turns off, and D₁ drops the relay supply to the holding voltage. (DI #2217)

EDN

To Vote For This Design, Circle No. 520

FIGURE 1

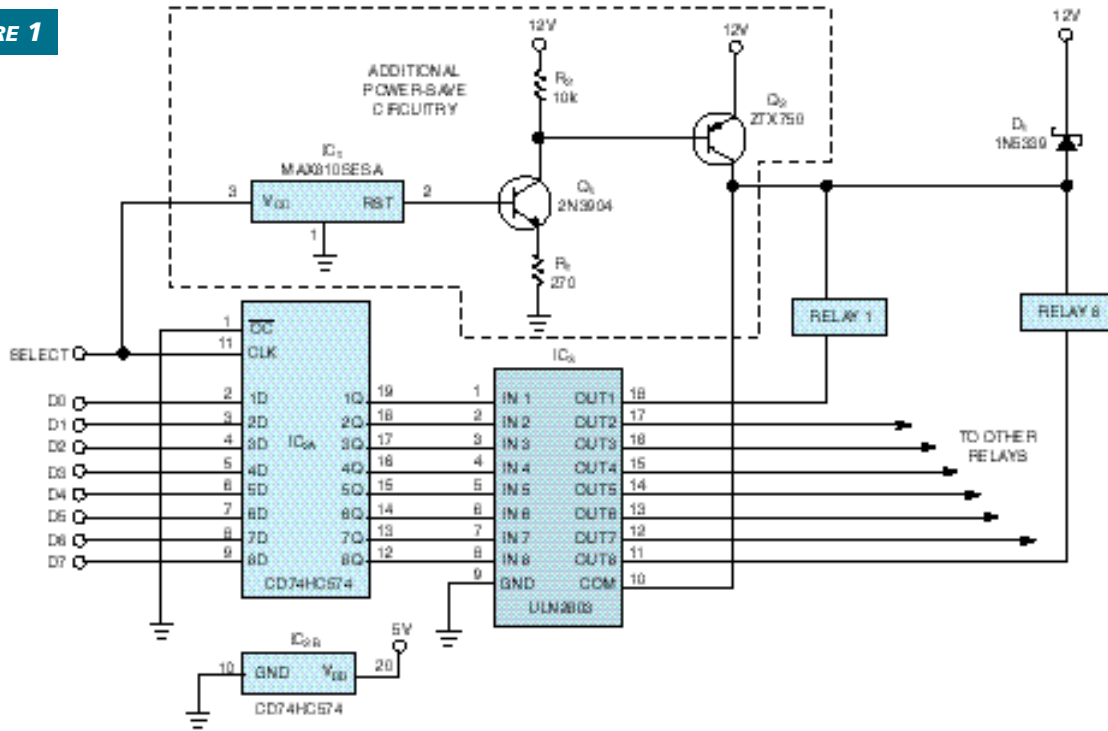

This power-saving circuit takes advantage of the large turn-on/turn-off hysteresis in electromechanical relays and solenoids.