


# Comparator directly controls power-MOSFET gate

Peter Demchenko, Vilnius, Lithuania




It is common practice to power a MOSFET with a comparator and with an unregulated voltage and to power the comparator driving it from a regulated one (**Figure 1**). Many loads are insensitive to driving voltage, so it would be a waste of money and power to use a regulated supply to drive the FET. It is also common practice to add resistors  $R_1$  and  $R_2$  to the comparator to put hysteresis in the operation, making the circuit less susceptible to noise, especially with slowly changing signals.


This circuit's comparator changes with changes in the unregulated power supply. You can correct this problem by adding diode  $D_2$  and resistor  $R_5$  to the circuit (**Figure 2**). This approach isolates the hysteresis circuit from the unregulated output and instead drives it from the same regulated supply that drives the comparator. When the comparator is on, it drives the FET just as the original circuit does, pulling the P-channel FET gate toward ground. In both cases, you connect zener diode  $D_1$  to the FET gate to avoid exceeding the gate-to-source voltage. The improvements in the circuit in **Figure 2** become

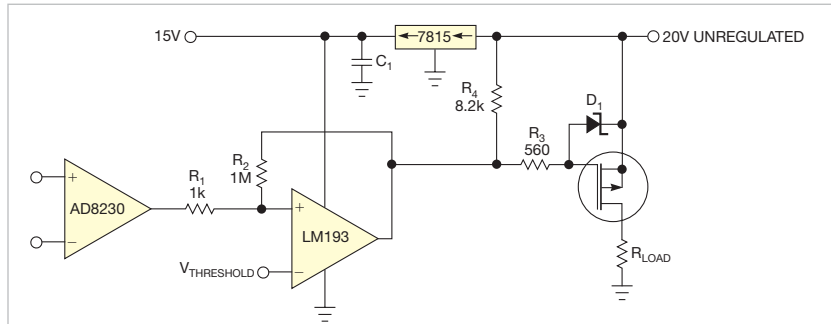

**Figure 1** Hysteresis components  $R_1$  and  $R_2$  tie to the unregulated supply, causing the comparator's switching point to vary with the power supply.

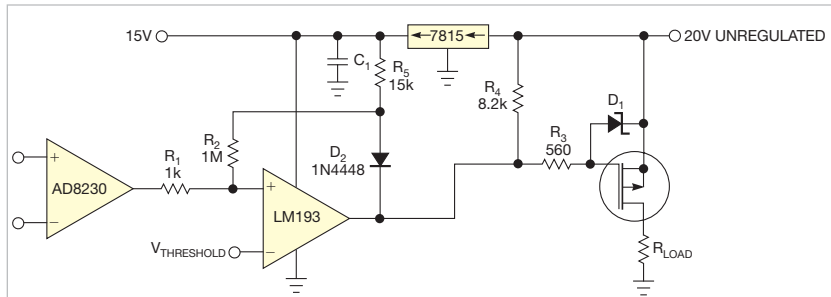

**Figure 2** Resistor  $R_5$  and an ORing diode isolate the hysteresis circuit from the power supply and keep the switching point constant no matter how the power supply changes.

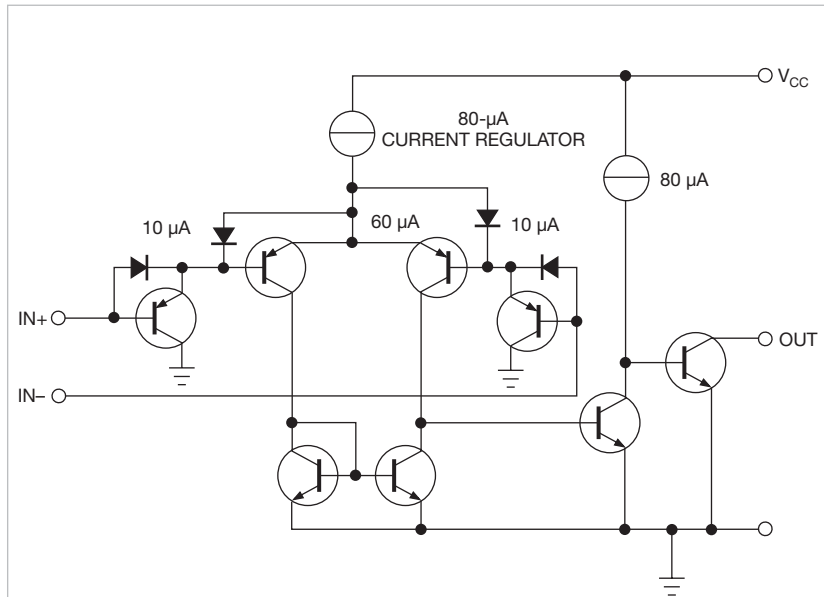

**Figure 3** The internal design of the LM193 comparator requires that you keep the input pins 2V below the positive rail (courtesy Texas Instruments).

apparent when the comparator turns off. In either case,  $R_4$  pulls the comparator's open-collector output up to the positive power supply. In **Figure 2**, however, the diode isolates the hysteresis circuit from the power supply so that  $R_4$  pulls up  $R_5$  to the regulated 15V, no matter how the power supply changes.

With a legacy comparator such as Texas Instruments' LM193, the common mode of the inputs must stay well below the power-supply rail (**Figure 3**). The circuit requires 1.5V head room at 25°C and 2V head room over temperature. Thus, for the circuits in **figures 1** and **2**, you cannot set the threshold voltage higher than 13V. If your circuit requires a threshold voltage closer to the power rail, consider using newer parts with rail-to-rail inputs. You must use an open-collector or open-drain comparator for this hysteresis-isolation circuit to work. It would be incompatible with a totem-pole-output IC. **EDN**