

# Capacitor-Powered Electronics Is At The Core Of Green Design

**The concept of using** supercapacitors (also known as ultracapacitors, supercaps, etc.), and replacing the batteries in portable micropower applications,<sup>1</sup> is gaining momentum. In fact, it has become one of the more noticeable technical trends of recent time.

Supercapacitors, such as the BOOSTCAP ultracapacitors from Maxwell Technologies ([www.maxwell.com](http://www.maxwell.com)) or DYNACAP from Elna ([www.elna-america.com](http://www.elna-america.com)), when used as a power source, hold tremendous advantages over traditional rechargeable batteries. For instance, they feature high endurance to short circuits, very short charging cycle, and practically unlimited charge-discharge cyclomatic durability (up to 1 million cycles compared to 1000 for batteries), thus providing an environmentally clean, “no-disposable-part” solution. In addition, most supercaps comply with the European Union’s Restrictions on Hazardous Substances (RoHS).


The fundamental difference between supercaps and batteries from a design prospective is the substantial voltage change during a capacitor’s charge/discharge cycles, which goes theoretically from zero to the maximum rated voltage, while a battery’s terminal voltage varies just a little during its operational cycle. Supercaps are the subset of electrical capacitors. Thus, the effective energy,  $E_{EFF}$ , that can be obtained from a supercap during its discharge cycle, when the terminal voltage changes from the maximum,  $V_{MAX}$ , to the minimal operating voltage,  $V_{MIN}$ , of the powered device could be calculated as:

$$E_{EFF} = 1/2 \times C \times (V_{MAX}^2 - V_{MIN}^2) \quad (1)$$

Correspondingly, the effective energy ratio (EER) could be defined as:

$$E_{EFF}/E_{MAX} = 1 - (V_{MIN}/V_{MAX})^2 \quad (2)$$

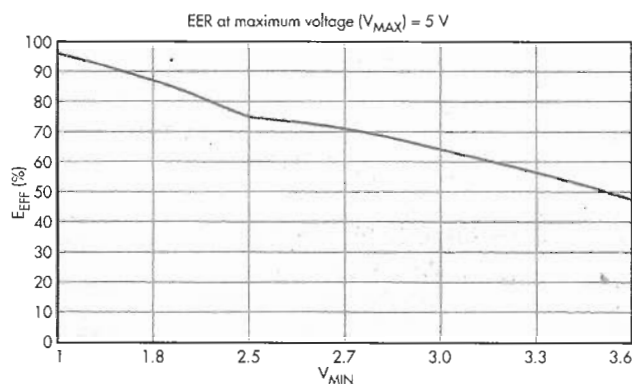where  $E_{MAX}$  stands for the total energy stored in the capacitor. Equation 2 clearly indicates that the effective energy ratio



1. The graph of capacitor effective energy ratio (EER) for  $V_{MAX} = 5\text{ V}$  shows a dramatic decrease as  $V_{MIN}$  increases from 1.0 V to 3.6 V.

increases dramatically as we lower the minimum operational voltage  $V_{MIN}$  of the powered electronic circuit due to the lower amount of residual electrical energy left in the capacitor. EER is a very important design consideration to be applied to any capacitor-powered electronic circuit.

The table and the corresponding graph in Figure 1 show a sample EER calculated for a capacitor-powered circuit with maximum terminal voltage  $V_{MAX} = 5\text{ V}$ . It’s quite noticeable that EER increases from 48% to 96% when the minimal operational voltage,  $V_{MIN}$ , of the powered electronic device changes from 3.6 V to 1 V. Therefore, “squeezing the device operating voltage” is the primary design consideration of capacitor-powered electronics.

The goal could be achieved by using an ultra-low-power dc-dc boost converter (e.g., the inductor-less type described in Reference 2, operating from as low as 0.7 V), but it could add to the design cost and energy consumption. The second alternative is to use a special design technique targeted at providing ultra-low-voltage device operation.

A good example of such low-voltage circuit design is described in Reference 3. The suggested micropower, ultra-low-voltage, full-wave, diode-less rectifier is an excellent fit for the design paradigm of capacitor-powered electronics (Fig. 2).

To understand the operational principle of the circuit, it’s important to notice that the op amp works in a single-supply mode. If a positive signal is applied to the input ( $V_{IN} > 0$ ), the op-amp output goes to zero and the whole circuit virtually transforms itself into a simple passive network of three resistors— $R_1$ ,  $R_2$ , and  $R_3$ —connected in series. When the input signal goes negative, the op amp returns to “normal linear life” and performs like a regular inverting amplifier. To produce the symmetrical output for both negative and positive half-waves,  $R_1$ ,  $R_2$ , and  $R_3$  must be selected to comply with the mathematical condition:

$$R_1 \times R_3 = R_2 \times (R_1 + R_2 + R_3) \quad (3)$$

As the condition of Equation 3 is fulfilled, the circuit has a gain of one-half at point 2 in the circuit. An optional non-inverting ampli-

EER For $V_{MAX} = 5\text{ V}$	
$V_{MIN}$ (V)	$E_{EFF}/E_{MAX}$
1.0	96%
1.8	87%
2.5	75%
2.7	71%
3.0	64%
3.3	56%
3.6	48%

ALEXANDER BELL, CEO, holds a PhD in electrical engineering from the Moscow Power Engineering Institute (now Technical University), Russia.


## IdeasForDesign

fier with a gain of two could be added to produce the overall unity gain, providing the operational equation of  $V_{OUT} = |V_{IN}|$ .

The circuit has certain limitations: its input resistance is different for the positive and negative half-waves. Theoretically, resistance is  $R1 + R2 + R3$  for the positive and just  $R1$  for the negative signals. Also, the input parasitic capacitance,  $C_p$ , of the op amp affects the ac mode operation, especially in the high-frequency range. (Detailed analysis of ac performance goes far beyond the scope of this article. I would recommend using Spice simulation for the practical design).

The circuit could employ a variety of rail-to-rail micropower op amps—for example, the dual LM6442 from National Semiconductor ( $V_{MIN} = 1.8\text{ V}$ ), the dual MAX 4289 from Maxim Integrated Products ( $V_{MIN} = 1.0\text{ V}$ ), or a similar type.

Since a typical silicon diode has a forward-voltage drop of about 0.6 V, output dynamic range is reduced to “consuming” that very 0.6 V from the supply voltage. This consideration has become rather important in the case of building capacitor-powered electronics, where the circuit supply voltage should go as low as possible. For this reason, the suggested diode-less design is a better fit when running in capacitor-powered mode. It saves the valuable 0.6 V (which is a rather significant value considering the possibility of an op amp

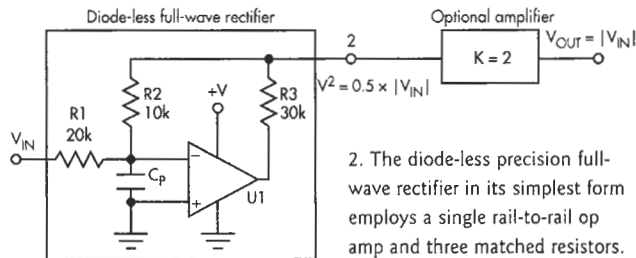

running at 1 V), and thus squeezes the minimum operating voltage of the circuit and increases the overall EER of the solution.

### References:

1. Bell, Alexander, "Single Capacitor Powers Audio Mixer," *EDN*, Mar. 14, 1997, [www.edn.com/archives/1997/031497/06DI\\_04.htm](http://www.edn.com/archives/1997/031497/06DI_04.htm).
2. Bell, Alexander, "Single NiCd Cells Drive Op Amp," *EDN*, Dec. 5, 1996; [www.edn.com/archives/1996/120596/25di\\_07.htm](http://www.edn.com/archives/1996/120596/25di_07.htm).
3. Bell, Alexander, "Simple Full-Wave Rectifier," *Electronic Design*, Apr. 4, 1994, p. 78.