

# Build a charge pump with ultralow quiescent current

Greg Sutterlin, Maxim Integrated Products, Sunnyvale, CA

**P**ORTABLE BATTERY-powered devices often spend most of their life in standby mode, in which the quiescent current of an internal boost converter continuously bleeds the battery. The quiescent current during standby can be larger than the actual load current. Though several inductor-based converters offer maximum quiescent current of less than 10  $\mu\text{A}$ , designers usually prefer or require a regulated charge pump for cost-sensitive designs that must be intrinsically safe. Off-the-shelf regulated charge pumps with output-current regulated capabilities of at least 10 mA have typical minimum quiescent currents of 50 to 100  $\mu\text{A}$ . If that level of quiescent current is unacceptable, you can reduce the overall average by adding circuitry that remotely monitors the regulated voltage and toggles the charge pump into and out of shutdown. That approach, however, may not achieve the desirable quiescent-current level of less than 10  $\mu\text{A}$ . The advent of low-on-resistance comparators and references makes possible a charge-pump circuit whose maximum quiescent current is approximately 7  $\mu\text{A}$  (Figure 1).

Charge pumps use an ac-coupling technique to transfer energy from a transfer capacitor to a storage capacitor. The transfer capacitor first charges via analog switches to the level of  $V_{\text{BATT}}$ , and then other analog switches transfer the

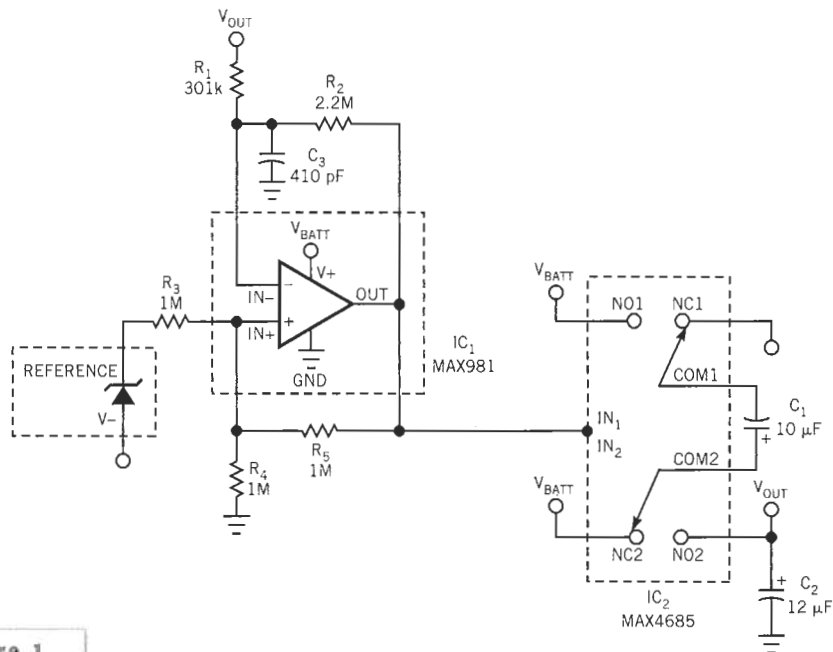


Figure 1

This charge-pump circuit uses analog switches to achieve ultralow quiescent current.

energy to a storage capacitor tied to  $V_{\text{OUT}}$ . The transfer capacitor then charges again, and the cycle repeats. With ideal analog switches exhibiting zero loss, the  $V_{\text{OUT}}$  level equals two times  $V_{\text{BATT}}$ . As expected, however, the analog switches' finite on-resistance produces an output level that drops in proportion to the load current. The basic regulated charge pump in Figure 1 includes an oscillator, several analog switches, a volt-

age reference, and a comparator. The comparator serves as a voltage monitor and an oscillator. When the circuit is in regulation, the comparator output is low, which closes the NC (normally closed) switches and allows  $C_1$  to charge to  $V_{\text{BATT}}$ . When the voltage at  $V_{\text{OUT}}$  dips below the output-regulation threshold—3.3V in this case—the comparator output goes high. The NO (normally open) switches close, transferring  $C_1$ 's

charge to  $C_2$ . This cycle repeats until  $V_{OUT}$  regains regulation.

Resistors  $R_3$  to  $R_5$  provide the hysteresis necessary for oscillation. Their value, 1 M $\Omega$ , creates a notable level of hysteresis and minimizes  $V_{BATT}$  loading. As the comparator output changes state, feedback resistor  $R_3$  creates hysteresis by moving the threshold you apply to the comparator's positive input. For the resistor values shown, reference value nominal for  $IC_1$  (1.182V), and  $V_{BATT}=3V$ , the  $V_{IN+}$  threshold swings between approximate values of  $V_{IN+}(low)=0.39V$  and  $V_{IN+}(high)=1.39V$ . When the circuit is in regulation,  $V_{IN-}$  slightly exceeds  $V_{IN+}$ , the comparator output is low, the  $R_1$ - $R_2$  divider senses the voltage at  $V_{OUT}$ , and the threshold at  $V_{IN+}$  is low (0.39V). With  $V_{IN+}$  at 0.39V, you can calculate the  $R_1$  and  $R_2$  values from the equation

$V_{IN+}=V_{OUT}[R_2/(R_1+R_2)]$ . The resistance of  $R_1+R_2$  should be greater than 1 M $\Omega$  to minimize  $V_{BATT}$  loading. If  $V_{OUT}=3.3V$  and  $R_2$  is 2.2 M $\Omega$ ,  $R_1$  calculates to 301 k $\Omega$ . Capacitor  $C_3$  connects to the comparator's  $V_{IN-}$  input. Along with  $R_1$  and  $R_2$ ,  $C_3$  sets the oscillation frequency according to the following simplified relationships:  $t_{DISCHARGE} = t_{LOW} = -(R_2C_3)\ln[(V_{IN+}(LOW))/(V_{IN+}(HIGH))]$ ;  $t_{CHARGE} = t_{HIGH} = -(R_2C_3)\ln[1 - (V_{IN+}(HIGH) - V_{IN+}(LOW))/(V_{BATT} - V_{IN+}(LOW))]$ ; and  $f_{OSC} = 1/t_{PERIOD}$ , where  $t_{PERIOD} = t_{LOW} + t_{HIGH}$ .

To maximize efficiency and reduce the effects of comparator slew rate, you should set a relatively low frequency. Choosing  $C_3=470$  pF yields the following:  $t_{LOW}=178$   $\mu$ sec, and  $t_{HIGH}=68$   $\mu$ sec; thus,  $f_{OSC}=4$  kHz.

Select the values of  $C_1$  and  $C_2$  to achieve the desired load current and rip-

ple. For this application ( $I_{LOAD}=10$  mA),  $C_1=10$   $\mu$ F. To calculate the value of  $C_2$ , make an approximation based on the desired ripple voltage:  $C_2=(I_{LOAD} \times t_{LOW})/V_{RIPPLE}$ . With  $I_{LOAD}=10$  mA and  $V_{RIPPLE}=150$  mV,  $C_2=12$   $\mu$ F.

With these component values, the circuit draws a maximum quiescent current of 6.9  $\mu$ A and offers a considerable improvement over off-the-shelf charge pumps. You can further lower the quiescent current by increasing the resistor values, but that effect is minimal because  $IC_2$ 's maximum quiescent current of 3.8  $\mu$ A dominates the total. This circuit lets you implement an ultralow-quiescent-current-regulated charge pump. Until off-the-shelf options are available, it provides an alternative for designers seeking to implement a low-cost design without the use of inductors. □

## A DESIGN CONTEST 400 YEARS IN THE MAKING. WHICH EXPLAINS THE \$10,000 FIRST PRIZE.

Empowered by Innovation

NEC



\*gift values are approximate

Centuries ago, Cornelius Van Drebbel was arguably the world's most prolific inventor. Today, unfortunately, nobody remembers his name. So we decided it was about time to hold a contest in his honor. Here's how it works: you design something cool using NEC Electronics 8-bit microcontrollers with integrated LCD drivers. If you plan to submit a hardware design, you're eligible to receive a design kit. Then when you submit a qualified design, you'll receive a gift valued at \$100.\* (e-Paper designs are eligible for a \$50 gift.\*) Our panel of judges will select the top three designs, which will win substantial cash prizes.

VAN DREBBEL INVENTED THE SUBMARINE IN 1620.  
IMAGINE WHAT HE'D DO WITH AN 8-BIT MCU.



OVER \$26,000 IN PRIZES. REGISTER AND GET A FREE DESIGN KIT.

[WWW.MADDESIGNCONTEST.COM](http://WWW.MADDESIGNCONTEST.COM)

CO-SPONSOR

EDN

©2004 NEC Electronics America, Inc.