


Simple two-transistor circuit lights LEDs

Barry A Tigner, Michigan State University, East Lansing, MI

 A previous Design Idea describes a circuit that uses an astable multivibrator to drive an LED (**Reference 1**). The circuit in **Figure 1** uses a simpler alternative approach. The circuit uses a 2N3904 NPN transistor and a 2N3906 PNP transistor, which operate as a high-gain amplifier.

The 1-M Ω resistor supplies bias current. The 1-k Ω resistor helps linearize the oscillator waveform into one that is close to a square wave with about a 50-to-50 duty cycle. The capacitor supplies positive feedback from the output of the amplifier to the noninverting input. The frequency of oscillation depends mostly on the RC constant of

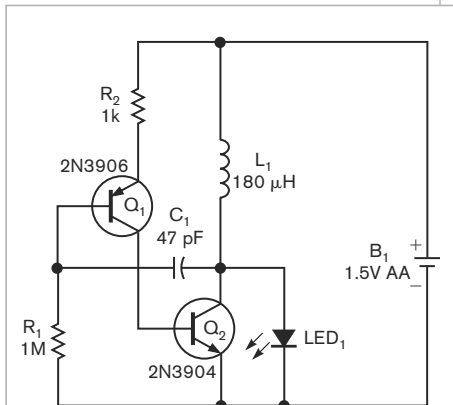


Figure 1 This two-transistor circuit operates as a high-gain amplifier to light LEDs.

the feedback capacitor and the input-stage impedance. The circuit oscillates at 91 kHz with a 48% duty cycle. You can use almost any common NPN or PNP transistors, as long as they have moderate forward-current gain of 50 or more and can handle 100-mA collector currents.

The LED connects across the output transistor because this approach lets the inductive kickback voltage add to the battery-supply voltage and makes the LED brighter. This circuit operates well from approximately 0.8 to 1.6V, which is the useful range of an alkaline battery. The LED-light output decreases as the supply voltage decreases from 1.6 to 0.8V.**EDN**

REFERENCE

1 Bruno, Luca, "Astable multivibrator lights LED from a single cell," *EDN*, Aug 21, 2008, pg 53, www.edn.com/article/CA6586223.