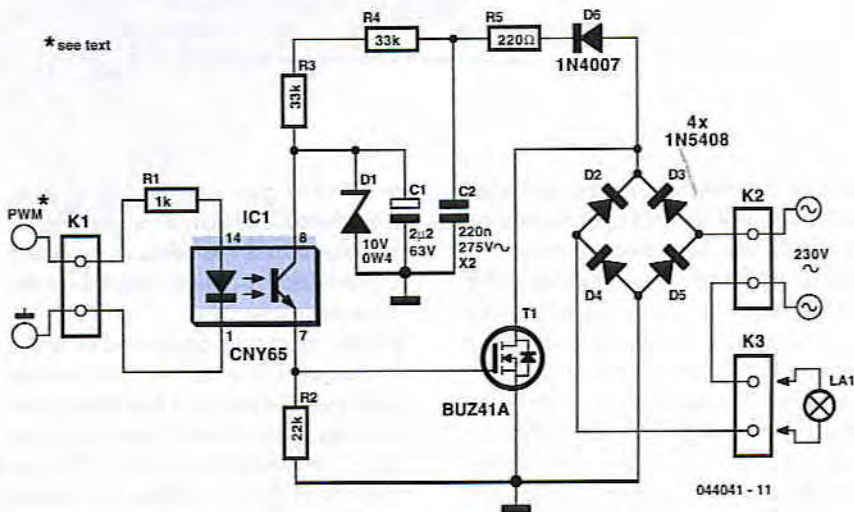


Ton Giesberts

This circuit shows that dimmers intended for use at mains voltage do not always have to contain a triac. Here, a MOSFET (BUZ41A, 500 V/4.5A) in a diode bridge is used to control the voltage across an incandescent bulb with pulse-width modulation (PWM). A useful PWM controller can be found elsewhere in this issue. The power supply voltage for driving the gate is supplied by the voltage across the MOSFET. D₆, R₅ and C₂ form a rectifier. R₅ limits the current pulses through D₆ to about 1.5 A (as a consequence it is no longer a pure peak rectifier). The voltage across C₂ is regulated to a maximum value of 10 V by R₃, R₄, C₁ and D₁.

An optocoupler and resistor (R₂) are used for driving the gate. R₁ is intended as protection for the LED in the optocoupler. R₁ also functions as a normal current limiting device so that a 'hard' voltage can be applied safely. The optocoupler is an old acquaintance, the CNY65, which provides class-II isolation. This ensures the safety of the regulator. The transistor in the optocoupler is connected to the positive power supply so that T₁ can be brought into conduction as quickly as possible. In order to reduce switching spikes as a consequence of parasitic inductance, the value of R₂ has been selected to be not too low: 22 k Ω is a compromise between inductive voltages and switching loss when going into and out of conduction. An additional effect is that T₁ will conduct a little longer than what may be expected



from the PWM signal only. When the voltage across T₁ reduces, the voltage across D₁ remains equal to 10 V up to a duty cycle of 88 %. A higher duty cycle results in a lower voltage. At 94 % the voltage of 4.8 V proved to be just enough to cause T₁ to conduct sufficiently. This value may be considered the maximum duty cycle. At this value the transistor is just about 100 % in conduction. At 230 V mains voltage, the voltage across the lamp is only 2.5 V lower, measured with a 100-W lamp.

Just to be clear, note that this circuit cannot be used to control inductive loads. T₁ is switched asynchronously with the mains frequency and this can cause DC current to flow. Electronic lamps, such as the PL types, cannot be dimmed with this circuit

either. These lamps use a rectifier and internally they actually operate off DC.

A few remarks about the size of R₃ and R₄. This is a compromise between the lowest possible current consumption (when the lamp is off) and the highest possible duty cycle that is allowed. When the duty cycle is zero, the voltage across the resistors is at maximum, around 128 V with a mains voltage of 230 V. Because (depending on the actual resistor) the voltage rating of the resistor may be less than 300 V, two resistors are connected in series. The power that each resistor dissipates amounts to a maximum of 0.5 W. With an eye on the life expectancy, it would be wise to use two 1-W rated resistors here.

(044041-1)