

design ideas

D_2 and resistor R_3 charge C_2 and establish a logic one at IC_1 's Pin 2. When the voltage at point E_1 reaches approximately 2.7V, IC_1 's input-voltage threshold, IC_1 's output goes to logic zero, switching off Q_1 .

Energy stored in L_1 's magnetic field discharges through fast-recovery diode D_3 and charges C_3 . Capacitor C_1 helps remove diode D_1 's stored charge and helps restart the charging cycle.

After several cycles, the voltage at E_2 reaches the device under test's reverse-breakdown voltage and feeds current via R_1 to IC_1 's Pin 1. As a result, the voltage at E_2 stabilizes at the sum of the device under test's reverse-breakdown voltage and a constant offset voltage of 5.4V comprising the voltage across D_1 —

4.7V—plus the forward voltage across D_3 —0.7V. Thus, for a 100V zener as the device under test, the voltage at E_2 measures approximately 105.4V.

At start-up and under fault conditions, resistor R_4 , diode D_2 , and resistor R_3 produce an asymmetrical oscillation at approximately 2 kHz, which reduces the average current through L_1 and Q_1 to a safe level.

To use the circuit as a variable medium-voltage power supply, replace the device under test with the network in **Figure 1b**. Adjusting the potentiometer varies the voltage at point E_2 from 22 to 120V. Maximum current available from the circuit depends on the dc resistance, L_1 's magnetic-saturation characteristics, and Q_1 's on-resistance. For a nominal 5V

power supply and 430 mA of input current, the circuit delivers 10 mA at 100V for a 100V output, yielding an efficiency of approximately 50%. Feeding L_1 from a separate 12V power supply improves efficiency.

If you design your own inductor for L_1 , aim for a nominal inductance of 330 μ H at 2A and a dc winding resistance of less than 0.5 Ω . For optimum operation, use a fast-recovery diode for D_3 and a logic-level N-channel MOSFET with a breakdown voltage of 200V or greater and an on-resistance of less than 0.3 Ω for Q_1 . Note that zener-diode manufacturers specify breakdown voltages at specific test currents. Also, when you subject them to high reverse voltages, signal diodes exhibit zener behavior. \square