

Shunt regulator serves as inexpensive op amp in power supplies

Michael O'Loughlin, Texas Instruments, Nashua, NH

Developed as a three-terminal shunt regulator, the popular and multiple-sourced TL431 IC offers designers many intriguing possibilities beyond its intended application. Internally, the TL431 comprises a precision voltage reference, an operational amplifier, and a shunt transistor (**Figure 1a**). In a typical voltage-regulator application, adding two external resistors, R_A and R_B , sets the shunt-regulated output voltage at the lower end of load resistor R_S (**Figure 1b**).

In today's power-supply market, cost reduction drives most designs, as evidenced by Asian manufacturers that have resorted to shaving pennies off their power-supply products by using single-sided pc boards. This Design Idea shows how a three-terminal shunt reg-

ulator can replace a more expensive conventional operational amplifier in a power-converter design.

A switched-mode power supply uses a galvanically isolated feedback portion of a PWM circuit (**Figure 2**). In designs that omit a voltage amplifier, a shunt regulator can serve as an inexpensive op amp. Resistors R_1 and R_2 set the power supply's dc output voltage, and optocoupler IC_2 provides galvanic isolation. Resistor R_1 provides bias for the optocoupler and the TL431, IC_1 . Resistor R_3 and zener diode D_1 establish a fixed bias voltage to ensure that bias resistor R_1 does not form a feedback path. Resistors R_1 and R_2 control the gain across the optocoupler. In most designs, the ratio of R_2 to R_1 is roughly 10-to-1.

Components C_p , C_z , and R_z provide frequency compensation for the control loop. The optocoupler includes a high-frequency pole, f_p , in its frequency response, an item that most optocouplers' data sheets omit. You can use a network analyzer to determine the location of the high-frequency pole or estimate that the pole occurs at approximately 10 kHz. The following equation describes the compensation network's small-signal transfer function:

$$G_C(s) = \frac{\Delta V_{ERR}}{\Delta V_{OUT}} = \frac{(s \times R_z \times C_z + 1)}{s \times R_1 (C_z + C_p) \left(\frac{s \times R_z \times C_p \times C_z + 1}{C_p + C_z} + 1 \right)} \times \frac{R_2}{R_1} \times \left(\frac{1}{\left(\frac{s}{2 \times \pi \times f_p} + 1 \right)} \right)$$

Note that, under some circumstances, adding a bypass capacitor across diode D_1 may be necessary for output-noise reduction. **EDN**

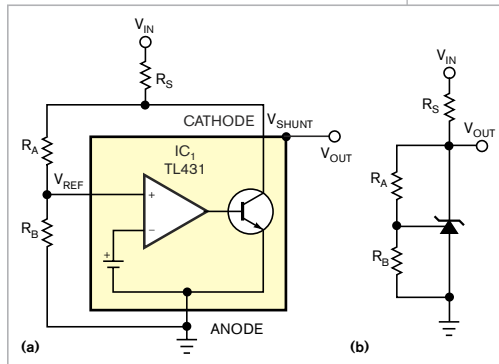


Figure 1 Despite the block diagram, the TL431 is internally complex (a), but you need only three external resistors to use the TL431 in a basic shunt-regulator circuit (b).

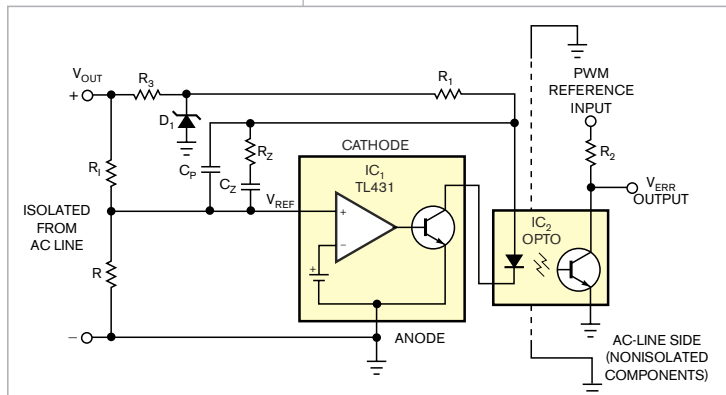


Figure 2 A TL431 replaces a more expensive operational amplifier in this power supply's PWM feedback-regulator circuit.