
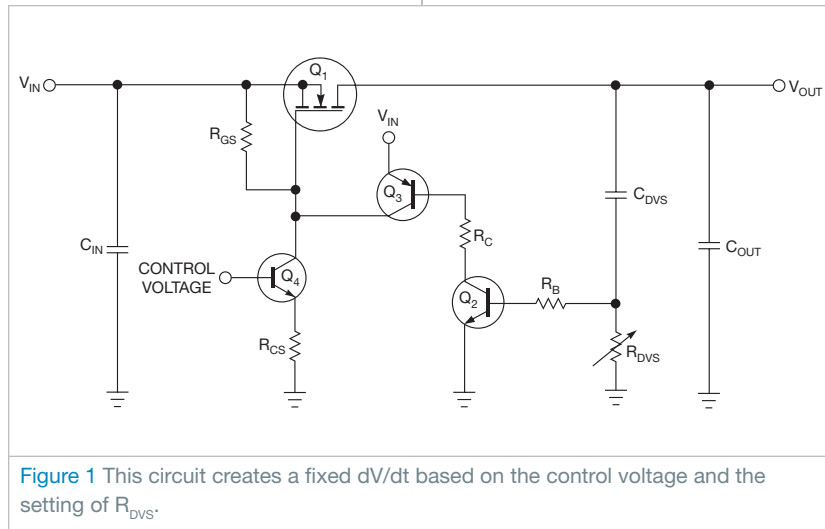


# Simple circuit controls the rate of voltage change across a capacitor or another load

Fabien Dubois, Ampere Lab, Lyon, France

 The circuit in this Design Idea lets you set a well-controlled voltage rate of change, often expressed as the differential  $dV/dt$  (instantaneous rate of voltage change over time in volts per second). You can vary the sensitivity with a potentiometer. Set the  $dV/dt$  from 1V/200 nsec to 1V/3 msec.

The input voltage can range from a few volts to 30V. Higher-voltage transistors can be used to increase the upper voltage limit. The circuit precharges a capacitor with a slow and controllable  $dV/dt$  to avoid a large inrush current during power-up. You can also use the circuit to create a high  $dV/dt$  for sus-



**Figure 1** This circuit creates a fixed  $dV/dt$  based on the control voltage and the setting of  $R_{DVS}$ .

ceptibility testing on other circuits.

The circuit uses a P-channel MOSFET,  $Q_1$ , to control the rate of change of the output voltage (**Figure 1**). You drive the MOSFET with a constant-current source comprising  $Q_4$  and  $R_{CS}$ , which feeds gate-to-source resistor  $R_{GS}$ . Applying a positive control voltage to the base of  $Q_4$  draws a current that creates a voltage across  $R_{GS}$ . This voltage occurs across the gate and source of  $Q_1$ , turning it on. The circuit uses capacitor  $C_{DVS}$  as a sensing device of the rate of change of the output voltage. Voltage variations across  $C_{DVS}$  generate a current that creates a current proportional to the  $dV/dt$ , as the following **equation** shows:

$$I_{CS} = C_{DVS} \times \frac{dV_{OUT}(t)}{dt}$$

Resistor  $R_{DVS}$  converts this current into a voltage signal. When that voltage reaches approximately 0.67V, it turns on  $Q_2$ , which turns on  $Q_3$ . The current that  $Q_3$  supplies from the input tends to lower the  $Q_1$  gate-to-source voltage and reduces its drive. You use  $R_B$  to limit the base current of  $Q_2$ . This servo action puts the gate-to-source voltage of the MOSFET in the Miller plateau, a constant-current region of the FET's characteristic curve. The FET has an internal Miller capacitance,  $C_{GD}$ , between the gate and the drain pins.

**TABLE 1** CIRCUIT PART NUMBERS

Component	Description	Manufacturer	Part no.
$C_{IN}$	10- $\mu$ F, 50V tantalum capacitor	AVX	TPSE106K050R0500
$C_{OUT}$	1- $\mu$ F, 50V ceramic capacitor	AVX	12065C105KAT2A
$C_{DVS}$	10-nF, 50V ceramic capacitor	AVX	08055C103KAT2A
$Q_2$ and $Q_4$	40V, 0.6A NPN transistor	On Semiconductor	MMBT2222ALT1G
$Q_3$	60V, 1.2A PNP transistor	On Semiconductor	MMBT2907ALT1G
$Q_1$	100V, 4A power MOSFET	Vishay	IRF9510SPBF
$R_B$	1-k $\Omega$ , 0603, 1% resistor	Vishay	CRCW12061K00FKEA
$R_C$	1-k $\Omega$ , 0603, 1% resistor	Vishay	CRCW12061K00FKEA
$R_{CS}$	10-k $\Omega$ , 0603, 1% resistor	Vishay	CRCW120610K0FKEA
$R_{DVS}$	10-k $\Omega$ trimming potentiometer	Bourns	3362W-1-503LF
$R_{GS}$	10-k $\Omega$ , 0603, 1% resistor	Vishay	CRCW120610K0FKEA

The circuit's constant-current source controls the charge current of this Miller capacitance. As transistor  $Q_3$  injects current to the gate, Miller current  $I_{GD}$  decreases and the slope of the output voltage decreases accordingly, as the following **equation** shows:

$$\frac{dV_{dS}(t)}{dt} = \frac{I_{GD}}{C_{GD}}.$$

The feedback loop keeps the  $dV/dt$  ratio constant. The rate of change of the output voltage is a function of the base-emitter voltage of  $Q_2$ ,  $R_{DVS}$ , and

$C_{DVS}$ , as the following **equation** shows:

$$\frac{dV_{OUT}(t)}{dt} \approx \frac{V_{BEQ1}}{R_{VDS} \times C_{DVS}}.$$

You can build the circuit with the part numbers in **Table 1**. **EDN**