

Dual transistor improves current-sense circuit

Robert Zawislak, PE, Consultant, Palatine, IL



In multiple-output power supplies in which a single supply powers circuitry of vastly different current draws, two perplexing steps are

sensing the current that each output draws and deactivating the power supply in the event of an overload on that output. These issues are especially important in protecting the fragile PCB (printed-circuit-board) traces in low-level circuits. A typical circuit would use the base-emitter threshold volt-

age of approximately 0.6V of a bipolar transistor to trigger the power-supply-protection circuits. Although economical, the transistor's threshold varies excessively over temperature; hence, the protection level is unstable.

The circuit in **Figure 1** essentially eliminates the base-emitter-voltage temperature-variation problem as the

derivation of the output voltage and as a function of the load current. By using dual bipolar devices in one case, the manufacturer nearly perfectly matches the two devices. Although this Design Idea describes a positive power supply, you can realize a similar negative-output-supply current-sense circuit using a dual NPN transistor in place of the

dual PNP that the **figure** shows.

The following **equations** show the derivation of the output voltage as a function of the load current (referring to **Figure 1**):

$$V_{BA} + (I_{LOAD} \times R_{SENSE}) + (I_E \times R_2) - V_{BB} = 0$$

$$[(V_{BA} - V_{BB}) + (I_{LOAD} \times R_{SENSE})] - I_E R_2 = 0$$

$$I_C + I_B = I_E$$

$$(V_{BA} - V_{BB}) + (I_{LOAD} \times R_{SENSE}) - (I_C + I_B) R_2 = 0$$

$$I_B = I_C / \beta$$

$$V_{BA} - V_{BB} + I_{LOAD} \times R_{SENSE} - (I_C + I_C / \beta) R_2 = 0$$

$$V_{BA} - V_{BB} + I_{LOAD} \times R_{SENSE} - [I_C \times (\beta + 1) / \beta] R_2 = 0$$

$$V_{OUT} = I_C R_3$$

$$I_C = V_{OUT} / R_3$$

$$V_{BA} - V_{BB} + I_{LOAD} \times R_{SENSE} - (V_{OUT} / R_3) (\beta + 1 / \beta) R_2 = 0$$

If $V_{BA} = V_{BB}$, then $V_{BA} - V_{BB} = 0$, and

$$I_{LOAD} \times R_{SENSE} - (V_{OUT} / R_3) (\beta + 1 / \beta) R_2 = 0$$

$$V_{OUT} = I_{LOAD} \times R_{SENSE} [R_3 / (\beta + 1)] (\beta / R_2)$$

If β is high, then $\beta / (\beta + 1) \approx 1$, and

$$V_{OUT} = (I_{LOAD} \times R_{SENSE} \times R_3) / R_2 \text{ EDN}$$

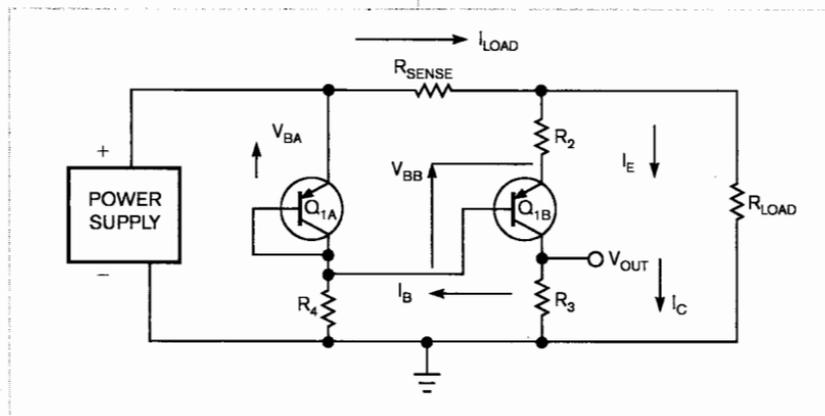


Figure 1 This simple two-transistor circuit provides a voltage output proportional to the current through sense resistor R_{SENSE} .

Improving High-Side Current Measurements

By **Maurizio Gavardoni**, Product Definer,
Maxim Integrated Products, Sunnyvale, Calif.

An IC that combines a high-side current-sense amplifier with an analog voltage multiplier can easily measure the power dissipated in a load. One multiplier input connects to the load voltage and the other to an internal analog of the load current (i.e., a proportional voltage produced by the internal current-sense amplifier). The multiplier output ($V_L \times I_L$) is then a voltage proportional to load power.

The internal multiplier also can enable extra accuracy in high-side current measurements, for applications in which the current signal is digitized by an analog-to-digital converter (ADC). Whether the ADC's voltage reference is internal or external to the ADC, the accuracy of the digitized load-current measurement depends strongly on the accuracy and stability of that reference.

To minimize this dependency on voltage-reference accuracy, connect the multiplier's external input to the reference voltage through a resistive divider (Fig. 1). The current measurement is then ratiometric. Any error or drift in the reference voltage has a proportional effect on the ADC's input, and thereby achieves a first-order cancellation of full-scale error caused by the reference voltage.

The circuit shown can measure battery charge and discharge currents in a wide range of applications. It works

equally well with a voltage reference internal to the ADC, driving the R1-R2 divider.

The IC's multiplier output (P_{OUT}) feeds a 16-bit ADC whose input voltage range is 0 V to V_{REF} . V_{REF} , provided here by an external voltage regulator, should be between 1.2 V and 3.8 V (3.8 V in this case). The multiplier input must be limited to a range of 0 V to 1 V, which is accomplished by dividing the 3.8-V reference voltage with the R1-R2 resistor divider.

Assuming $R2 = 1 \text{ k}\Omega$ and $R1 = 2.8 \text{ k}\Omega$, then $V_{IN} = 1 \text{ V}$. The IC has a gain of 25 between V_{SENSE} and I_{OUT} , and a sense-voltage range (V_{SENSE}) of 0 V to 150 mV, which produces (at both P_{OUT} and I_{OUT}) an output range of 0 V to 3.75 V.

Thus, the use of P_{OUT} (instead of I_{OUT}) confers an advantage: the signal fed to the ADC, which is proportional to current in the load, is scaled by V_{REF} . The following equation relates the P_{OUT}/V_{REF} ratio to I_{LOAD} , R_{SENSE} , and the values of R1 and R2:

$$\frac{P_{OUT}}{V_{REF}} = I_{LOAD} \times R_{SENSE} \times 25 \times V_{REF} \times R2 / (R1 + R2) / V_{REF} = I_{LOAD} \times R_{SENSE} \times 25 \times R2 / (R1 + R2)$$

Note that the ratio of ADC input to ADC full scale (P_{OUT}/V_{REF}) does not depend on the accuracy of V_{REF} .

Overall accuracy of the current measurement depends on many factors: resistor tolerance, amplifier gain error, voltage offset and bias current, reference voltage accuracy, ADC errors and drift versus temperature for all the above. This circuit improves accuracy by eliminating only one of these causes: the reference voltage inaccuracy. V_{REF} is affected by at least three sources of error: initial dc error as a percentage of the nominal value, V_{REF} changes with load and V_{REF} changes with temperature.

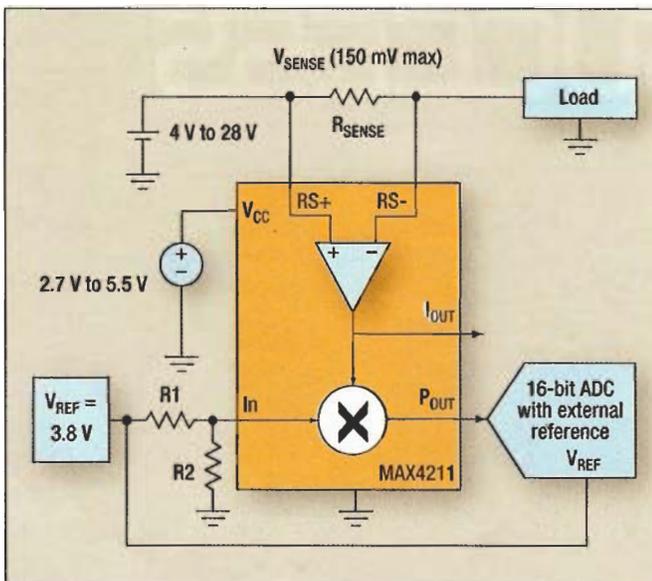


Fig. 1. This circuit uses a high-side power/current monitor (MAX4211) plus an ADC with external reference voltage to measure battery-charge currents with a high level of precision.

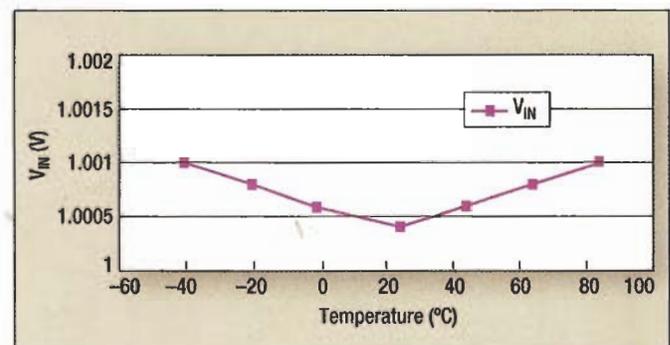


Fig. 2. The input voltage to the multiplier (V_{IN}) in Fig. 1 varies as a function of temperature, reflecting the voltage reference's variation over temperature ($V_{CC} = 5 \text{ V}$ and $V_{SENSE} = 100 \text{ mV}$).

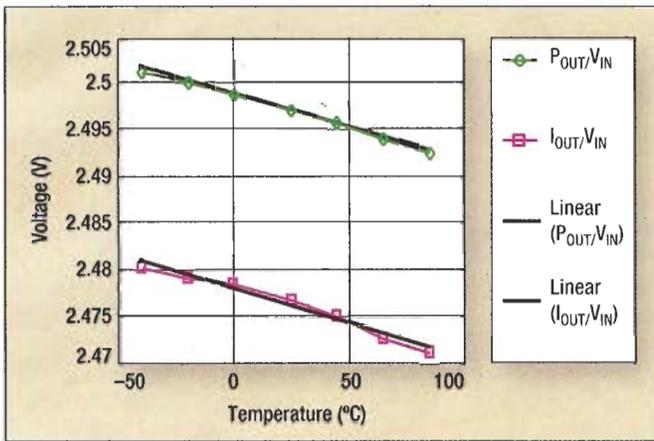


Fig. 3. The measured P_{OUT}/V_{IN} ratio in Fig. 1. is the same as the expected (linear) value of this ratio over temperature, unlike the measured I_{OUT}/V_{IN} ratio ($V_{SENSE} = 100$ mV).

A graph of the multiplier input (IN) versus temperature, with $V_{CC} = 5$ V and V_{SENSE} constant at 100 mV, shows the affect of temperature on the reference voltage (Fig. 2). To see the advantage of the ratiometric output at P_{OUT} , compare the P_{OUT}/V_{IN} ratio and its linear ideal with the I_{OUT}/V_{IN} ratio and its linear ideal, as they vary with temperature (Fig. 3). Note that the ratiometric P_{OUT} output (top) does not deviate from the ideal.

PETech

Bringing Innovation to Current Sense Transformers

The CTO2 Series, Another Innovative Solution from ICE Components.



- ▶ 33% Smaller Footprint
- ▶ 300% Increase in Current Rating
- ▶ 300% Increase in Hi-pot Rating: 1,500VAC
- ▶ Current Rating up to 18A
- ▶ Improved Frequency Range

In the business of power, smaller is better, and the CTO2 Series is the clear market leader. Boasting a 33% smaller footprint and 3x the current rating, comparable parts in the market cannot compete.

(800) 729-2099 Toll-free
www.icecomponents.com
custserv@icecomp.com

ice components
Helping Engineer the Technology of Power

When your products must meet the world's safety standards, design in Bel's circuit protection devices! From PTC resettable devices, to fuses for telecom, ballast, power supply and charger, plus portable applications, our parts are UL, CSA, PSE, CCC, VDE and Semko approved.

Circuit Protection Devices

Polymer PTC Resettable Devices

- Radials to 240VAC Continuous Operation
- Radials to 600VAC for Telecom Applications
- 2920/1812 Chips

Fuses

- Fast Act 0603/1206 & Slow Blow 1206 Chips
- SIP Modules for Tip and Ring Applications
- Telecom Surge Protection-600V (UL60950, GR1089)

bel COMPONENTS FOR A CONNECTED PLANET

www.belfuse.com • 1-800-BELFUSE