


## High-side current sensing with comparator circuit

### Design Goals

Load Current ( $I_L$ )		System Supply ( $V_S$ )	Comparator Output Status	
Over Current ( $I_{OC}$ )	Recovery Current ( $I_{RC}$ )	Typical	Over Current	Normal Operation
1 A	0.5 A	10 V	$V_{OL} < 0.4$ V	$V_{OH} = V_{PU} = 3.3$ V
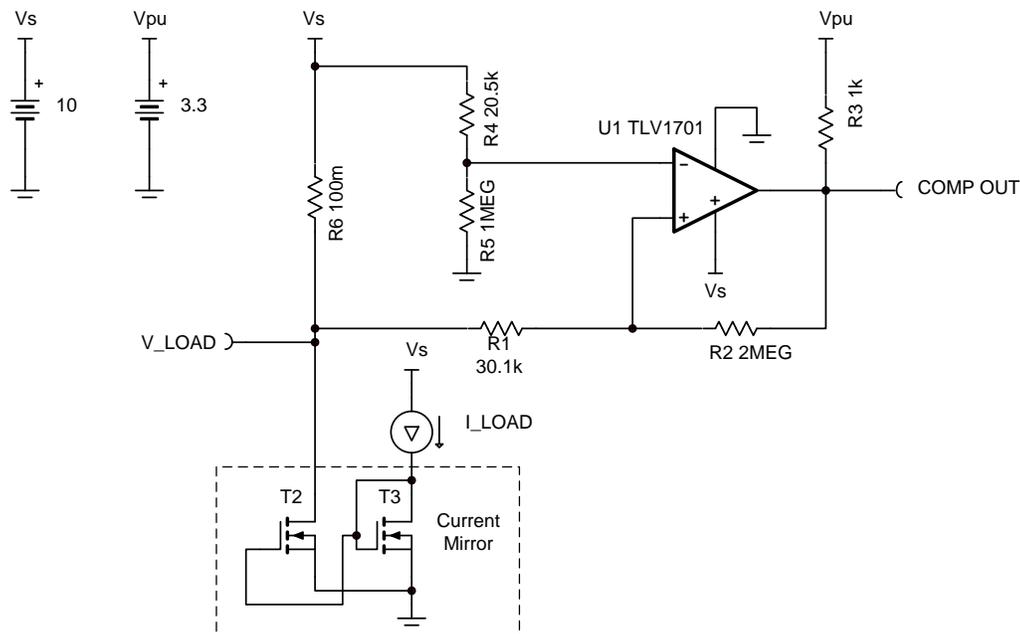
### Design Description

This high-side, current sensing solution uses one comparator with a rail-to-rail input common mode range to create an over-current alert (OC-Alert) signal at the comparator output (COMP OUT) if the load current rises above 1A. The OC-Alert signal in this implementation is active low. So when the 1A threshold is exceeded, the comparator output goes low. Hysteresis is implemented such that OC-Alert will return to a logic high state when the load current reduces to 0.5A (a 50% reduction). This circuit utilizes an open-drain output comparator in order to level shift the output high logic level for controlling a digital logic input pin. For applications needing to drive the gate of a MOSFET switch, a comparator with a push-pull output is preferred.



### Design Notes

1. Select a comparator with rail-to-rail input common mode range to enable high-side current sensing.
2. Select a comparator with an open-drain output stage for level-shifting.
3. Select a comparator with low input offset voltage to optimize accuracy.
4. Calculate the value for the shunt resistor ( $R_S$ ) so the shunt voltage ( $V_{SHUNT}$ ) is at least ten times larger than the comparator offset voltage ( $V_{IO}$ ).

## Design Steps

1. Select value of  $R_6$  so  $V_{SHUNT}$  is at least 10x greater than the comparator input offset voltage ( $V_{IO}$ ). Note that making  $R_6$  very large will improve OC detection accuracy but will reduce supply headroom.


$$V_{SHUNT} = (I_{OC} \times R_6) \geq 10 \times V_{IO} = 55\text{mV}$$

$$\text{set } R_6 = 100\text{m}\Omega \text{ for } I_{OC} = 1\text{A} \ \& \ V_{IO} = 5.5\text{mV}$$

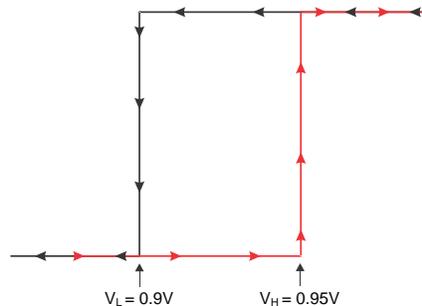
2. Determine the desired switching thresholds for when the comparator output will transition from high-to-low ( $V_L$ ) and low-to-high ( $V_H$ ).  $V_L$  represents the threshold when the load current crosses the OC level, while  $V_H$  represents the threshold when the load current recovers to a normal operating level.

$$V_L = V_S - (I_{OC} \times R_6) = 10 - (1 \times 0.1) = 0.9\text{V}$$

$$V_H = V_S - (I_{RC} \times R_6) = 10 - (0.5 \times 0.1) = 0.95\text{V}$$




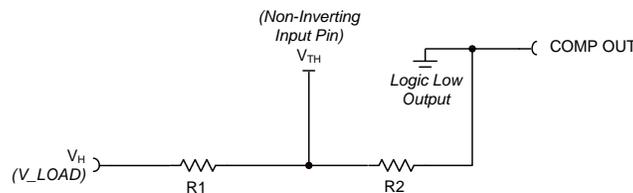3. With the non-inverting input pin of the comparator labeled as  $V_{TH}$  and the comparator output in a logic low state (ground), derive an equation for  $V_{TH}$  where  $V_H$  represents the load voltage ( $V_{LOAD}$ ) when the comparator output transitions from low to high. Note that the simplified diagram for deriving the equation shows the comparator output as ground (logic low).



$$V_{TH} = V_H \times \left( \frac{R_2}{R_1 + R_2} \right)$$

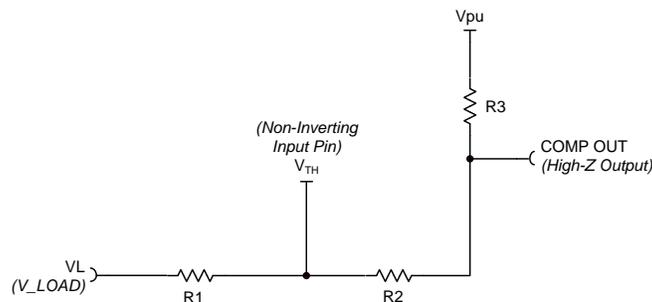4. With the non-inverting input pin of the comparator labeled as  $V_{TH}$  and the comparator output in a high-impedance state, derive an equation for  $V_{TH}$  where  $V_L$  represents the load voltage ( $V_{LOAD}$ ) when the comparator output transitions from high to low. Applying "superposition" theory to solve for  $V_{TH}$  is recommended.



$$V_{TH} = V_L \times \left( \frac{R_2 + R_3}{R_1 + R_2 + R_3} \right) + V_{PU} \times \left( \frac{R_1}{R_1 + R_2 + R_3} \right)$$

5. Eliminate variable  $V_{TH}$  by setting the two equations equal to each other and solve for  $R_1$ . The result is the following quadratic equation. Solving for  $R_2$  is less desirable since there are more standard values for small resistor values than the larger ones.

$$0 = (V_{PU}) \times R_1^2 + (V_{PU} \times R_2 + V_L \times (R_3 + R_2) - V_H \times R_2) \times R_1 + (V_L - V_H) \times (R_2^2 + R_2 \times R_3)$$

6. Calculate  $R_1$  after substituting in numeric values for  $V_{PU}$ ,  $R_2$ ,  $V_L$ ,  $V_H$ , and  $R_3$ . For this design, set  $V_{PU}=3.3$ ,  $R_2=2M$ ,  $V_L=9.9$ ,  $V_H=9.95$ , and  $R_3=1k$ . Please note that  $R_3$  is significantly smaller than  $R_2$  ( $R_3 \ll R_2$ ). Increasing  $R_3$  will cause the comparator logic high output level to increase beyond  $V_{PU}$  and should be avoided. For example, increasing  $R_3$  to a value of 100k can cause the logic high output to be 3.6V.

$$0 = (3.3) \times R_1^2 + (6.591M) \times R_1 - (200.1G)$$

the positive root for  $R_1 = 29.9k\Omega$

using standard 1% resistor values,  $R_1 = 30.1k\Omega$

7. Calculate  $V_{TH}$  using the equation derived in Design Step 3; use the calculated value for  $R_1$ . Note that  $V_{TH}$  is less than  $V_L$  since  $V_{PU}$  is less than  $V_L$ .

$$V_{TH} = V_H \times \left( \frac{R_2}{R_1 + R_2} \right) = 9.802V$$

8. With the inverting terminal labeled as  $V_{TH}$ , derive an equation for  $V_{TH}$  in terms of  $R_4$ ,  $R_5$ , and  $V_S$ .

$$V_{TH} = V_S \times \left( \frac{R_5}{R_4 + R_5} \right)$$


9. Calculate  $R_4$  after substituting in numeric values  $R_5=1M$ ,  $V_S=10$ , and the calculated value for  $V_{TH}$ .

$$R_4 = \left( \frac{R_5 \times (V_S - V_{TH})}{V_{TH}} \right) = 20.15k\Omega$$


using standard 1% resistor values,  $R_4 = 20.5k\Omega$

Design Simulations

DC Simulation Results

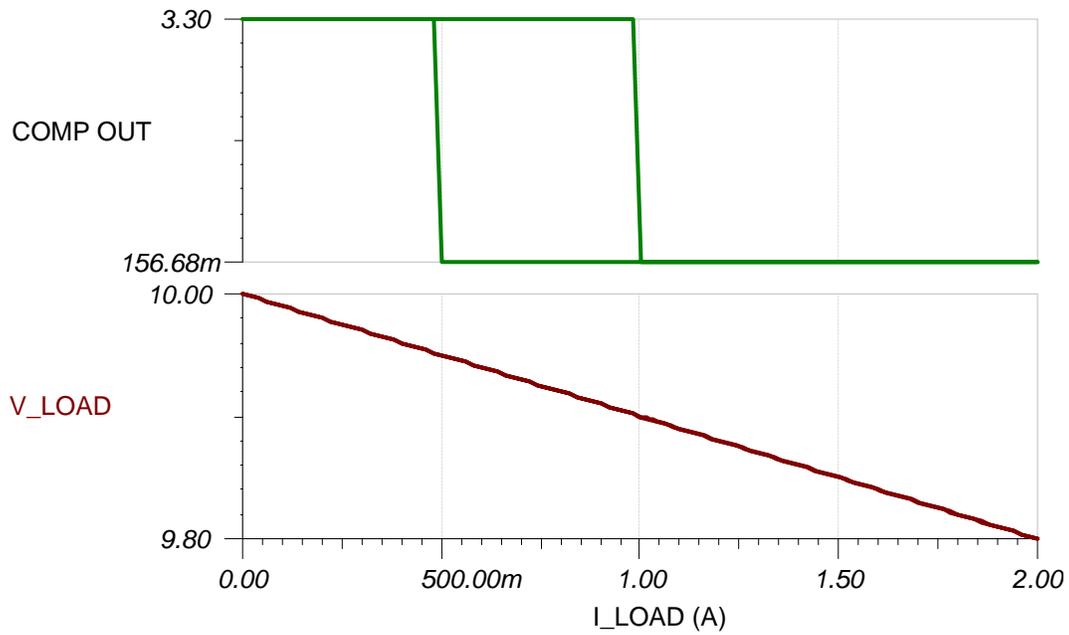

Transient Simulation Results

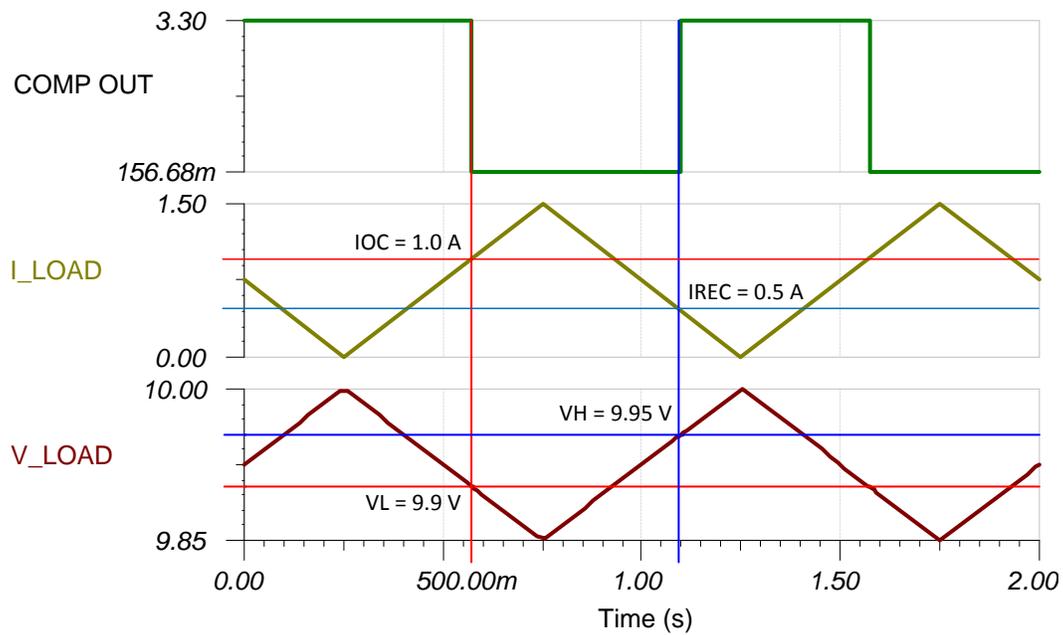

### Design References

See [Analog Engineer's Circuit Cookbooks](#) for TI's comprehensive circuit library.

See Circuit SPICE Simulation File SLOM456, <http://www.ti.com/lit/zip/slom456>.

### Design Featured Comparator

TLV170x-Q1, TLV170x	
$V_S$	2.2 V to 36 V
$V_{inCM}$	Rail-to-rail
$V_{OUT}$	Open-Drain, Rail-to-rail
$V_{OS}$	500 $\mu$ V
$I_Q$	55 $\mu$ A/channel
$t_{PD(HL)}$	460 ns
#Channels	1, 2, 4
<a href="http://www.ti.com/product/tlv1701-q1">www.ti.com/product/tlv1701-q1</a>	

### Design Alternate Comparator

	TLV7021	TLV370x-Q1, TLV340x
$V_S$	1.6 V to 5.5 V	2.7 V to 16 V
$V_{inCM}$	Rail-to-rail	Rail-to-rail
$V_{OUT}$	Open-Drain, Rail-to-rail	Push-Pull, Rail-to-rail
$V_{OS}$	500 $\mu$ V	250 $\mu$ V
$I_Q$	5 $\mu$ A	560 $\mu$ A/Ch
$t_{PD(HL)}$	260 ns	36 $\mu$ s
#Channels	1	1, 2, 4
	<a href="http://www.ti.com/product/tlv7021">www.ti.com/product/tlv7021</a>	<a href="http://www.ti.com/product/tlv3701-q1">www.ti.com/product/tlv3701-q1</a>