


3-decade, load-current sensing circuit

Design Goals

| Input | | Output | | Supply | | |
|------------|------------|------------|------------|----------|----------|-----------|
| I_{iMin} | I_{iMax} | V_{oMin} | V_{oMax} | V_{cc} | V_{ee} | V_{ref} |
| 10 μ A | 10mA | 100mV | 4.9V | 5.0V | 0V | 0V |

Design Description

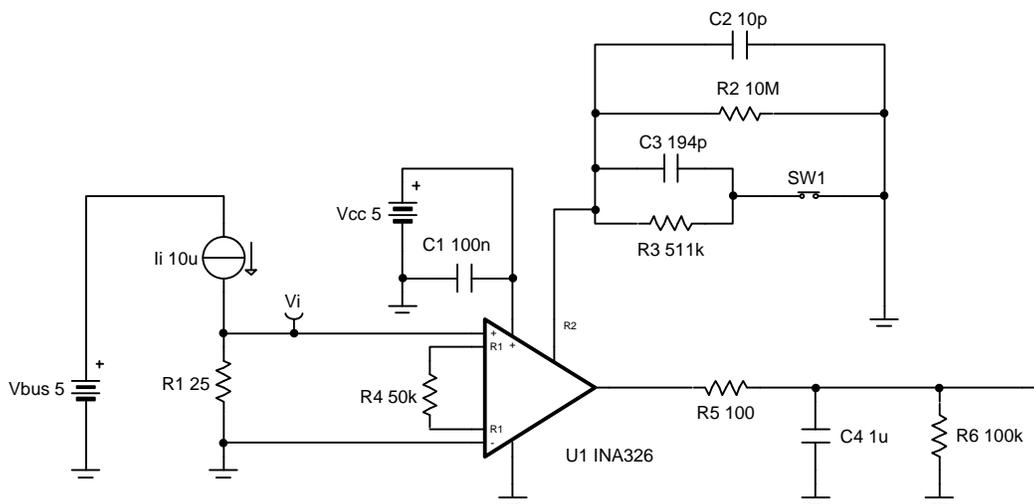This single-supply, low-side, current-sensing solution accurately detects load current between 10 μ A and 10mA. A unique yet simple gain switching network was implemented to accurately measure the three-decade load current range.



Design Notes

1. Use a maximum shunt resistance to minimize relative error at minimum load current.
2. Select 0.1% tolerance resistors for R_1 , R_2 , R_3 , and R_4 in order to achieve approximately 0.1% FSR gain error.
3. Use a switch with low on-resistance (R_{on}) to minimize interaction with feedback resistances, preserving gain accuracy.
4. Minimize capacitance on INA326 gain setting pins.
5. Scale the linear output swing based on the gain error specification.

Design Steps

1. Define full-scale shunt resistance.

$$R_1 = \frac{V_{iMax}}{I_{iMax}} = \frac{250mV}{10mA} = 25\Omega$$

2. Select gain resistors to set output range.

$$G_{iiMax} = \frac{V_{oMax}}{V_{iMax}} = \frac{V_{oMax}}{R_1 \times I_{iMax}} = \frac{4.9V}{25\Omega \times 10mA} = 19.6 \frac{V}{V}$$

$$G_{iiMin} = \frac{V_{oMin}}{V_{iMin}} = \frac{V_{oMin}}{R_1 \times I_{iMin}} = \frac{100mV}{25\Omega \times 10\mu A} = 400 \frac{V}{V}$$

$$R_2 = \frac{R_4 \times G_{iiMin}}{2} = \frac{50k\Omega \times 400 \frac{V}{V}}{2} = 10M\Omega$$

$$R_2 \parallel R_3 = \frac{R_4 \times G_{iiMax}}{2} = \frac{50k\Omega \times 19.6 \frac{V}{V}}{2} = 490k\Omega$$

$$R_3 = \frac{490k\Omega \times R_2}{R_2 - 490k\Omega} = 515.25k\Omega \approx 511k\Omega \text{ (Standard Value)}$$

3. Select a capacitor for the output filter.

$$f_p = \frac{1}{2 \times \pi \times R_5 \times C_4} = \frac{1}{2 \times \pi \times 100\Omega \times 1 \mu F} = 1.59kHz$$

4. Select a capacitor for gain and filtering network.


$$C_2 = \frac{1}{2 \times \pi \times R_2 \times f_p} = \frac{1}{2 \times \pi \times 10M\Omega \times 1.59kHz} = 10pF$$

$$C_3 = \frac{1}{2 \times \pi \times (R_2 \parallel R_3) \times f_p} - C_2 = \frac{1}{2 \times \pi \times (10M\Omega \parallel 511k\Omega) \times 1.59kHz} - 10pF$$


$$C_3 = 196pF \approx 194pF \text{ (Standard Value)}$$

Design Simulations

DC Simulation Results

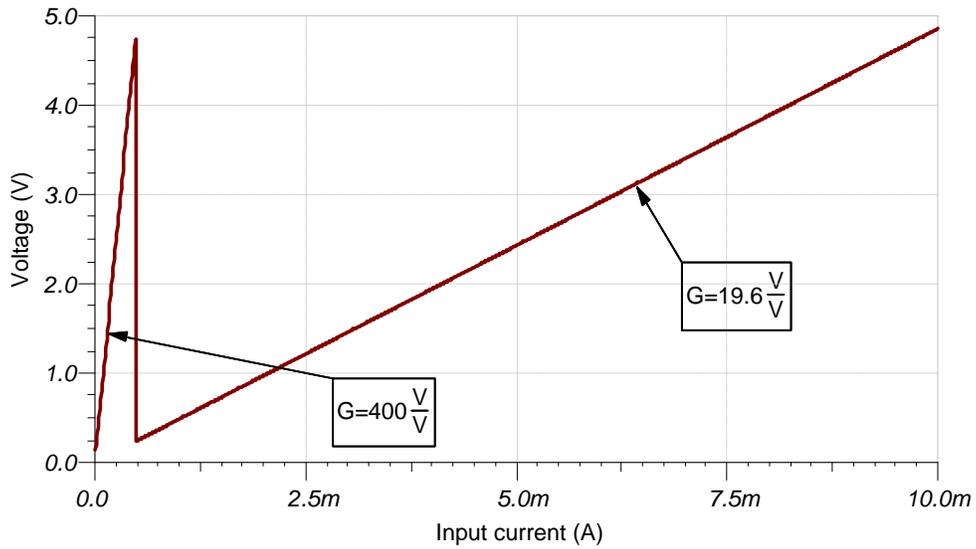

AC Simulation Results

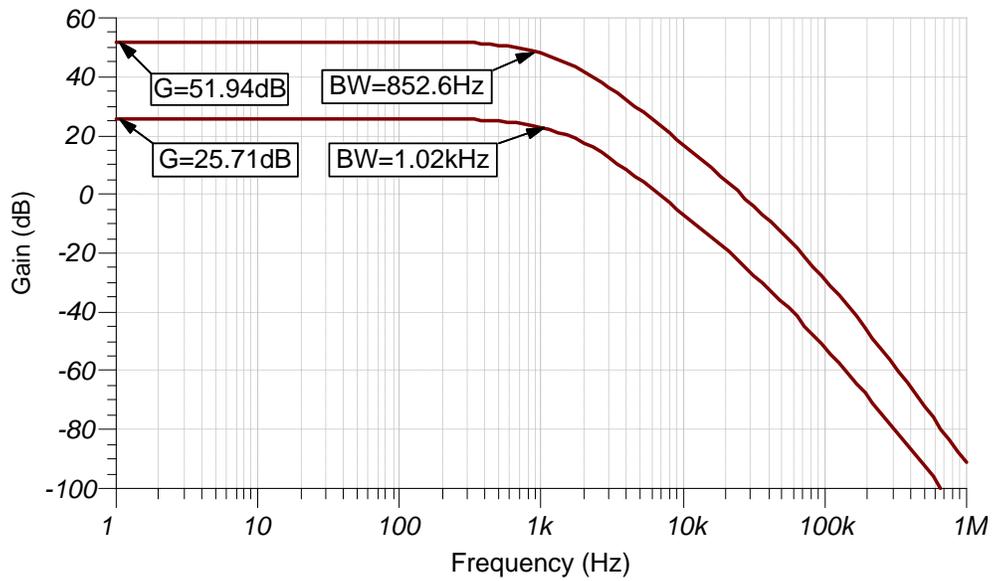

Design References

See [Analog Engineer's Circuit Cookbooks](#) for TI's comprehensive circuit library.

See circuit SPICE simulation file [SBOC498](#).

See TIPD104, www.ti.com/tool/tipd104.

Design Featured Op Amp

| INA326 | |
|--|----------------|
| V_{SS} | 1.8V to 5.5V |
| V_{inCM} | Rail-to-rail |
| V_{out} | Rail-to-rail |
| V_{os} | 0.1mV |
| I_q | 3.4mA |
| I_b | 2nA |
| UGBW | 1kHz |
| SR | Filter limited |
| #Channels | 1 |
| www.ti.com/product/ina326 | |

Revision History

| Revision | Date | Change |
|----------|--------------|---|
| A | January 2019 | Downscale the title and changed title role to 'Amplifiers'. Added link to circuit cookbook landing page. |