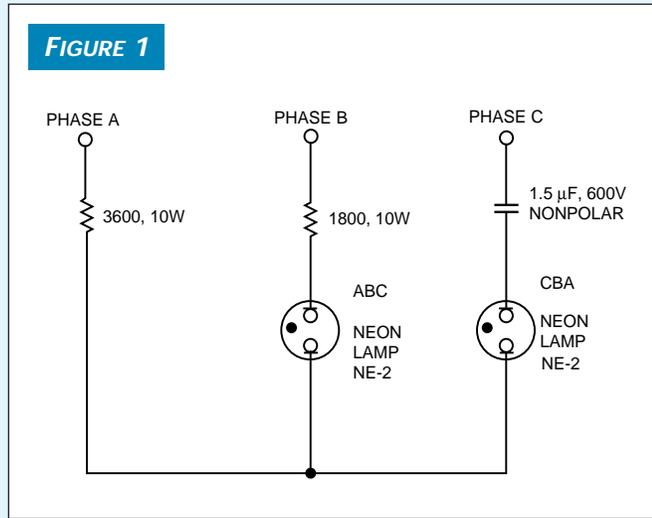


\$5 junk-box circuit determines phase sequence

HUGH ADAMS, FORT WALTON BEACH, FL

Have you ever wondered which way a blower motor is going to turn when you plug it into another socket, or have you ever inherited the task of modifying three-phase wiring in your plant? The circuit in **Figure 1** is a simple, approximately



The brighter of the two neon lamps indicates the phase sequence, either ABC or CBA.

\$5 phase sequencer that you can probably build from parts in your junk box and save approximately \$50 to boot. The component values reflect 60-Hz operation, but the design equations in **Figures 2** and **3** allow you to select values for other frequencies. The equations are in MathCAD spread-

FIGURE 2

$$f=60$$

$$C=1.5 \cdot 10^{-6}$$

$$V=0$$

$$R1=3600 \quad R2=1800$$

$$x = \frac{1}{2 \cdot \pi \cdot f \cdot C}$$

$$x = 1.768 \cdot 10^3$$

$$IA = \frac{1}{R1} (120 \cdot \cos(2 \cdot \pi \cdot f) - V)$$

$$IB = \frac{1}{R2} (120 \cdot \cos(2 \cdot \pi \cdot f - 2 \cdot \frac{\pi}{3}) - V - 90)$$

$$IC = \frac{1}{\left[\left(\frac{1}{2 \cdot \pi \cdot f \cdot C} \right)^2 \right]^{wQ}} (120 \cdot \cos(2 \cdot \pi \cdot f - 4 \cdot \frac{\pi}{3} - \frac{\pi}{4}) - V - 90)$$

$$IA = 0.033$$

$$IB = -0.083$$

$$IC = -0.033$$

MathCAD spreadsheet equations show a higher current in Phase B than in Phase C of the circuit in Figure 1; therefore, the phase sequence is ABC.

sheet format, but almost any other spreadsheet would do.

Referring to **Figure 1** and the equations, you can see that the neon bulb that glows brighter indicates the phase sequence, or phase-rotation order, ABC or CBA. The bulb glows brighter because it carries more current because of the phase shift the 1.5- μ F capacitor provides. You can verify this assertion by examining the two sets of equations. Note that the two sets of equations have different expressions for I_B and I_C . In one, I_B lags I_A by $2\pi/3$; in the other, it lags by $4\pi/3$, and vice versa for I_C . The equations provide the mathematical way of reversing the phase sequence, and, as you can see, the two currents I_B and I_C reverse their relative magnitudes as the phase rotation reverses. (DI #2180) EDN

To Vote For This Design, Circle No. 369

FIGURE 3

$$\begin{aligned}
 f &= 60 & x &= \frac{1}{2 \cdot \pi \cdot f \cdot C} \\
 C &= 1.5 \cdot 10^{-6} & x &= 1.768 \cdot 10^3 \\
 V &= 0 \\
 R_1 &= 3600 \quad R_2 = 1800 \\
 I_A &= \frac{1}{R_1} (120 \cdot \cos(2 \cdot \pi \cdot f) - V) \\
 I_B &= \frac{1}{R_2} (120 \cdot \cos(2 \cdot \pi \cdot f - 4 \cdot \frac{\pi}{3}) - V - 90) \\
 I_C &= \frac{1}{\left[\left(\frac{1}{2 \cdot \pi \cdot f \cdot C} \right)^2 \right]^{wQ}} (120 \cdot \cos 2 \cdot \pi \cdot f - 2 \cdot \left(\frac{\pi}{3} - \frac{\pi}{4} \right) - V - 90) \\
 I_A &= 0.033 \\
 I_B &= -0.083 \\
 I_C &= -0.116
 \end{aligned}$$

A CBA phase sequence produces a higher current, thus a brighter neon lamp, in Phase C of the circuit in Figure 1.