

Phase-sequence indicator uses few passive components

Metodi Iliev, University of California—Berkeley



In a three-phase ac system, a power source with three wires delivers ac potentials of equal frequency and amplitudes with respect to a zero-potential wire, each shifted in phase by 120° from one wire to the next. Two possibilities exist for establishing a phase sequence. In the first, voltage on the second wire shifts by 120° relative to the first, and, in the second, a -120° shift occurs with respect to the first wire. Phase order determines the direction of rotation of three-phase ac motors and affects other equipment that requires the correct phase sequence: a positive 120° shift. You can use a few low-cost passive components to build a phase-sequence indicator.

Figure 1 shows a conceptual circuit that can detect both phase sequences.

For certain component values, the following conditions apply: The voltages across R_1 and C_2 are equal—that is, their magnitudes and phases are the same—only when V_{S2} occurs exactly 120° ahead of V_{S1} , which indicates the correct phase sequence. In this case, the voltage between points A and B is zero. Conversely, the voltages across C_2 and R_3 are equal only when V_{S2} is ahead of V_{S3} by 120° , which corresponds to a reversed sequence.

Referring to the phasor diagram in **Figure 2**, when the voltages across R_1 and C_2 are equal, $V_{C1} = -V_{R2}$, $V_{C1} + V_{R1} = V_{S1}$, and $V_{C2} + V_{R2} = V_{S2}$. The following equations satisfy these conditions: $|V_{R1}| = |V_{C2}| = (1/2) |V_{S2}| = (1/2) |V_{S1}|$, and $|V_{C1}| = |V_{R2}| = \cos(30^\circ) |V_{S1}| = \cos(30^\circ) |V_{S2}|$. You calculate the component values by

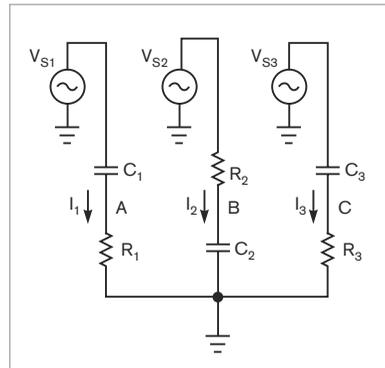


Figure 1 This conceptual circuit can detect both phase sequences.

solving the following equations: $|X_{C1}| = \tan(60^\circ) \times R_1 = \sqrt{3} \times R_1$, and $R_2 = \tan(60^\circ) \times |X_{C2}|$, where $X_C = -j[1/(2\pi \times f \times C)]$, and f represents the frequency of the V_S voltages.

Also, to ensure detection of a reversed phase sequence, $C_1 = C_3$, and $R_1 = R_3$; that is, the components in the

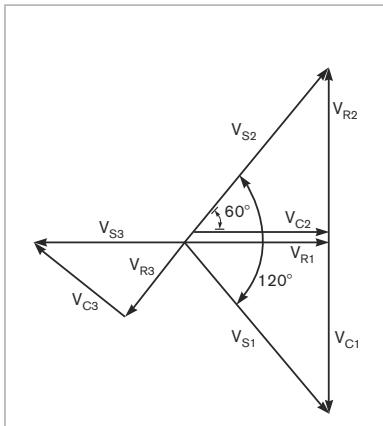


Figure 2 When the voltages across R_1 and C_2 are equal, $V_{C1} = -V_{R2}$, $V_{C1} + V_{R1} = V_{S1}$, and $V_{C2} + V_{R2} = V_{S2}$.

third branch are identical to those in the first branch. The phase-sequence-detection circuit in **Figure 3** eliminates the requirement for an accessible ground wire by adding resistors R_4 and R_5 that connect in parallel with the first and third branches. Eliminating the ground-wire requirement also dictates a ratio between $|X_{C1} + R_1|$ and $|X_{C2} + R_2|$. For no current to flow to ground from Node G, the sum of currents in the branches must equal zero, and, if you disconnect Node G from

ground, its potential with respect to ground is also zero.

As long as the proportions of X_{C1} to R_1 , X_{C2} to R_2 , and X_{C3} to R_3 remain as noted, the balance of voltage drops remains across R_1 , C_2 , and R_3 . Multiplying the impedance of any branch by a constant influences only the magnitude of the currents through the respective branch. The current through any branch presents the same phase angle as the voltage across a resistor in the branch. The phasor diagram in **Figure 4** shows the currents in **Figure 3**. From this diagram, if $|I_2| = \tan(60^\circ) \times |I_1|$, then $I_1 + I_2 = -2 \times I_3$. Thus, I_3 has half the magnitude of and an exactly opposite direction from $(I_1 + I_2)$.

A vector diagram of the currents shows that adding two currents, each with magnitudes equal to I_3 and the same phases as V_{S1} and V_{S3} , produces a summed current with the same magnitude and phase as I_3 ; therefore, the total current at Node G is zero: $I_1 + I_2 + I_3 + I_1' + I_3' = I_1 + I_2 + 2 \times I_3 = 0$. To make the sum of the currents equal zero, $R_4 = R_5 = |R_1 + X_{C1}| = |R_1 - j[1/(2\pi \times f \times C_1)]|$. The two LEDs in **Figure 3** indicate correct or reversed-phase sequence. When LED₂ lights and LED₁ remains dark, the voltage between nodes A and B is 0V, which corresponds

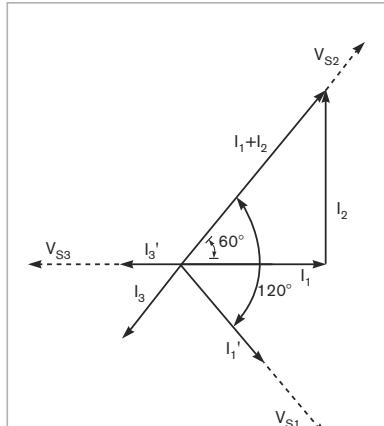


Figure 4 I_3 has half the magnitude and an exactly opposite direction to $(I_1 + I_2)$ in **Figure 3**.

to a correct phase sequence. A reversed-phase sequence lights LED₁ while LED₂ remains dark. The diodes connected in parallel with the LEDs protect against exceeding the LEDs' reverse-breakdown voltages, and resistors R_6 and R_7 limit forward currents through the LEDs. For greater sensitivity, you can replace the LEDs with high-input-impedance ac-detector circuits.

The circuit's final version includes indicators that show whether all three phases carry voltage. In the circuit in **Figure 3**, a phase that carries 0V lights both LEDs. Depending on your application, you can connect voltage-detection circuits comprising LEDs and protection diodes in series with current-limiting resistors between V_{S1} , V_{S2} , and V_{S3} and Node G. You can also use low-wattage neon lamps with appropriate series-current-limiting resistors.

When selecting components, ensure that their values conform to the following proportions. For an arbitrarily chosen value for C_1 , $R_1 = R_2 = R_3 = 1/(2\pi \times f \times C_1 \times \tan(60^\circ))$, $C_1 = C_3$, $C_2 = 3C_1$, and $R_4 = R_5 = 2 \times R_1$. When you select a value for C_1 , the currents through the detection circuitry should be significantly lower than the currents through the branches, which excludes arbitrarily low values for C_1 . **EDN**

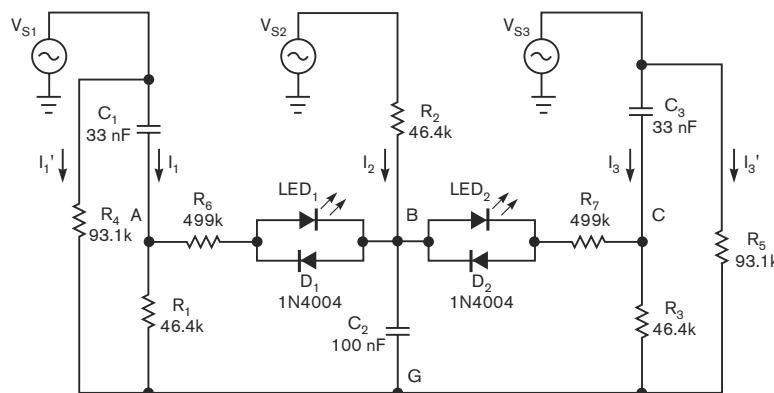


Figure 3 This phase-indicator circuit balances branch voltages and currents and requires no ground reference. These component values are for a 60-Hz line frequency.