



Save a link to this article and return to it at www.savethis.com Save a link to this article and return to it at www.savethis.com Email a link to this article

SAVE THIS EMAIL THIS PRINT THIS MOST POPULAR

Implementing Flyback Transformer Design for Continuous Mode

Jun 1, 2003 12:00 PM

By Keith Billings, DKB Power Inc., Ontario, Canada

For the PDF version of this article, [click here](#).

In [last month's Power Design column](#), we examined the functional principles of continuous mode (or incomplete energy transfer mode) of a flyback transformer. In this ferrite core.

Transformer Design Example

Fig. 1 shows a typical flyback converter as used for single output application. **Fig. 2** shows typical waveforms found in continuous mode operation. In this mode, energy the secondary when Q1 turns OFF We have a variable (top) part of the waveform, and an effective dc component, (as there would be in an output smoothing choke in a

For this transformer design example, we'll assume an output power requirement of 100W. The input voltage is 100V. The secondary voltage is 20V at a mean current of The example assumes 100% efficiency and zero diode drop.

The first step is to decide the load current range over which the continuous mode of operation is to be maintained. The larger the load range, the more turns and induct. This choice results in a ripple current of half the mean value at maximum load. The waveforms in **Figs. 2** and **3** show this condition. We must choose the maximum flux optimum choice is where total copper loss equals the core loss. This is an iterative process and can't be fully established at this stage. It must be checked in the final de provides a 50% flux margin for the dc polarizing force shown as B_{dc} on the vertical B scale in **Fig. 3**.

Further Flyback

- Designing Flyback Transformer for Discontinuous Mode
- Choosing Core for Flyback Transformer and Choke Designs
- Improving the Performance of Flyback Power Supplies

We can now calculate the minimum primary turns N_p ; (See **Equations**)

$V_p = 100V$, t (the ON period of Q1) is $10\mu s$, B_{max} is 0.166 Tesla and A_e (the area of the core) is 100 mm^2

Hence the primary turns (N_p) will be 60 turns.

The primary inductance can be calculated as follows; Assuming 100% efficiency at a power of 100W and an input voltage of 100V the time averaged input current will be this example). From inspection of the top part of **Fig. 2**, the primary current change is from 1.5A to 2.5A, a ΔI of 1A. The ON period is $10\mu s$, and we can now calculate

The primary inductance

This will be $1000\ \mu H$. (See **Equations**)

While the OFF (flyback) period of Q1 is also $10\mu s$, the secondary volts per turn during the flyback period will be the same as the primary volts per turn during the ON pe transformer like ratio won't apply, and you must obtain the secondary turns from the calculated secondary inductance, in the same way as it was in the discontinuous m

The secondary current ratio follows the turns ratio, since the primary ampere turns product must be maintained. Thus, $I_s = I_p \times 60/12$. As shown in **Figs. 2** and **3**, the average at 20V and power equality is maintained.

The "transformer" is now wound using a wire size for the 60 turns primary that will use less than 50% of the bobbin area to allow for insulation. The remaining space is no direct transformer action (because the primary and secondary aren't conducting at the same time), the leakage inductance should still be minimized. As Q1 turns OF commutation and will produce a voltage overshoot on the primary when Q1 turns OFF. Hence, the windings would normally be interleaved — 1/2 primary, secondary and 1 However, it can also be calculated. (See **Equations**.)

The main advantage of the continuous mode is reduced ripple current. The disadvantages are that the "transformer" must support a dc current component, the output d plane zero" in the transfer function leading to poor transient response. However, the reduced ripple current, makes this mode more suitable for higher power application

The mode of operation was defined by adjusting the inductance, (by using a smaller air gap). Low inductance (large air gap) leads to the discontinuous mode, while larg gap, or a combination of these.

For multiple outputs, sum the total output power and use this value in the equations when calculating the primary and secondary inductance of the main controlled outp

Although we've ignored the transformer action, as it's not a design parameter, it still exists. The flyback voltage is reflected back to the primary winding during the OFF |

The following equations are dimensionally modified to yield convenient answers.

Equations

Primary Turns

Where:

N_p = Primary Turns

V_p = Primary Voltage

t = Q1 ON time (μs)

ΔB = Peak flux density (tesla)

A_e = effective area of center pole (mm^2)

Primary Inductance Where:

L_p = Primary inductance (μH)

Δt = Q1 ON time (μs)

ΔI_p = Current change I_1 to I_2 (A)

Inductance Factor

Where:

A_L = Inductance of a single turn (μH)

Secondary Inductance $L_S = N_S^2 \times A_L$

Where:

L_S = Secondary inductance (μH)

N_S = Secondary turns

Secondary Turns

Air Gap Length

Where:

Air gap = (mm)

$\mu_0 = 4 \pi \times 10^{-7}$

N_p = Primary turns

A_e = Area of core(mm^2)

L_p = Primary inductance (mH)

a = Air Gap (mm)

ac Flux Density

dc Flux Density

where a = Air Gap (mm)

In the next Power Design column, we'll cover a transformer design for a forward converter, including alternative core materials.

Keith Billings is president of DKB Power Inc. (dkbp@rogers.com) and author of the Switchmode Power Supply Handbook published by McGraw Hill ISBN 0-07-006719-8.

References

1. Switchmode Power Supply Handbook. Keith Billings, Published by McGraw Hill ISBN 0-07-006719-8.
2. Switching Power Supply Design. Abe Pressman, Published by McGraw Hill ISBN 0-07-052236-7.

For more information on this article, CIRCLE 339 on Reader Service Card

<p>Transformer Manufacturer We build custom designed power transformers from 1 KVA to 500 KVA www.lcmagnetics.com</p>
<p>Transformer Complete Transformer Systems Experts In Electrical Loads & More! www.solaheviduty.com</p>
<p>Linear Technology DC/DC Step-up, step-down, buck-boost and inverting topologies. www.linear.com</p>
<p>Transformer Manufacturer We build custom designed power transformers from 1 KVA to 500 KVA www.lcmagnetics.com</p>
<p>Transformer Complete Transformer Systems Experts In Electrical Loads & More! www.solaheviduty.com</p>
<p>Linear Technology DC/DC Step-up, step-down, buck-boost and inverting topologies. www.linear.com</p>

Back to Top

TOPIC INDEX

Discrete Semis
Bipolar Transistors
IGBTs
Power Modules
Power MOSFETs
Rectifiers/Diodes
Thyristors

Power Management
Digital Power Control

Portable Power Management
Batteries
Battery Charger ICs
Fuel Gauges Controllers and Regulators
Micro Fuel Cells

Passives/Packaging
Capacitors
Circuit Protection Devices
Connectors

Thermal Management
Fans
Heatpipes & Spreaders
Heatsinks
Liquid Cooling
Thermal Interface Materials
Thermal Management Simulation

Power Systems
DC-DC Converters

[High-Voltage Devices](#)
[LED Drivers](#)
[Lighting Power Management](#)
[Motor Power Management](#)
[Power ICs](#)
[PWM Controllers](#)
[Regulator ICs](#)

[Magnetics](#)
[Packaging](#)
[Printed Circuit Boards](#)
[Resistors](#)
[Sensors & Transducers](#)
[Switches & Electromagnetic Relays](#)

Topic Pages
[Wind Power](#)
[Flyback Transformers](#)

[Distributed Power Architectures](#)
[EMI & EMC](#)
[Linear Power Supplies](#)
[Safety/Environmental Approvals](#)
[Simulation/Modeling](#)
[Switch-Mode Power Supplies](#)
[Test & Measurement Uninterruptible Power Supplies](#)

[Digital Power](#)
[Commentaries](#)
[Digital Power News](#)
[Digital Power Products](#)
[Design Features](#)

[Contact Us](#) [For Advertisers](#) [For Search Partners](#) [Privacy Policy](#) [Subscribe](#)
© 2007 Penton Media, Inc. All rights reserved.