



Webcasts. Application Notes. Tutorials. Design Tools.



PartFinder™ by  
GLOBALSPEC

57075 Pressure Regulators  
165 Search Over  
30 Million Parts.

FIND:

Search Part Numbers

Google Search

Web  DiscoverCircuits.com



DiscoverCircuits.com, has **30,000+** electronic circuits, cross-referenced into 500+ categories. We have searched the web to help you find quick design ideas. We make every effort to link to material posted by the designer. Please let us if you would like us to link to or post your design.

HOME

Schematics

Discover Forum

Hobby Corner

Dave's Circuits

Electronic Resources

Book Corner

Contact Info

Imagining Ezine

[Discover Solar Energy](#)

Dave Johnson & Associates

Faraday Touch Switches

## Circuit Solutions Notebook

Last Updated On: Saturday October 23, 2010

[DC/DC Converter](#) Custom and Standard DC/DC solutions Specification and Selection Guide [www.calex.com](http://www.calex.com)

[Power Supply Circuit Diagram](#) Easy to Use! Design and Prototype Your Power Supply within Minutes [National.com/WEB](http://National.com/WEB)

[Lineage Power®](#) AC-DC Custom Power Supplies 80PLUS® Platinum Total Efficiency™ [www.lineagepower.com](http://www.lineagepower.com)

Ads by Google

[Latest Technical Challenge](#)

[Previous Circuits Solutions](#)

[Circuit Solutions in Progress](#)


## Non-Isolated Off-Line AC to DC Power Supply


### Challenge:

Is it possible to design a circuit that can efficiently produce say 6 volts at a couple watts, without the use of a transformer or switching regulator? The circuit would not have to be isolated from the power line. Also, can the circuit be designed to fit inside a one square inch circuit board area?
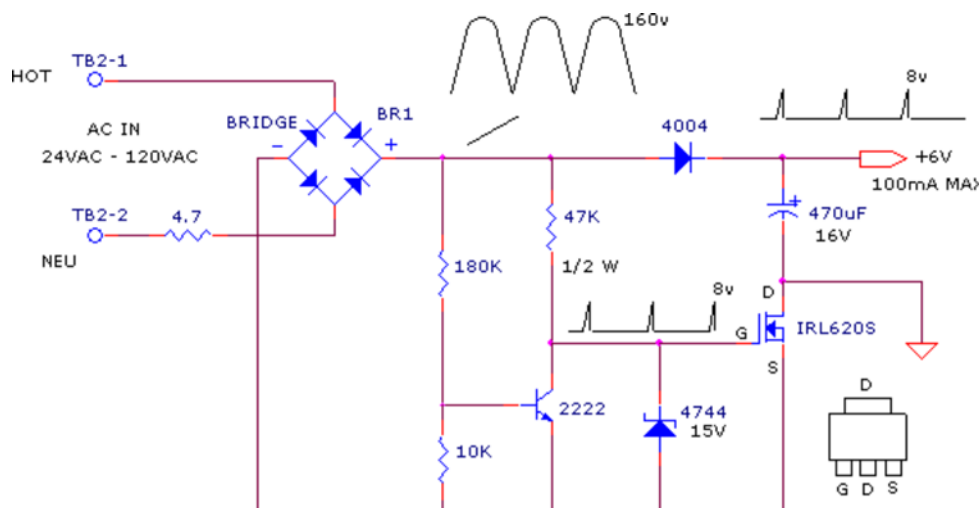
### Solution:

The design below does indeed fit within a one square inch circuit board area. It can be used over a wide 24vac – 120vac input voltage. The circuit gates only small slivers of the rectified AC signal to a 470uF energy storage capacitor. The 180K and the 10K resistors define the peak voltage fed to the capacitor. Other resistor values can be used to shift the DC output voltage up or down. Remember, this circuit should only be used with DC circuits that can be connected directly to the power line. Dangerous voltages exist everywhere.



 

**Industry's First SuperSpeed USB (3.0) Transceiver**

- Receiver sensitivity of < 50mV differential peak-to-peak
- Integrated spread-spectrum clocking reduces BOM costs
- Enables USB 3.0 end-to-end

**Order samples now**



[HOME](#)   [Schematics](#)   [Discover Forum](#)   [Hobby Corner](#)   [Dave's Circuits](#)   [Electronic Resources](#)   [Book Corner](#)   [Contact Info](#)  
[Discover Solar Energy](#)   [Imagineering Ezine](#)   [Dave Johnson & Associates](#)   [Faraday Touch Switches](#)

*Linking is welcomed but **COPYING** any content or graphics to your web site is expressly prohibited.*

[About Us](#) | [Advertise on DiscoverCircuits.com](#) | [Report Broken Links](#) | [Link to DiscoverCircuits.com](#) | [Privacy Policy](#)