

Variable power supply with zener stabilization

In regulated power supplies it is advantageous to feed the reference zener diode from the stabilized line. This is more difficult with a variable voltage supply; however, a simple solution to

the problem is to use a dual linear potentiometer as in the circuit shown.

L. J. Baughan,
Charlbury,
Oxon.

