

Figure 2. The circuit diagram: a voltage quad comparator with open-collector outputs and three discrete transistors are the active components on which the voltage source is based.


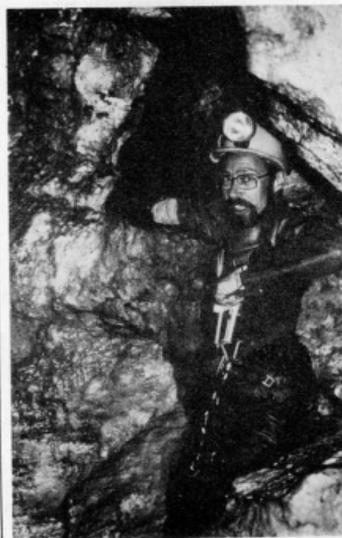


figure 2). One stage of the LM 339, A2, in conjunction with transistor T1, forms a voltage reference source for pulse-width controls A1 and A3. The voltage source is formed by diode D1 to which the output of T1 is applied via R3. The reference voltage is set by P1. For a supply voltage, U_b , of 10 volts, the reference voltage, U_r , can be preset between 1.0 and 3.0 V by P1.

The two pulse-width controls (PWCs) operate at frequencies of about 1.2 kHz and 3.6 kHz respectively. The frequency separation is necessary to prevent (visible) interference between their output signals. The outputs of A1 and A3 are fed to the non-inverting input of A4 via R10 and R16. Opamp A4 is connected as an AND gate so that its output is only '1' if both A1 and A3 have a '1' at their output.

The circuit terminates in an economical output amplifier based on transistors T2 and T3. Power transistor T3 is a type BD 437 which has a low collector/emitter saturation voltage.

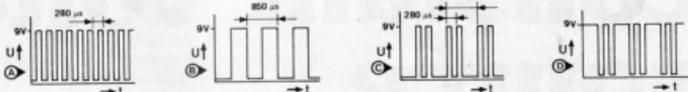With values shown in figure 2, the constant-voltage source is suitable for lamps of 3.5 ... 6.3 V consuming not more than 1 A. A graph of the efficiency, η , of various



Some arithmetic

In the following,

U_b = battery voltage

U_e = effective value of pulse voltage

D = duty factor of BOTH pulse-width controls

P = power supplied to lamp

R = resistance of lamp

The duty factor, D , is inversely proportional to U_b

Each PWC delivers a (pulse) voltage of which

$U_e = U_b \sqrt{D}$

Multiplier A4, an AND gate which only recognizes logic levels, multiplies pulse-widths but NOT voltages: its output is, therefore

$U = U_b \sqrt{D} \sqrt{D} = U_b D$

The power supplied to the lamp is therefore

$P = U_b^2 D^2 / R$

As both U_b and D are expressed as second-order quantities which are inversely proportional, and R is constant, it is evident that P is independent of U_b .

lamps versus U_b is given in figure 3. The circuit is suitable for use with input voltages, U_b , of 3.5 . . . 15 V. The average current consumed is about 15 mA.

Calibration

Calibrating the voltage source is fairly simple. Connect a suitable lamp to the lamp terminals and a variable, stabilized power supply to the battery terminals. Set the output of the power supply to the nominal voltage of the lamp used.

3

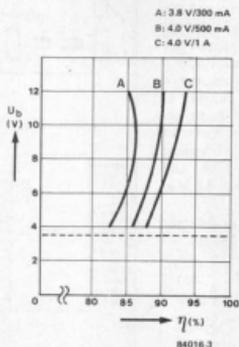


Figure 3. Characteristics showing the efficiency of three different lamps versus the battery voltage: the efficiency rises with larger lamp currents.

Connect an oscilloscope to pin 2 of IC1 and adjust PI until A1 just commences to oscillate.

If no instruments other than a multimeter are available, the voltage source may be calibrated as follows. Connect a suitable lamp to the lamp terminals, and the multimeter (resistance range) between pin 6 of IC1 and the junction of PI-R1. Adjust PI for minimum resistance. Remove the multimeter and connect a suitable battery to the battery terminals. Adjust PI for good brightness of the lamp.