

## REDUCED RIPPLE AT LOW CURRENT

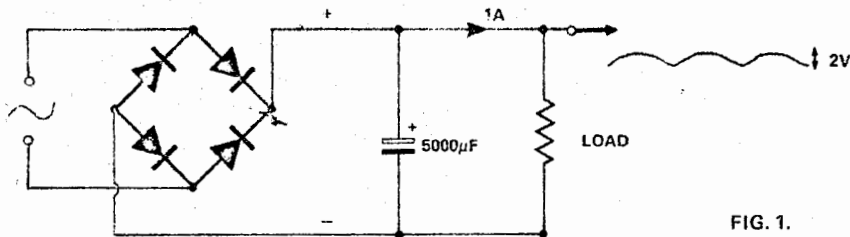


FIG. 1.

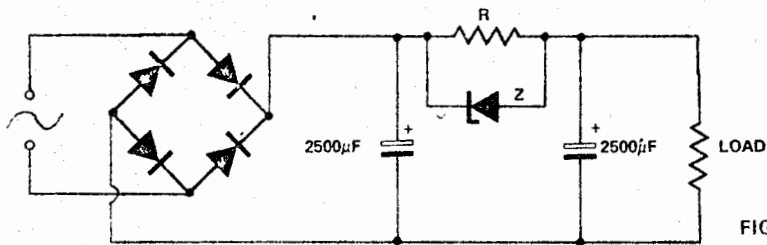


FIG. 2.

In the normal circuit (Fig. 1) the ripple at 1 amp is at least 2 volts. Cheap power amps use this circuit (with low supply ripple rejection) and produce annoying amounts of hum at low signal levels.

In the circuit in Fig. 2 the ripple is considerably reduced at low levels and

at high currents the supply voltage is only minimally affected.

Maximum low ripple current ( $I_m$ ) =  $V_z/R$  where  $P_{tot}$  R must be more than  $V_z^2/R = I_m V_z$ .  $I_M$  = maximum total current so  $P_{tot} = I_M I_m V_z$ . A typical set of values for  $I_m = \frac{1}{2}$  Amp' is  $V_z = 3V$ ,  $R = 1\frac{1}{2}$  ohms.