

# DESIGN SHOWCASE

## Micropower Circuit Monitors Positive Supply Current


The inexpensive circuit of **Figure 1** converts the load current of a positive power supply to a ground-referenced signal voltage, without recourse to the instrumentation amplifier, extra power supply, and matched sets of resistors typical of such circuits. The output current  $I_O$  (proportional to supply current) flows through  $R_O$  to produce  $V_O$ . Because  $I_O$  is generated by a true current source, you can reference  $V_O$  to ground or to any reasonable level within the supply range. The measurement is independent of variations in the supply voltage.

Because the op amp's common-mode range includes the supply rails, it can sense small voltages near the positive rail, such as those across  $R_S$ . Feedback resistor  $R_F$  should equal  $100R_S$  or  $1000R_S$ . The op amp drives P-channel MOSFET  $Q_1$ , whose drain-source current produces a voltage across  $R_F$  equal to that across  $R_S$ , subject to an error of  $\pm V_{OS}$ . As a result,

$$I_O = (I_L R_S \pm V_{OS}) / R_F, \text{ and}$$

$$V_O = (I_L R_S \pm V_{OS}) (R_O / R_F).$$

The component values shown provide a  $V_O$  range of 0 to 1V for the supply-current range 0 to 1A. You can add a trimming potentiometer to null  $V_{OS}$ . The remaining gain error depends on the tolerance of  $R_S$ ,  $R_F$ , and  $R_O$ , and you can set this error to zero by trimming  $R_F$  or  $R_O$ . The op amp draws  $20\mu\text{A}$  and operates with a voltage as low as 2.5V. This op amp supply is produced by the five diodes, which are biased by  $R_Z$  and the input supply voltage as shown in the table.

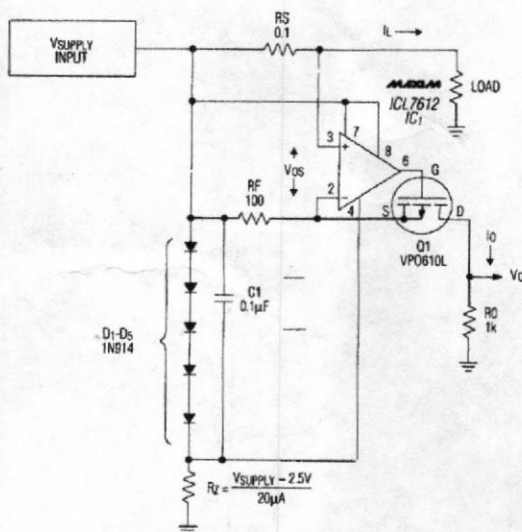

$V_{SUPPLY}$	$R_Z$
+5V	120k
+9V	320k
+12V	470k
+24V	1.1m
+48V	2.2m

$$V_O = (I_L R_S \pm V_{OS}) \times \frac{R_O}{R_F}$$

$$I_O = (I_L R_S \pm V_{OS}) \times \frac{1}{R_F}$$

**Figure 1.** This simple load-current monitor produces a proportional signal voltage  $V_O$ .

(Circle 4)