

# Resistor snipping trims regulator voltage to within 1%

by Robert A. Pease  
National Semiconductor Corp., Santa Clara, Calif.

Five low-cost resistors are used in this production-line technique for setting the output voltage of a three-terminal regulator to within  $\pm 1\%$  of the desired output voltage. Thus, expensive and often unreliable potentiometers can be eliminated by this iterative trimming procedure, which removes up to three resistors until the output voltage is within tolerance.

In a typical three-terminal adjustable regulator such as the LM117 (a), the output voltage will be:

$$V_{out} = V_{REF}(R_2/R_1 + 1) + R_2 I_{ADJ}$$

where  $V_{REF}$  is nominally 1.25 volts,  $R_1$  and  $R_2$  are the regulator's external voltage-programming resistors, and  $I_{ADJ}$  is 100 microamperes maximum. Generally,  $V_{REF}$  will vary less than  $\pm 3\%$  under normal operating conditions; if  $R_1$  and  $R_2$  each have a tolerance of  $\pm 1\%$ , the regulator's overall accuracy then becomes  $\pm 5\%$ .

The standard method for attaining a 1% tolerance is to substitute a trimming potentiometer,  $R_T$ , and some fixed resistor,  $R_F$ , for  $R_2$ , where in general  $R_{Tmax} + R_F$  will exceed the value of  $R_2$  previously used by a factor of 10% or so. But this scheme may be superseded with the circuit shown in (b) to avoid the disadvantages of using a trimming potentiometer, one of which is a tendency to misadjust it sooner or later.

In this particular case, a 22-v output voltage is sought for a 28-v source input. When first measured,  $V_{out}$  will be 4% to 6% higher than the 22v target no matter what conditions exist within the regulator, because the effective value of  $R_1$  is lowered (see equation).  $R_3$ ,  $R_4$ , and  $R_5$  are selected so that one or more may be systematically removed to bring  $V_{out}$  within limits.

The method is as follows:

- If  $V_{out} \geq 23.08$ , cut out  $R_3$ .
- If  $V_{out}$  is or then becomes  $\geq 22.47$ , cut out  $R_4$ .
- If  $V_{out}$  becomes  $\geq 22.16$ , cut out  $R_5$ .


Note that the values of  $R_3$ ,  $R_4$ , and  $R_5$  are independent of the output voltage desired; it is only necessary to select a new value of  $R_2$  so that  $V_{REF}(R_2/R_1 + 1)$  is a few percent below the desired output voltage, assuming a  $V_{REF}$  of 1.25. In practice, this means selecting  $R_2$  to be proportional to the output voltage desired.

An alternative trimming scheme is shown in (c), whereby  $R_3$ ,  $R_4$ , and  $R_5$ , placed in the  $R_2$  line, are initially shorted by jumpers. Here  $V_{out}$  is initially lower than the target value and never exceeds that voltage during trimming.

In this procedure:

- If  $V_{out} \leq 20.90$ , snip link 1.
- If  $V_{out}$  is or becomes  $\leq 21.55$ , snip link 2.
- If  $V_{out}$  is or becomes  $\leq 21.82$ , snip link 3.

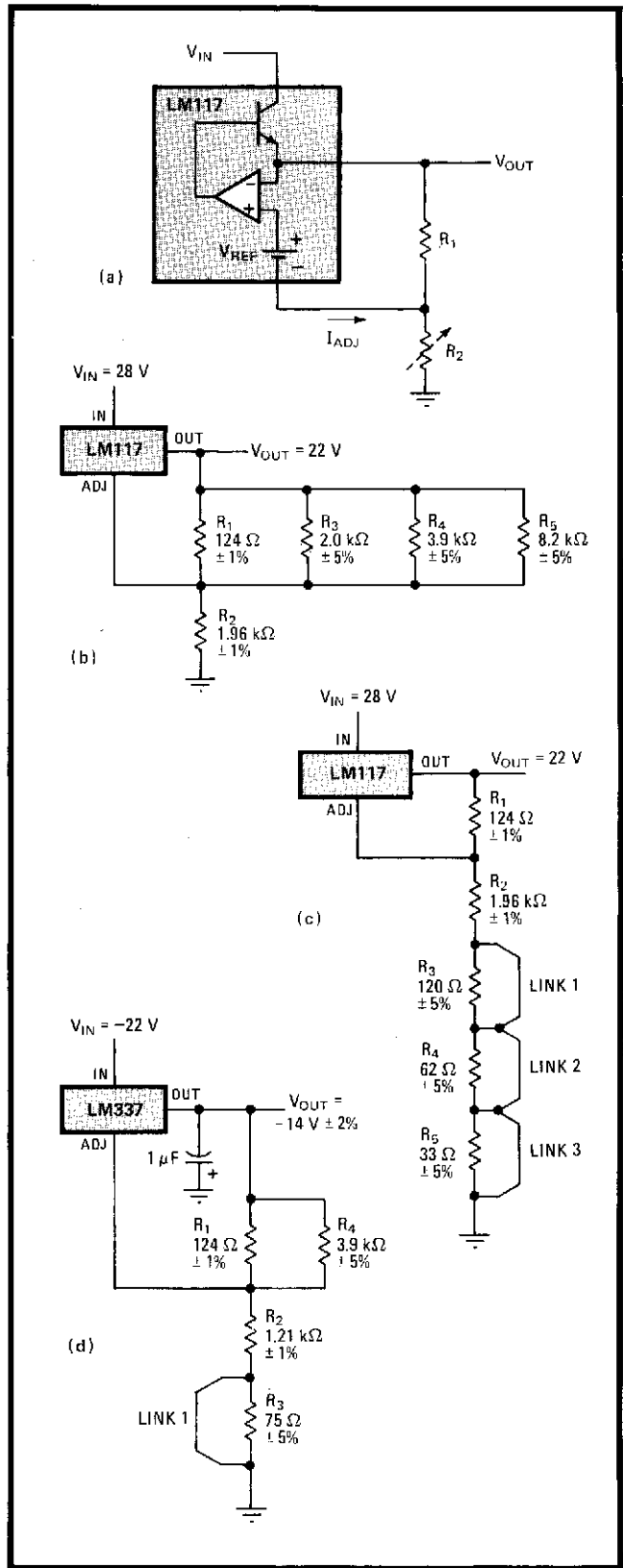When the output voltage is other than 22,  $R_3$ - $R_5$  need to be chosen in the same proportion to  $R_2$ . Thus if the



**Tolerance.** Programmable regulator's trimmer (a), which is costly and may drift, may be replaced with low-cost, fixed resistor network  $R_3$ - $R_5$  (b) for production-line trimming. Each resistor is systematically removed to bring  $V_{out}$  to within 1% of desired value. Alternate scheme uses resistors in series (c). If 2% tolerance is acceptable, one less resistor (d) and simplified procedure accomplishes task.

scheme in (c) is used for  $V_{out} = 12$ , then  $R_2 = 1.0$  k $\Omega$ ,  $R_3 = 62\Omega$ ,  $R_4 = 31\Omega$ , and  $R_5 = 16\Omega$ . Note too that when approach (b) is used, some care must be taken that all the snipped resistors be removed without shorting anything out. If (c) is used, one end of the cut link should be curled back to prevent shorting.

If 2% tolerance is acceptable, the circuit in (d) will provide trimming with one less resistor and fewer itera-

tions. In this instance, the configuration is shown for the LM337 negative-voltage regulator, where the desired  $V_{out} = -14$  v. If the magnitude of  $V_{out} \leq 13.75$  v, link 1 is snipped. Then if  $V_{out} \geq 14.20$  v,  $R_4$  is cut out.

In most cases, no trimming at all will be required, because most  $\pm 1\%$  resistors are well within a tolerance of  $\pm 1/2\%$ , and most often the LM337's  $V_{ref}$  term is within  $1 1/2\%$  of its nominal value. □