

# MC44603 in a 110 W Output SMPS Application (80-140 Vrms and 180-280 Vrms Mains Voltages)

by Joël Turchi  
Power Management Products Operation  
Application Laboratory, Motorola, Toulouse, France

The purpose of this application note is to present a way of designing the MC44603 in a fly-back dedicated to a 110 W output power supply in two distinct cases: 110 Vrms mains and 220 Vrms mains.

For this range of power, the discontinuous mode must be chosen as it limits the stress on the power switch and the output diodes. This kind of working can be guaranteed, thanks to the demagnetization arrangement of the MC44603.

This application note considers both high and low mains voltages.

- In the high voltage a.c. line case, it deals with both MOSFET and BIPOLAR transistor use.
- In the low mains voltage case, only the MOSFET solution is considered as the inductor peak current is high.

The MC44603 is a high flexibility SMPS controller. It offers a wide variety of protection (accurate maximum current limitation, Vcc overvoltage detection, fold-back, demagnetization, soft start).

In addition, distinct working modes can be used with this circuit:

- **a fixed frequency working mode**  
Here, the frequency is given by the circuit oscillator.
- **a variable frequency working mode**  
This kind of working can be obtained when the chosen oscillator period is shorter than the cycle time for transformer magnetization and complete demagnetization.
- **a stand-by mode**  
This reduces the working frequency during this phase. This method reduces the stand-by losses that are mainly proportional to the switching frequency, and avoids the unstable very high frequency working that is generally associated with traditional free frequency systems.

In the MC44603 design proposed here, the variable frequency mode is not used. Indeed, as shown later, the fixed frequency mode enables a more accurate control of the power that is drawn from the mains.

## I — THE APPLICATIONS

OUTPUT: 110 W

In the following calculations, the maximum input power will be considered equal to 135 W ( $\eta \approx 80\%$ ).

Application 1: 110 V mains 80 Vrms  $\leftrightarrow$  140 Vrms

Application 2: European mains 180 Vrms  $\leftrightarrow$  280 Vrms

The outputs:	120 V	0.5 A
	28 V	1.0 A
	15 V	1.0 A
	8 V	1.0 A

## Consequences for the Transformer

This output voltage values are obtained using four secondary windings of the transformer. Now, as a diode is located between the output capacitor and the winding, this diode voltage must be taken into account in the choice of the number of turns of each of the windings.

So, if the diode voltage is considered equal to 1 V, the desired voltages on the windings are nearly:

121 V
29 V
16 V
9 V

To obtain the output voltage values of the specification with a good accuracy, we need at least 3 turns for the 9 V and then:

9 V	3 turns
16 V	5 turns
29 V	10 turns
121 V	40 turns

This solution seems to be correct, since with three turns, the 9 V should be well coupled; also, 40 turns (for the 120 V) is not too large a value (no ferrite saturation).

In our application, in order to obtain a very well regulated high voltage output, an opto coupler is used. By this means, the regulation uses feedback drawn from the 120 V output.

## II — GENERAL DESIGN EQUATIONS

### Calculation of the Main SMPS Parameters

#### II-1 — Fixed frequency working mode:

To obtain a fixed frequency discontinuous working mode (the discontinuous mode is guaranteed by the demagnetization section), the transformer primary inductor magnetization and demagnetization cycle must be shorter than the oscillator period (that is the chosen working period) for any working point.

This condition can be expressed by the following inequality:

$$T_{on} + T_{off} \leq T_{osc} \quad (\text{ineq 1})$$

## AN1669

where:  $T_{on}$  is the on-time,  $T_{off}$  is the off-time  
 $T_{osc}$  is the MC44603 oscillator period

The current increases linearly during the on-time and decreases linearly in the inductor for the off-time.

$$\text{So, } I_{pk} = \frac{V_{in}}{L} \times T_{on} \quad (\text{eqn 1})$$

$$\text{and, } I_{pk} = \frac{N V_o}{L} \times T_{off} \quad (\text{eqn 2})$$

where:  $I_{pk}$  is the primary inductor peak current  
 $V_{in}$  is the rectified a.c. line voltage (fly-back input voltage)  
 $L$  is the primary inductor value  
 $N V_o$  is the output voltage considered in the primary side  
 $(N)$ : turn ratio

$$\text{So, } T_{on} + T_{off} = L \times I_{pk} \times \frac{V_{in} + N V_o}{V_{in} \times N V_o} \quad (\text{eqn 3})$$

In addition, the energy drawn through the transformer during one cycle is:

$$E = \frac{1}{2} \times L \times I_{pk}^2 \quad (\text{eqn 4})$$

So,  $P_{in}$  (input power) is:

$$P_{in} = \frac{1}{2} \times L \times I_{pk}^2 \times f_{osc} \quad (\text{eqn 5})$$

where  $f_{osc}$  is the MC44603 oscillator frequency

Using equations 3 and 5 and inequality 1,

**condition required to work in a fixed frequency mode:**

$$L \times f_{osc} \leq \frac{1}{2 \times P_{in}} \times \left( \frac{V_{in} \times N V_o}{V_{in} + N V_o} \right)^2 \quad (\text{ineq 2})$$

### II-2 — Peak inductor current expression

$P_{in}$  is given by the following expression:

$$P_{in} = V_{in} \times I_{in} \quad (\text{eqn 6})$$

where  $I_{in}$  is the input current

$$\text{and } I_{in} = \frac{1}{2} \times I_{pk} \times d \quad (\text{eqn 7})$$

where  $d$  is the duty cycle

$$\text{Now, } T_{on} = d \times T_{osc} \quad (\text{eqn 8})$$

Using equations 1, 7 and 8:

$$I_{in} = \frac{1}{2} \times L \times I_{pk}^2 \times \frac{f_{osc}}{V_{in}} \quad (\text{eqn 9})$$

Using equations 6 and 9:

$$I_{pk} = \sqrt{\frac{2 \times P_{in}}{L \times f_{osc}}} \quad (\text{eqn 10})$$

Thus, Peak inductor current:

$$(I_{pk})_{max} = \sqrt{\frac{2 \times (P_{in})_{max}}{L \times f_{osc}}} \quad (\text{eqn 11})$$

### II-3 — Power switch on-time losses

#### II-3-1 — MOSFET:

$R_{dson}$  being the MOSFET on-time resistor, the on-time losses can be calculated from:

$$P_{on} = \left( \frac{1}{T_{osc}} \right) \times \int_0^{T_{on}} R_{dson} \times I_T^2 \times dt \quad (\text{eqn 12})$$

where  $I_T$  is the MOSFET current.

$$\text{So, as: } I_T = V_{in} \times \frac{t}{L} \quad (\text{eqn 13})$$

$$P_{on} = \frac{1}{3} \times R_{dson} \times V_{in}^2 \times \frac{T_{on}^3}{(T_{osc} \times L^2)} \quad (\text{eqn 14})$$

Consequently, using equations 1, 5 and 14, the following expression can be written:

$$P_{on} = \frac{2 \times \sqrt{2}}{3} \times R_{dson} \times \frac{P_{in}}{V_{in}} \times \sqrt{\frac{P_{in}}{L \times f_{osc}}} \quad (\text{eqn 15})$$

Consequently,

#### **maximum MOSFET on-time losses**

(eqn 16)

$$(P_{on})_{max} = \frac{2 \times \sqrt{2}}{3} \times R_{dson} \times \frac{(P_{in})_{max}}{(V_{in})_{min}} \times \sqrt{\frac{(P_{in})_{max}}{L \times f_{osc}}}$$

Using the  $(I_{pk})_{max}$  value, the following equation could also be written:

$$(P_{on})_{max} = \frac{1}{3} \times R_{dson} \times (I_{pk})_{max}^2 \times d_{max}$$

where  $d_{max}$  is the maximum duty cycle.

#### II-3-2 — BIPOLAR TRANSISTOR

$$P_{on} = \frac{1}{T_{osc}} \times \int_0^{T_{on}} V_{CE} \times I_T \times dt \quad (\text{eqn 17})$$

$$\text{So: } P_{on} = V_{CE} \times \langle I_T \rangle \quad (\text{eqn 18})$$

$$\text{Thus: } P_{on} = V_{CE} \times I_{in} \quad (\text{eqn 19})$$

where  $I_{in}$  is the input current

$$\text{So: } P_{on} = V_{CE} \times \frac{P_{in}}{V_{in}} \quad (\text{eqn 20})$$

Consequently,

#### **maximum BIPOLAR transistor on-time losses**

$$(P_{on})_{max} = V_{CE} \times \frac{(P_{in})_{max}}{(V_{in})_{min}} \quad (\text{eqn 21})$$

### II-4 — Maximum duty cycle

$$\text{The duty cycle, } d, \text{ is equal to: } d = \frac{T_{on}}{T_{osc}} \quad (\text{eqn 22})$$

Now, 
$$T_{on} = L \times \frac{I_{pk}}{V_{in}} \quad (\text{eqn 23})$$

so, 
$$d = L \times f_{osc} \times \frac{I_{pk}}{V_{in}} \quad (\text{eqn 24})$$

Thus, using equation 10:

$$d = \sqrt{2 \times P_{in} \times L \times \frac{f_{osc}}{V_{in}^2}} \quad (\text{eqn 25})$$

So, **maximum duty cycle:**

$$d_{max} = \sqrt{2 \times (P_{in})_{max} \times L \times \frac{f_{osc}}{(V_{in})_{min}^2}} \quad (\text{eqn 26})$$

## II-5 — Other design parameters

The other parameters that must be taken into account are:

**$(V_T)_{max}$ : the maximum voltage the power switch must face:**

$$(V_T)_{max} = (\sqrt{2} \times (V_{in})_{max}) + (N \times 120) \quad (\text{V}) \quad (\text{eqn 27})$$

where:  $(V_{in})_{max}$  is the maximum rms a.c. line voltage (140 V or 280 V according to the line)

120 is the maximum output voltage

N is the transformer turn ratio between the 120 V output winding and the primary inductor

**$(V_D)_{max}$ : the maximum voltage the 120 V output diode must face:**

$$(V_D)_{max} = \left( \sqrt{2} \times \frac{(V_{in})_{max}}{N} \right) + 120 \quad (\text{V}) \quad (\text{eqn 28})$$

**$(ni)$ : the transformer ferrite saturation parameter**

To avoid any risk of saturation in the transformer, the inductor peak current must be lower than  $(n_i/n_p)$ , where  $n_p$  is the turns number of the primary inductor.

Now, 
$$n_p = N \times n_{120V} \quad (\text{eqn 29})$$

where  $n_{120V}$  is the turns number of the 120 V winding

So, 
$$n_i = N \times n_{120V} \times I_{pk} \quad (\text{eqn 30})$$

These parameters are the main elements that have to be taken into account as they allow you to choose the power switch, the diodes, the transformer and the working frequency.

As shown by the preceding calculations, the design parameters depend on some elements like N or the value of  $(f_{osc} \times L)$ .

## SUMMARY

Condition Required to Work in a Fixed Frequency Mode	$L \times f_{osc} \leq \frac{1}{2 \times P_{in}} \times \left( \frac{V_{in} \times NV_o}{V_{in} + NV_o} \right)^2$
Maximum Peak Inductor Current	$(I_{pk})_{max} = \sqrt{\frac{2 \times (P_{in})_{max}}{L \times f_{osc}}}$
Maximum Power Mosfet On-Time Losses	$(P_{on})_{max} = \frac{1}{3} \times R_{dson} \times (I_{pk})_{max}^2 \times d_{max}$
Maximum Bipolar Transistor On-Time Losses	$(P_{on})_{max} = V_{CE} \times \frac{(P_{in})_{max}}{(V_{in})_{min}}$
Maximum Duty Cycle	$d_{max} = \sqrt{2 \times (P_{in})_{max} \times L \times \frac{f_{osc}}{(V_{in})_{min}^2}}$

# AN1669

## III — APPLICATION 1: 110 V INPUT

### III-1 — Choice of the transformer

One way to use the above design equations, consists of drawing up a table showing how the main SMPS parameters vary with the value of the turn ratio.

To calculate these values, it is necessary to know the input power level. This value is taken equal to (135W) in our application (135W corresponds to an efficiency equal to about 80%). The application results will show that this assumption ensures a desirable margin with the nominal input voltage).

On the other hand, the parameters calculation shows that  $(L \times f_{osc})_{max}$  is the  $(L \times f_{osc})$  value that results in the lowest  $(I_{pk})_{max}$  and  $(P_{on})_{max}$  ones (refer to  $I_{pk}$  or  $P_{on}$  expressions). This  $(L \times f_{osc})$  value is the maximum one that guarantees a fixed frequency working for any working point (refer to section II-1). The SMPS parameters given in the following table are calculated using this threshold value.

#### Choice criteria and definition of the transformer:

As shown by the following table, the higher the turn ratio (N) is, the lower the peak current is. Now, the  $(ni)_{max}$  is proportional to N and the voltage the transistor must face, increases when N rises. That is why an optimal N value must be chosen.

In fact, there are three main choice criteria:

- the peak current and the on-time losses.  
N must be as large as possible in order to reduce the peak current and the on-time losses
- the voltage the power MOSFET must face.  
Indeed, this voltage must be as low as possible to reduce its cost and in order to decrease the  $R_{dson}$ . That is why a MOSFET 400 V should be used. It is necessary to have a safety voltage margin, to avoid the need to incorporate a lossy and costly clamping network

that would cut the voltage spikes due to the leakage inductor (refer to Figure 1). Consequently, N must be chosen lower than 1.25 ( $V_{Tmax} = 350$  V).

- the transformer must be well coupled.  
This is to obtain a consistently accurate regulation of the output and to reduce the leakage inductor and hence the turning off spikes (refer to Figure 1). That is why a low air-gap ferrite must be used. Practically, a ferrite whose  $(ni)$  is lower than 200 A.turns, seems to be a good choice. So, N must be lower than 1. (The appendix gives details of OREGA transformers; the SMT4 suits our application).

Finally, in order to use a ferrite ( $ni = 180$ ,  $A_L = 250$  nH/turns<sup>2</sup>),  $(N = 0.75)$  seems to be a suitable value.

Indeed, this value should result in a well coupled transformer with a low leakage inductor value. On the other hand, if we do not take into account the turning off spikes, then the theoretical highest value the power MOSFET must face, is 290 V. Consequently, with a 400 V power switch, only a low loss clamping arrangement is required.

The chosen MOSFET, is the MTP10N40E ( $R_{dson} = 0.55$   $\Omega$ , 400 V).

Consequently,

$$L_p = A_L \times (N \times 40)^2 \longrightarrow L_p \approx 225 \mu H$$

and the optimal working frequency is:

$$L_p \times f_{osc} \leq 9.3 \longrightarrow f_{osc} \leq 41.3 \text{ kHz}$$

So, the following values can be chosen:

$$\begin{aligned} L_p &= 225 \mu H \\ f_{osc} &\approx 40 \text{ kHz} \quad (R_{ref} = 10 \text{ k}\Omega, C_T = 1 \text{ nF}) \end{aligned}$$

and then:  $I_{pk} \approx 5.4$ A

N	$(L \cdot f_{osc})_{max}$	$(I_{pk})_{max}$ (A)	$(V_T)_{max}$ (V)	$(V_D)_{max}$ (V)	MOSFET on losses/ $R_{dson}$ (W/ $\Omega$ )	$(ni)_{max}$
0.50	5.6	6.9	260	520	5.7	139
0.75	9.3	5.4	290	390	4.3	162
0.90	11.0	5.0	300	340	4.1	180
1.00	12.5	4.6	320	320	3.7	184
1.25	14.9	4.3	350	280	3.5	215
1.50	17.3	4.0	380	250	3.2	240
2.00	21.9	3.5	440	220	2.8	281

NOTE: N: turn ratio (refer to II-5)  
 $(V_T)_{max}$ : maximum voltage the power switch must face  
 $(V_D)_{max}$ : maximum voltage the 120 V output diode must face

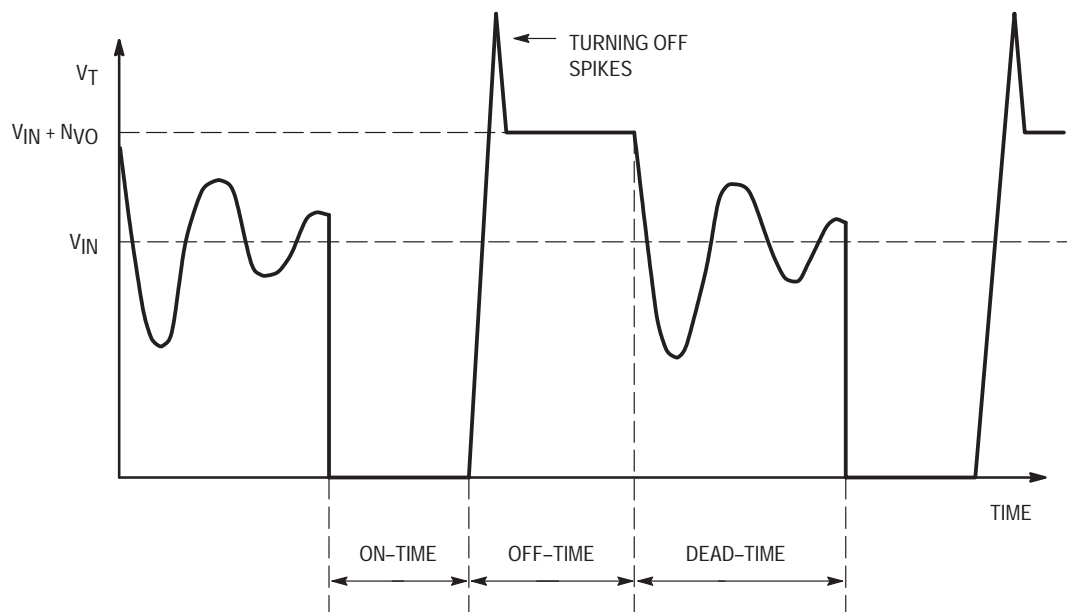


Figure 1. Voltage Spikes Due to the Leakage Inductor

### III-2 — MC44603 pins use: (refer to the application schematics)

#### 1 — $V_{CC}$ (PIN 1):

The pin  $V_{CC}$  must be connected to a transformer auxiliary winding. This extra winding turns number can be taken equal to 5 in order to obtain a  $V_{CC}$  nearly equal to 15 V.

#### 2 — $V_C$ and OUTPUT (pins 2 and 3):

$V_C$  is the output high state of the circuit. This pin offers the possibility of setting the output source current at a different level than the sink current but it is no use in our case.

In fact, a resistor of  $33.2\ \Omega$  must be connected between the output and the MOSFET gate to make the switchings smoother. A resistor of about  $1\ \text{k}\Omega$  can be connected between the gate and the ground (or the current sense external resistor) to avoid any inadvertent MOSFET switching on due to noise (see Figure 2).

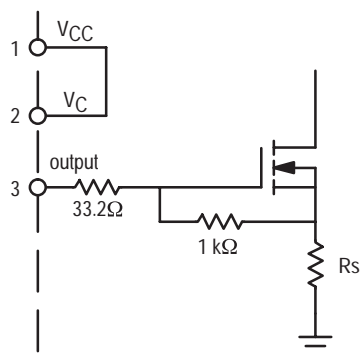


Figure 2.

#### 3 — Foldback (pin 5):

Part of  $V_{CC}$  must be applied to this pin thanks to a resistor divider. This voltage value must be slightly higher than 1 V in normal use, so that this value drops below this threshold value as soon as an overload occurs.

#### 4 — Overvoltage protection (pin 6):

This pin can remain free and then, the  $V_{CC}$  threshold level is fixed equal to nearly 17 V.

On the other hand, to make detection quicker and more accurate, an external resistor divider can be used with a diode and an integration capacitor (refer to the proposed application). The resistor divider is not directly connected to the  $V_{CC}$  because  $V_{CC}$  has a high time constant (refer to the application schematic — Figure 4).

#### 5 — Current sense (pin 7):

The current sense resistor must be designed in order to limit the current below the maximum peak calculated in section II in order to limit the power that the converter is able to draw from the mains; in a fixed frequency mode,  $P_{in} = 1/2 \times L \times I_{pk}^2 \times f_{osc}$ .

Now,  $(I_{pk})_{max} = 5.4\ \text{A}$


In addition, the ( $V_C$ s) clamp level is nearly 1 V (refer to the data sheet).

So, ( $R_s$ ) the current sense resistor, must be equal to

$$(1\ \text{V} / 5.4\ \text{A}), \text{ that is nearly: } 0.18\ \Omega.$$

This value can be obtained using a 1 W,  $0.2\ \Omega$  resistor and a resistor divider ( $442\ \Omega$ ,  $3.16\ \text{k}\Omega$ ) (refer to Figure 3).

## AN1669

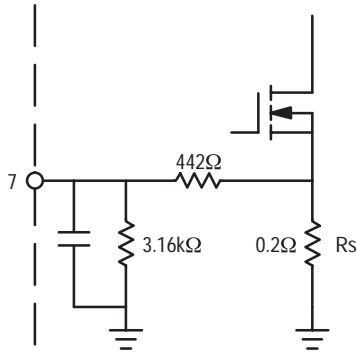

**Figure 3.**

Finally, as the fixed frequency mode is obtained for any working point, the peak current limitation results in an accurate input power limitation (135W in this application note).

### 6 — Oscillator (pins 10 and 16):

The oscillator frequency is determined by the couple ( $C_T$ ,  $R_{ref}$ ) (refer to the data sheet).

Even if capacitors have discrete values, the choice of  $R_{ref}$  allows you to fix precisely the oscillator frequency (however,  $R_{ref}$  also fixes the internal current source ( $I_{ref}$ ), which must be lower than 500  $\mu$ A and higher than 100  $\mu$ A).

$$\begin{aligned} f_{osc} = 40 \text{ kHz} &\longrightarrow R_{ref} = 10 \text{ k}\Omega \\ &\longrightarrow C_T = 1 \text{ nF} \end{aligned}$$

### 7 — Stand-by mode (pins 12 and 15):

In the MC44603, it is possible to reduce the working frequency when little power is being drawn from the mains (stand-by mode).

This stand-by frequency is fixed by connecting a resistor  $R_{Fstby}$  to pin 15, while the power level at which the stand-by mode must be applied is determined by connecting another resistor  $R_{Pstby}$  to pin 12 (this power level is labelled  $P_{thL}$  in the data sheet).

In the data sheet, the equations needed to calculate  $R_{Fstby}$  and  $R_{Pstby}$  are indicated.

Using them, to obtain a power level equal to 10W and a stand-by frequency equal to 20 kHz, the calculated  $R_{Fstby}$  and  $R_{Pstby}$  values are:

$$R_{Pstby} = 8.45 \text{ k}\Omega \text{ and } R_{Fstby} = 22.1 \text{ k}\Omega$$

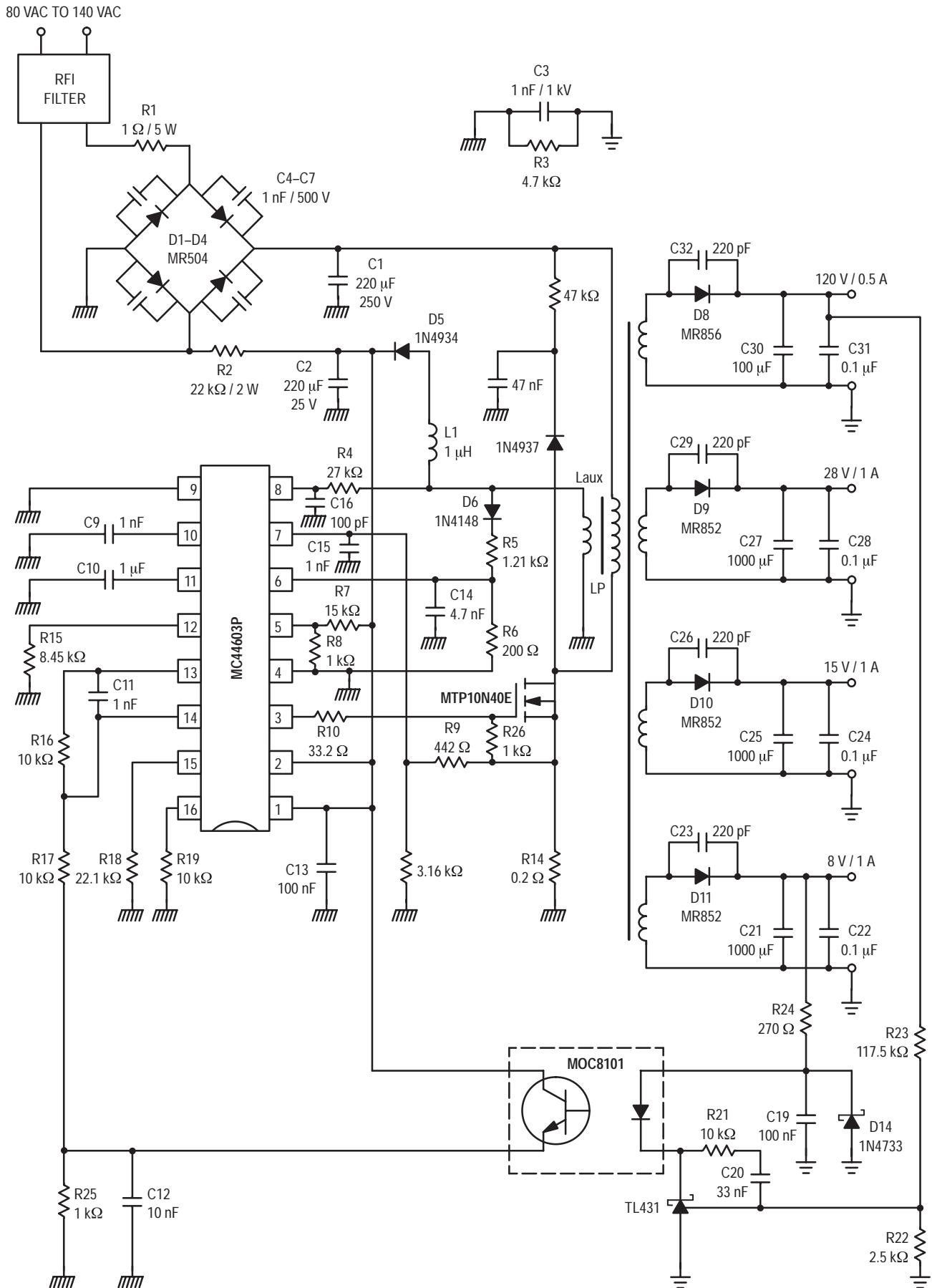


Figure 4. 110W Output Off-Line Flyback Converter with MOSFET Switch, 80 V ↔ 140 V Mains Voltage

# AN1669

**Table 1. 110W Fly-Back Converter, 80 Vrms-140 Vrms Mains Range, MC44603 and MTP10N40E**

Test	Conditions	Results
Line Regulation	Vin = 90 Vac to 140 Vac Fmains = 50 HZ Fmains = 50 HZ	
	120 V Iout = 0.5A	$\Delta = 0 \text{ V}$
	28 V Iout = 1A	$\Delta = 0 \text{ V}$
	15 V Iout = 1A	$\Delta = 0 \text{ V}$
	8 V Iout = 1A	$\Delta = 0 \text{ V}$
Load Regulation	Vin = 110 Vac Iout = 0.3A to 0.5A	$\Delta = 0.05 \text{ V}$
Cross Regulation	Vin = 110 Vac Iout (120 V) = 0.5A Iout (28 V) = 0A to 1A Iout (15 V) = 1A Iout (8 V) = 1A	$\Delta = 0 \text{ V}$
Efficiency	Vin = 110 Vac, Po = 110 W	84.5%
Standby Mode		
P input	Vin = 110 Vac, Pout = 0 W	1.2 W
Switch. freq.		20 KHz fully stable
Output short circuit		Safe on all outputs
Start-up	Pin 110 W	Vac = 80 V

### MOSFET application: information about the transformer


	110W
Lp (turns)	30
Laux (turns)	5
L1 (turns)	40
L2 (turns)	10
L3 (turns)	5
L4 (turns)	3
Al (nH/turns <sup>2</sup> )	274
Core	E-4215A
Material	B2
Former	specific Thomson design
Wire size (mm <sup>2</sup> )	0.315 all windings

### Flyback transformer construction

For cost reduction and simplicity, all windings have the same size. For optimal Lp/Laux coupling, Laux is wound on the second section of Lp.
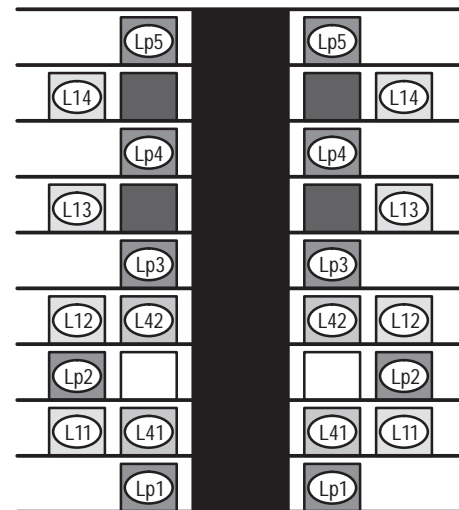
### Former

The normalized primary/secondary isolation is obtained using the multi-slotted former depicted on the figure. This former uses designs patented by LCC Thomson.



### SMT4

- Lp Primary Winding  
(Lp1//Lp3//Lp5) + (Lp2//Lp4)
- Laux Auxilliary Winding
- L1 High Voltage Secondary Winding  
L11//L12//(L13 + L14)
- L2 Secondary Winding (28 V)  
(2 X 10 turns)
- L3 Secondary Winding (15 V)  
(2 X 5 turns)
- L4 Secondary Winding (8 V)  
L41//L42



## IV — APPLICATION 2: 220 V INPUT VOLTAGE

### IV-1 — Choice of the transformer:

One way to use the above design equations, consists of drawing up a table showing how the main SMPS parameters vary with the value of the turn ratio.

To calculate these values, it is necessary to know the input power level. This value is taken equal to (135W) in our application (135W corresponds to an efficiency equal to about 80%). The application results will show that this assumption ensures a desirable margin with the nominal input voltage).

On the other hand, the parameters calculation shows that  $(L \times f_{osc})_{max}$  is the  $(L \times f_{osc})$  value that results in the lowest  $(I_{pk})_{max}$  and  $(p_{on})_{max}$  ones (refer to  $I_{pk}$  or  $p_{on}$  expressions). This  $(L \times f_{osc})$  value is the maximum one that guarantees a fixed frequency working for any working point (refer to section II-1). The SMPS parameters given in the following table are calculated using this threshold value.

#### Choice criteria and definition of the transformer:

As shown by the following table, the higher the turn ratio (N) is, the lower the peak current is. Now, the  $(n_i)_{max}$  is proportional to N and the voltage the transistor must face, increases when N rises. That is why an optimal N value must be chosen.

#### MOSFET case:

To perform a low cost SMPS, it is required to use a MOSFET 600 V. It is necessary to have a safety voltage margin, to avoid the need to incorporate a lossy and costly clamping network that would cut the voltage spikes due to the leakage inductor at the power switch turning off (refer to Figure 1 in section III-1).

Practically, about 550 V is acceptable. Consequently,  $(N = 1.2)$  seems to be a maximum value.

Now, in order to obtain a well coupled transformer with a low leakage inductor value, it is desirable to use a ferrite with a low air-gap.

So, in order to be able to use a ferrite ( $n_i = 140$ ,  $A_L = 274 \text{ nH/turns}^2$ ),  $(N = 1)$  seems to be a preferable value.

Consequently,

$$L_p = A_L \times (N \times 40)^2 \longrightarrow L_p \approx 438 \mu\text{H}$$

and the optimal working frequency is:

$$L \times f_{osc} \leq 24.3 \longrightarrow f_{osc} \leq 55 \text{ kHz}$$

So, the following values can be chosen:

$$\begin{aligned} L &= 438 \mu\text{H} \\ f_{osc} &= 50 \text{ kHz} \end{aligned}$$

and then  $I_{pk} = 3.5\text{A}$

#### BIPOLAR transistor case:

As the gain of a Bipolar transistor decreases when the collector current level rises, the SMPS peak current must be as low as possible. That is why N must be chosen as high as possible. Now, if classical BIPOLAR transistors are able to face 1000 V or 1200 V, their  $V_{CEO}$  is generally low. The transistor used in the application, the MJE18206, has a  $V_{CES}$  equal to 1200 V and a  $V_{CEO}$  equal to 600 V. Since there are damped oscillations (converging to  $V_{in}$ ) during the dead-time (refer to Figure 1), the transistor may be turned on while its  $V_{CE}$  voltage is higher than  $V_{in}$  (the maximum  $V_{in}$  value being nearly equal to 400 V). That is why, even if a resistor is connected between the base and the emitter of the transistor (refer to section IV-2), the  $(V_T)_{max}$  (that is,  $(V_{in} + N V_o)_{max}$ ) must be chosen lower than 600 V, to ensure system reliability.

In addition to this, a second choice criterion is  $(n_i)_{max}$ , since transformer saturation must be avoided.

$(N = 1.6)$  seems to be a good choice that enables the use of a ferrite ( $A_L = 250 \text{ nH/turns}^2$ ;  $n_i = 180$ )

Consequently,

$$L = A_L \times (N \times 40)^2 \longrightarrow L \approx 1\text{mH}$$

So, the optimal working frequency is:

$$L \times f_{osc} \leq 43.7 \longrightarrow f_{osc} \leq 43 \text{ kHz}$$

Finally, the following value can be taken:

$$\begin{aligned} L &= 1\text{mH} \\ f_{osc} &= 43 \text{ kHz} \\ (I_{pk})_{max} &= 2.5\text{A} \end{aligned}$$

N	$(L \cdot f_{osc})_{max}$	$(I_{pk})_{max}$ (A)	$(V_T)_{max}$ (V)	$(V_D)_{max}$ (V)	MOSFET on losses/ $R_{dson}$ (W/ $\Omega$ )	BIPOLAR on losses/ $V_{CE}$ (W/A)	$(n_i)_{max}$
0.75	16.2	4.1	490	650	1.5	0.54	122
1.00	24.3	3.3	520	520	1.2	0.54	133
1.20	30.9	3.0	540	450	1.1	0.54	144
1.40	37.4	2.7	570	400	1.0	0.54	150
1.60	43.7	2.5	590	370	0.9	0.54	159
1.80	49.7	2.3	620	340	0.8	0.54	168
2.00	55.5	2.2	640	320	0.8	0.54	176

NOTE: N: turn ratio (refer to II-5)

$(V_T)_{max}$ : maximum voltage the power switch must face

$(V_D)_{max}$ : maximum voltage the 120 V output diode must face

# AN1669

## IV-2 — MC44603 pins use: (refer to the application schematics)

### 1 — Vcc (PIN 1):

The pin Vcc must be connected to a transformer auxiliary winding. This extra winding turns number can be chosen equal to 5, in order to obtain a Vcc nearly equal to 15 V.

### 2 — Vc and OUTPUT (pins 2 and 3):

Vc is the output high state of the circuit. This pin offers the possibility of setting the output source current at a different level than the sink current.

#### — MOSFET case:

A resistor of 10 Ω must be connected between the output and the MOSFET gate to make the switchings smoother. A resistor of about 1 kΩ can be connected between the gate and the ground (or the current sense external resistor) to avoid any inadvertent MOSFET switching on due to noise.

#### — BIPOLAR transistor case:

For the on-time, a bipolar transistor requires a base current labelled IB1, that must be higher than:

$$(Ic)_{max} / \beta_{min}$$

where

(Ic)max is the maximum collector current (that is Ipkmax if the current sense resistor is well designed — refer to section IV-5), and

βmin is the minimum guaranteed transistor gain for (Ic = (Ic)max)

Now, with the MJE18206: (βmin ≈ 7) for (Ic)max = 2.5A


So, (IB1 = 400mA) is a good value that ensures a safety margin.

On the other hand, the turn off base current peak must be nearly equal to (2 x IB1). The couple (Dz,Cz) is used to build a voltage source Vz (during the on-time), able to produce IB2.

$$So, \quad I_{B1} = (V_{cc} - V_z - V_{be}) / (r_1 + r_2)$$

$$I_{B2} = (V_z + V_{be}) / r_2$$

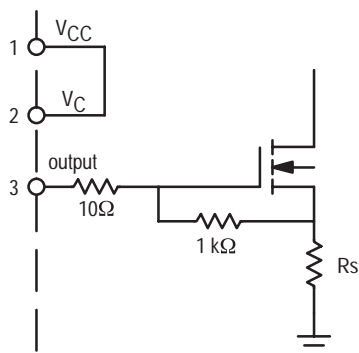Consequently, using  $V_z = 3.3 \text{ V}$   
 $C_z = 1 \mu\text{F}$



MOSFET drive

$$r_1 = 22 \Omega$$

$$r_2 = 4.7 \Omega$$

As (Vcc ≈ 15 V), the obtained base currents are:

$$I_{B1} \approx 410 \text{ mA}$$

$$I_{B2} \approx 850 \text{ mA}$$

These base currents enable a correct transistor drive.

### 3 — Foldback (pin 5):

A portion of Vcc must be applied to this pin thanks to a resistor divider. This voltage value must be slightly higher than 1 V in normal working so that this value drops below this threshold value as soon as an overload occurs.

### 4 — Overvoltage protection (pin 6):

This pin can remain free and then, the Vcc threshold level is fixed equal to nearly 17 V.

On the other hand, to make detection quicker and more accurate, an external resistor divider can be used with a diode and an integration capacitor. In the proposed application, this resistor divider is not directly connected to the Vcc because Vcc has a high time constant (refer to the application schematics).

### 5 — Current sense (pin 7):

The current sense resistor must be designed in order to limit the current down to the maximum peak calculated in section II in order to limit the power the converter is able to draw from the mains (in a fixed frequency mode, Pin = 1/2 x L x Ipk<sup>2</sup> x fosc).

— MOSFET case: (Ipk)max = 3.5A


Now, the (Vcs) clamp level is nearly 1 V (refer to the data sheet).

So, (Rs) the current sense resistor, must be equal to (1 V / 3.5A), that is nearly: 0.28Ω (2 x 0.56 Ω in parallel).

— BIPOLAR case: (Ipk)max = 2.5A

So, (Rs) must be equal to (1 V / 2.5A), that is: 0.4 Ω (3 x 1.2 Ω in parallel).

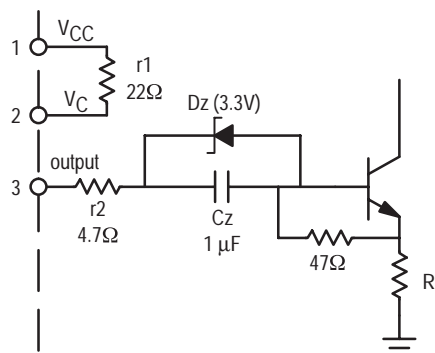Finally, as the fixed frequency mode is ensured for any working point, the peak current limitation results in an accurate input power limitation (135W in this application).



BIPOLAR transistor drive

Figure 5.

### 6 — Oscillator (pin 10 & 16):

The oscillator frequency is determined by the couple ( $C_T$ ,  $R_{ref}$ ) (refer to the data sheet).

As capacitors have discrete values, the choice of  $R_{ref}$  allows you to fix precisely the oscillator frequency (however,  $R_{ref}$  also fixes the internal current source ( $I_{ref}$ ), which must be lower than 500  $\mu$ A and higher than 100  $\mu$ A).

MOSFET case:

$$f_{osc} = 50 \text{ kHz} \longrightarrow R_{ref} = 10 \text{ k}\Omega \longrightarrow C_T = 820\text{pF}$$

BIPOLAR case:

$$f_{osc} = 43 \text{ kHz} \longrightarrow R_{ref} = 10 \text{ k}\Omega \longrightarrow C_T = 1\text{nF}$$

### 7 — Stand-by mode (pins 12 and 15):

In the MC44603, it is possible to reduce the working frequency when little power is being drawn from the mains (stand-by mode).

This stand-by frequency is fixed by connecting a resistor  $R_{Fstby}$  to pin 15, while the power level at which the stand-by mode must be applied is determined by connecting another resistor  $R_{Pstby}$  to pin 12 (this power level is labelled  $P_{thL}$  in the data sheet).

In the data sheet, the equations needed to calculate  $R_{Fstby}$  and  $R_{Pstby}$  are indicated.

Using them, to obtain a power level equal to 15W and a stand-by frequency equal to 20 kHz, the calculated  $R_{Fstby}$  and  $R_{Pstby}$  values are:

$$\text{MOSFET case:} \quad R_{Pstby} = 10 \text{ k}\Omega \quad R_{Fstby} = 27 \text{ k}\Omega$$

$$\text{BIPOLAR case:} \quad R_{Pstby} = 10 \text{ k}\Omega \quad R_{Fstby} = 22 \text{ k}\Omega$$

# AN1669

180 VAC TO 280 VAC

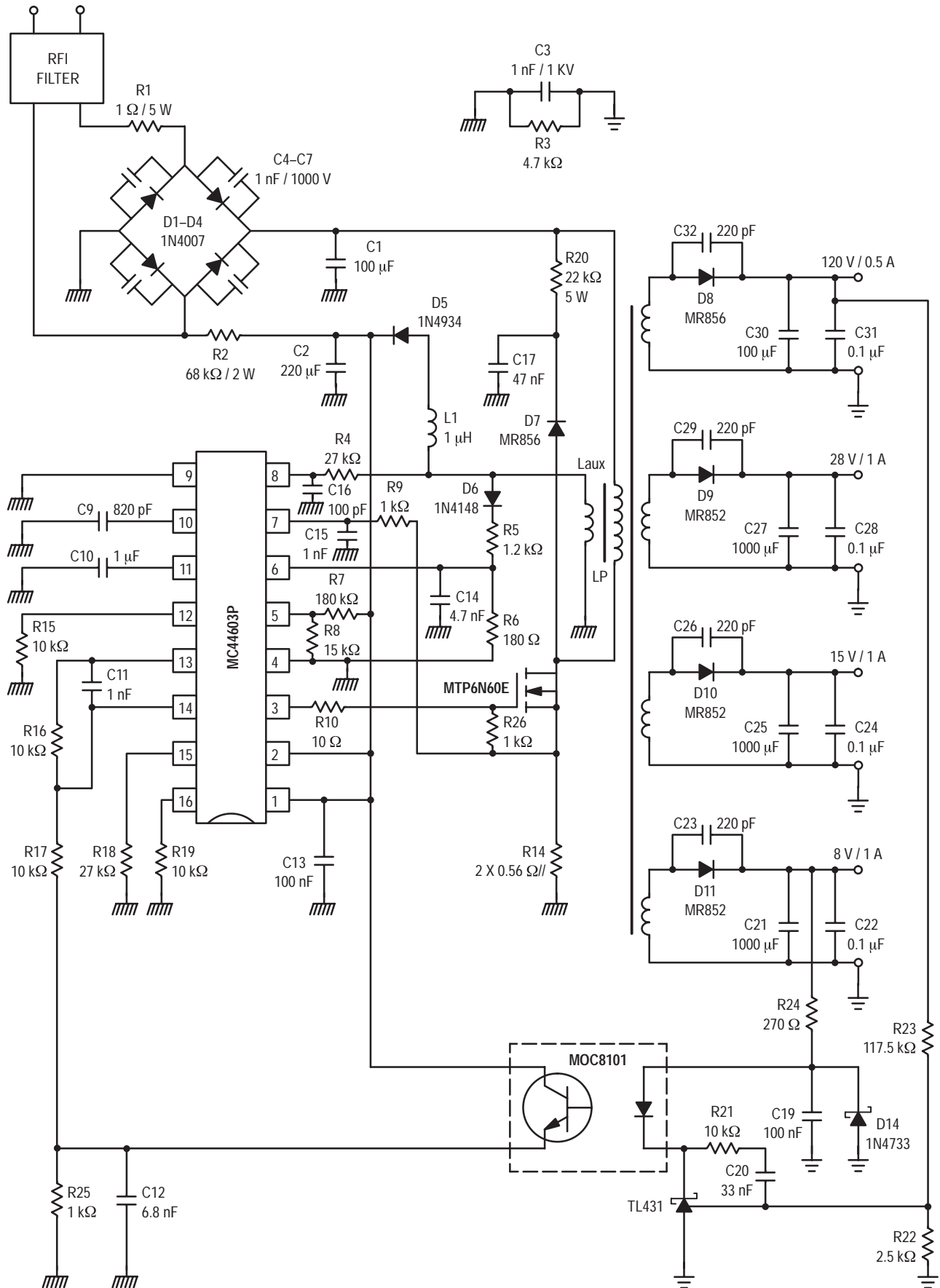


Figure 6. 110 W Output Off-Line Flyback Converter with MOSFET Switch. 180 V-280 V MAINS RANGE

Table 2. 110W Fly-Back Converter, 180 V-280 V Mains Range, MC44603 and MTP6N60E

Test	Conditions	Results
Line Regulation	Vin = 180 Vac to 280 Vac Fmains = 50 HZ	
120 V	Iout = 0.5A	$\Delta = 0 V$
28 V	Iout = 1A	$\Delta = 0 V$
15 V	Iout = 1A	$\Delta = 0 V$
8 V	Iout = 1A	$\Delta = 0 V$
Load Regulation	Vin = 220 Vac	
155 V	Iout = 0.3A to 0.5A	$\Delta = 0.05 V$
Cross Regulation	Vin = 220 Vac	
120 V	Iout (120 V) = 0.5A Iout (28 V) = 0A to 1A Iout (15 V) = 1A Iout (8 V) = 1A	$\Delta = 0 V$
Efficiency	Vin = 220 Vac, Po = 110 W	84%
Standby Mode		
P input	Vin = 220 Vac, Pout = 0 W	3 W
Switch. freq.		20 KHz fully stable
Output short circuit		Safe on all outputs
Start-up	Pin 110 W	Vac = 160 V

**MOSFET application: information about the transformer**


	110W
Lp (turns)	40
Laux (turns)	5
L1 (turns)	40
L2 (turns)	10
L3 (turns)	5
L4 (turns)	3
Al (nH/turns <sup>2</sup> )	274
Core	E-4215A
Material	B2
Former	specific Thomson design
Wire size (mm <sup>2</sup> )	0.315 all windings

**Flyback transformer construction**

For cost reduction and simplicity, all windings have the same size. For optimal Lp/Laux coupling, Laux is wound on the second section of Lp.

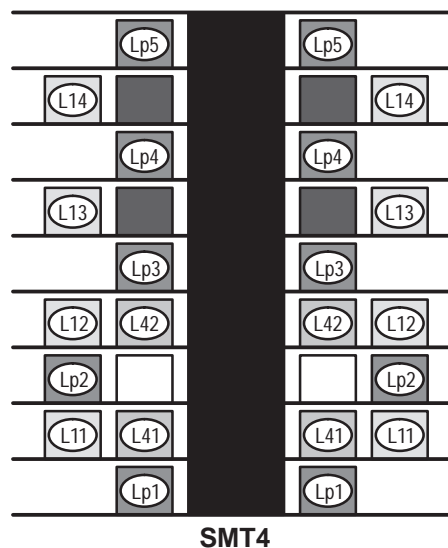**Former**

The normalized primary/secondary isolation is obtained using the multi-slotted former depicted on the figure. This former uses designs patented by LCC Thomson.



- Lp Primary Winding  
(Lp1//Lp3//Lp5) + (Lp2//Lp4)
- Laux Auxilliary Winding
- L1 High Voltage Secondary Winding  
L11//L12//(L13 + L14)
- L2 Secondary Winding (28 V)  
(2 X 10 turns)
- L3 Secondary Winding (15 V)  
(2 X 5 turns)
- L4 Secondary Winding (8 V)  
L41//L42

# AN1669

180 VAC TO 280 VAC

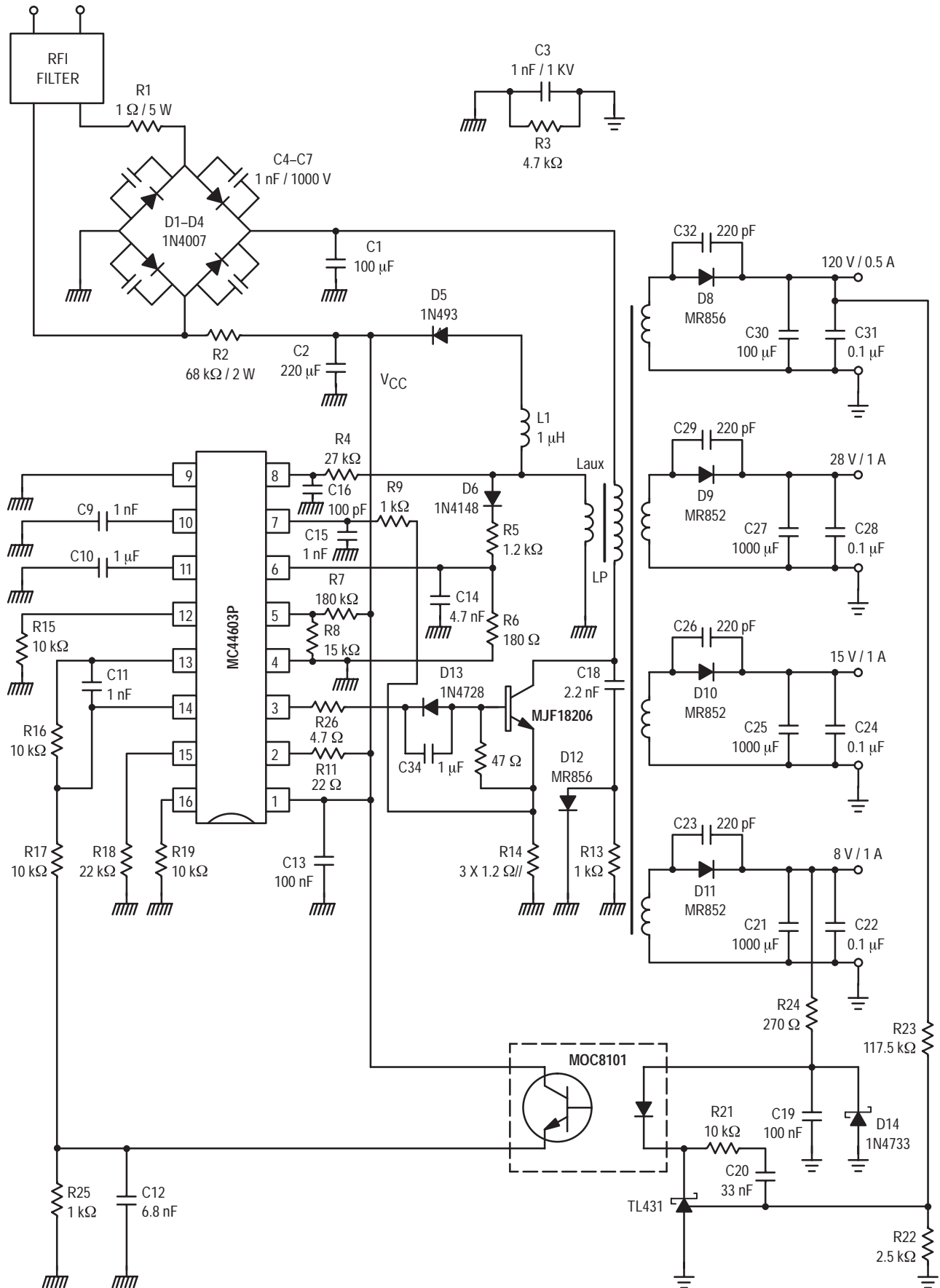


Figure 7. 110 W Output Off-Line Flyback Converter with Bipolar Switch. 180 V–280 V MAINS RANGE

Table 3. 110W Fly-Back Converter, 180 V-280 V Mains Range, MC44603 and MJF18206

Test	Conditions	Results
Line Regulation	Vin = 180 Vac to 280 Vac Fmains = 50 HZ	
120 V	Iout = 0.5A	$\Delta = 0 V$
28 V	Iout = 1A	$\Delta = 0 V$
15 V	Iout = 1A	$\Delta = 0 V$
8 V	Iout = 1A	$\Delta = 0 V$
Load Regulation	Vin = 220 Vac	
120 V	Iout = 0.2A to 0.5A	$\Delta = 0.05 V$
Cross Regulation	Vin = 220 Vac	
120 V	Iout (120 V) = 0.5A Iout (28 V) = 0A to 1A Iout (15 V) = 1A Iout (8 V) = 1A	$\Delta = 0 V$
Efficiency	Vin = 220 Vac, Po = 110 W	85%
Standby Mode		
P input	Vin = 220 Vac, Pout = 0 W	3W
Switch. freq.		20 KHz fully stable
Output short circuit		Safe on all outputs
Start-up	Pin 110 W	Vac = 160 V

**BIPOLAR application: information about the transformer**


	110 W
Lp (turns)	64
Laux (turns)	5
L1 (turns)	40
L2 (turns)	10
L3 (turns)	5
L4 (turns)	3
Al (nH/turns <sup>2</sup> )	250
Core	E-4215A
Material	B2
Former	specific Thomson design
Wire size (mm <sup>2</sup> )	0.315 all windings

**Flyback transformer construction**

For cost reduction and simplicity, all windings have the same size. For optimal Lp/Laux coupling, Laux is wound on the second section of Lp.

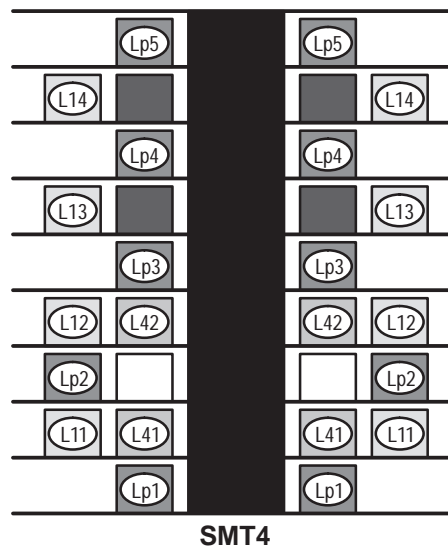**Former**

The normalized primary/secondary isolation is obtained using the multi-slotted former depicted on the figure. This former uses designs patented by LCC Thomson.



- Lp Primary Winding (Lp1//Lp3//Lp5) + (Lp2//Lp4)
- Laux Auxilliary Winding
- L1 High Voltage Secondary Winding L11//L12//(L13 + L14)
- L2 Secondary Winding (28 V) (2 X 10 turns)
- L3 Secondary Winding (15 V) (2 X 5 turns)
- L4 Secondary Winding (8 V) L41//L42

# AN1669

## V — CONCLUSION

These applications show a significant advantage of the fixed frequency mode: it enables us to precisely limit the maximum power that may be drawn by the converter from the mains (135 W in our case).

Note that the stand by losses are lower in the 110 V application because in this case, only a low loss, costly clamping network is used to protect the MOSFET (no snubber). Indeed, the snubber and clamping arrangements dissipate some energy (that is not insignificant) at each switching. That is why the reduction of the switching frequency is a very effective means to decrease the stand-by losses (the snubber and clamping arrangement cannot be removed in most cases).

This application note does not pay much attention to the MC44603's protection features. Two features are especially noteworthy:

- the foldback that protects the converter when there is an overload
- the effective demagnetization section that ensures a discontinuous mode

### Notes:

- the MOSFET on time losses are high in the 110 V application. The use of a MOSFET having a lower  $R_{ds(on)}$  (or two MOSFET in parallel) would improve the efficiency
- because of these losses, the input range of the proposed solution is actually: 90 V–140 V

In order to minimize the length of this application note, it does not consider a universal mains range application. Such a SMPS could be designed using the methods described here.

## APPENDIX

### OREGA TRANSFORMERS

Type	$A_L$	(ni) @100°C	Ferrite	Wire $\varnothing$ (mm)	Nmax
SMT1	448	40	5H20	0.25	56
	260	80	5H20	0.25	56
	240	85	5H20	0.224	68
	220	90	5H20	0.224	68
	180	125	5H20	0.224	68
SMT3	350	80	B1	0.315	75
	250	110	B1	0.315	75
	250	130	B3	0.315	75
	190	160	B1	0.315	75
	178	180	B1	0.315	75
SMT4	336	110	B1	0.28	68
	320	135	B3	0.315	52
	274	140	B1	0.40	36
	250	180	B3	0.40	36
	238	200	B3	0.40	36
	215	190	B1	0.40	36
	192	210	B1	0.40	36
	192	245	B3	0.40	36
SMT47	560	100	B3	0.315	76
	428	140	B1	0.40	46
	428	150	B3	0.50	26
	372	190	B3	7 X 0.2	20
	315	220	B3	7 X 0.2	20
	262	270	B1	7 X 0.2	20
	234	310	B3	7 X 0.2	20


The last column indicates the maximum number of turns per slot (refer to page 14) that will fall within the insulation norms, when using wires whose size is indicated in the "wire" column.



# NOTES

# NOTES

All products are sold on Motorola's Terms & Conditions of Supply. In ordering a product covered by this document the Customer agrees to be bound by those Terms & Conditions and nothing contained in this document constitutes or forms part of a contract (with the exception of the contents of this Notice). A copy of Motorola's Terms & Conditions of Supply is available on request.

Motorola reserves the right to make changes without further notice to any products herein. Motorola makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does Motorola assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation consequential or incidental damages. "Typical" parameters which may be provided in Motorola data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. Motorola does not convey any license under its patent rights nor the rights of others. Motorola products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the Motorola product could create a situation where personal injury or death may occur. Should Buyer purchase or use Motorola products for any such unintended or unauthorized application, Buyer shall indemnify and hold Motorola and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that Motorola was negligent regarding the design or manufacture of the part. Motorola and  are registered trademarks of Motorola, Inc. Motorola, Inc. is an Equal Opportunity/Affirmative Action Employer.

The Customer should ensure that it has the most up to date version of the document by contacting its local Motorola office. This document supersedes any earlier documentation relating to the products referred to herein. The information contained in this document is current at the date of publication. It may subsequently be updated, revised or withdrawn.

Mfax is a trademark of Motorola, Inc.

**How to reach us:**

**USA/EUROPE/Locations Not Listed:** Motorola Literature Distribution;  
P.O. Box 5405, Denver, Colorado 80217. 1-303-675-2140 or 1-800-441-2447

**JAPAN:** Nippon Motorola Ltd.; SPD, Strategic Planning Office, 141,  
4-32-1 Nishi-Gotanda, Shinagawa-ku, Tokyo, Japan. 81-3-5487-8488

**Customer Focus Center: 1-800-521-6274**

**Mfax™:** RMFAX0@email.sps.mot.com – TOUCHTONE 1-602-244-6609  
Motorola Fax Back System – US & Canada ONLY 1-800-774-1848  
– <http://sps.motorola.com/mfax/>

**ASIA/PACIFIC:** Motorola Semiconductors H.K. Ltd.; 8B Tai Ping Industrial Park,  
51 Ting Kok Road, Tai Po, N.T., Hong Kong. 852-26629298

**HOME PAGE:** <http://motorola.com/sps/>



**MOTOROLA**

