



Relay PSU Protector

This circuit may prove very useful when trying out a project for the first time. Any power supply shorts will pull the supply voltage (V_i) down, turning the transistors on and tripping the relay. This then causes the 10 k resistor to latch the circuit in the 'tripped' mode. The relay is connected so that it disconnects the supply to the circuit being tested. The circuit can be reset by pressing the momentary-contact switch shown.

R_1 is selected so that V_i/R_1 is greater than V_s/R_2 . R_2 must be greater than R_1 and V_s/R_2 must be large enough to turn the first transistor on.

The circuit (which was sent in by Scott Field of Taree) work with V_i ranging from 3 to 18 volts.