In part three of our <u>Understanding Voltage References</u> series, my colleague Marek Lis talked about how to achieve shunt reference flexibility with series reference precision. In this blog, you'll see how to use an adjustable shunt reference as a comparator.

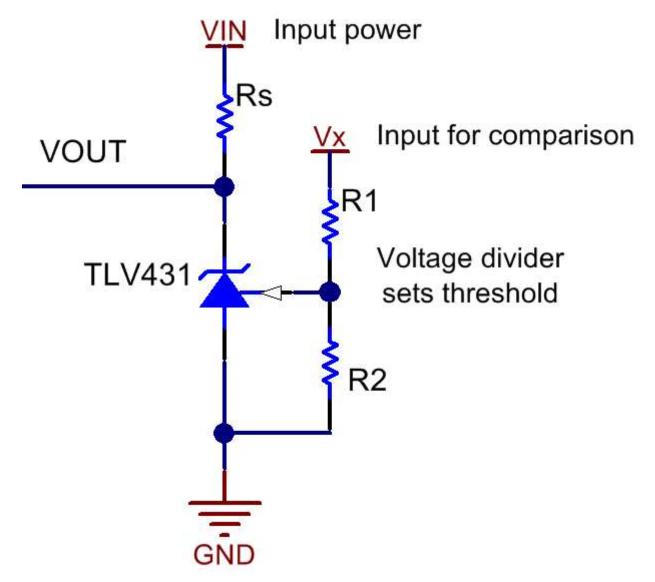


Figure 1: <u>TLV431</u> as a comparator

In a typical adjustable shunt reference application, the output is fed through a resistor divider to the feedback pin, such that the feedback pin is equal to the internal reference voltage during steady state.

In the schematic shown in Figure 1, the  $\underline{\text{TLV431}}$  adjustable shunt reference is configured for open-loop operation, which means that the output is not connected to the feedback pin. Instead, the signal  $V_X$  drives the feedback pin through a resistor divider. The resistor divider is set such that the value at the feedback pin is equal to the internal reference voltage when  $V_X$  is at the threshold voltage,  $V_{TH}$ .

This configuration is similar to running an op-amp in an open loop, and driving the positive terminal with V<sub>X</sub>.
 However, instead of having to create a reference with another supply or a resistor divider for the negative terminal, the comparator reference voltage is internal to the part.

The output  $V_{OUT}$  is driven high to  $V_{IN}$  when the internal reference voltage is less than the threshold voltage, and is driven low when the internal reference voltage is greater than the threshold voltage. These conditions are summarized in Table 1 and illustrated in Figure 2.

**Table 1: Conditions of Voltage Reference Comparator Output** 

V <sub>OUT</sub> Value	Conditions
V <sub>OUT</sub> = Vin	$V_X < V_{TH}$
V <sub>OUT</sub> = low	$V_X > V_{TH}$

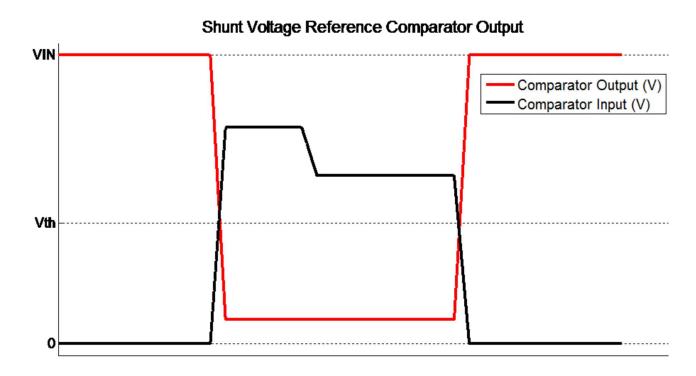


Figure 2: Output of <u>TLV431</u> Comparator Circuit

The output does not reach 0V on a logic low, because there is a minimum voltage drop across the shunt. For the <u>TLV431</u>, logic low in this comparator configuration is approximately 1V. The output of the comparator could be fed into another circuit to compensate for communication with various logic levels. A resistor divider on V<sub>OUT</sub> would be a very simple means of dropping the logic levels, but the impedance of the resistors should be high enough to not have a significant impact on the current into the shunt.

As an example, if we want a comparator with a threshold at 5V with a VIN of 12V, select an  $R_S$  to sufficiently provide the minimum operating current for the selected device. For an input voltage of 12V, a supply resistor of  $20k\Omega$  will provide  $600\mu$ A, which is more than enough to power the device that has a typical minimum

• operating current of  $55\mu A$ . The resistor divider on  $V_X$  to set the threshold voltage can be calculated from the following equation:

$$V_{TH} = V_{REF} \left( rac{R_1}{R_2} + 1 
ight)$$

In this case,  $V_{REF}$  is 1.24V and  $V_{TH}$  is 5V. This results in a relationship between  $R_1$  and  $R_2$  where  $R_1 \approx 3R_2$ . Figure 3 shows the schematic with values.

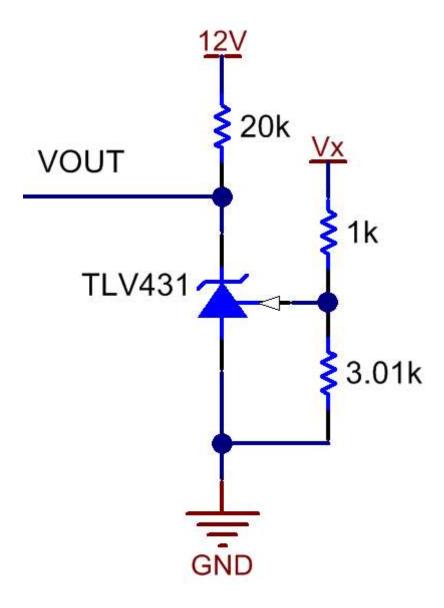


Figure 3: TLV431 as a comparator with 5V threshold

To sum this up, voltage references can be used for more purposes than for a simple fixed reference. This post demonstrates how a shunt voltage reference can act as a comparator. Coming up in the next post in the series, Understanding Voltage References, my colleague Marek Lis will discuss level shifting of precision voltage references.

• For an overview of the difference between a series and shunt voltage reference, read Part 1: "Shunt versus series: Which voltage reference topology is right for you?"

In the meantime, get more more information on <u>TI's voltage reference products</u>.





jun yin over 7 years ago

what's the difference betwen lmv431 and tlv431?



Mark Tarnowski over 3 years ago

In figure 3, you have the correct values... just in the wrong places. Swap 1k and 3.01k resistors for the correct circuit configuration.

1 0 members are here

3 comments



Brian S. Hansen over 1 year ago

What will be the voltage drop over the regulator when  $V_X > V_{TH}$ ?