

LATCHING CURRENT

By E. Leblanc

An important problem concerning the utilization of components such as thyristors or triacs is the holding of the component in the conducting state after the trigger current has disappeared during firing. Very often, the firing problems supposedly due to the gate current I_G or to the firing time t_{GT} are in reality due to the latching current I_L .


After a definition we will illustrate the importance of this parameter by concrete examples. Then we will describe how to measure it and its variation according to the utilization conditions of the components.

The study will be based on the triac. The points treated are valid for thyristors (except for the various conduction modes).

DEFINITION

The latching current, I_L , of a triac is the minimum value of the main current (current flowing between electrodes A_2 and A_1) which enables the component to remain in the conducting state after the gate current I_G has ceased (Figure 1).

Figure 1 : Controlled by the gate pulse, I_G , the triac is fired, and a current I_T flows through it, imposed by the main current. If the gate current I_G is stopped before current I_T reaches the value of the latching current I_L , the triac is blocked (as shown in the figure).

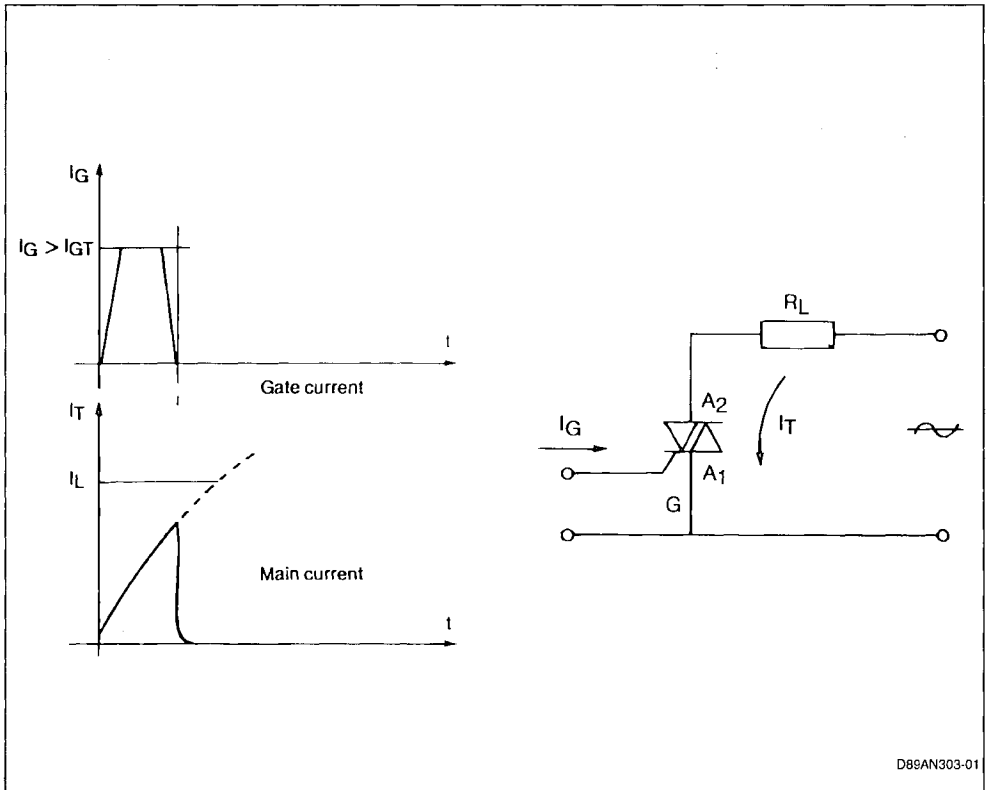


D88AN303-01

APPLICATIONS

Example 1 : Control of a low power signalling lamp by triac.

Figure 2 : Control of a Low Power Signalling Lamp by Triac.

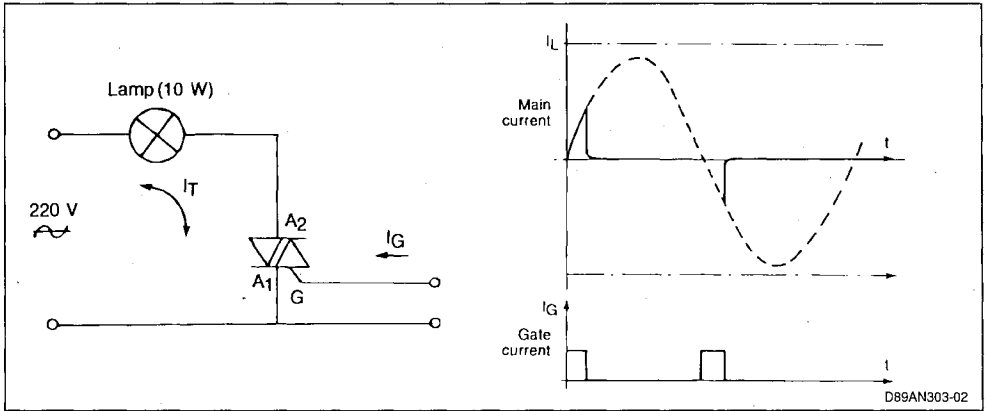


Current in the main circuit of the triac and gate current. The lamp power is too low (eg. : $P \leq 10$ W and the triac BTA 12.400 B) to impose a sufficient current (shown in dotted lines in the diagram) in the triac to keep it in the conducting state after interruption of the gate current I_G . The triac does not conduct.

A BTA 12.400 B triac is used to control the flashing of a 10 W signalling light. The peak current in the circuit

will therefore be 65 mA. This value is very close to that of the typical latching current given in the data book for this type of triac : 50 mA (quadrant 1, 3 and 4). Thus the user's case could be that described in figure 2, that is, a triac whose latching current I_L in the first quadrant is equal to 70 mA. His triac will never be fired. For correct operation, the user should thus employ a sensitive triac (e.g. T08-6A I_L : 8 mA).

Example 2 : Control of an inductive load by triac.

Figure 3 : Voltage Across and Current Through the Triac.

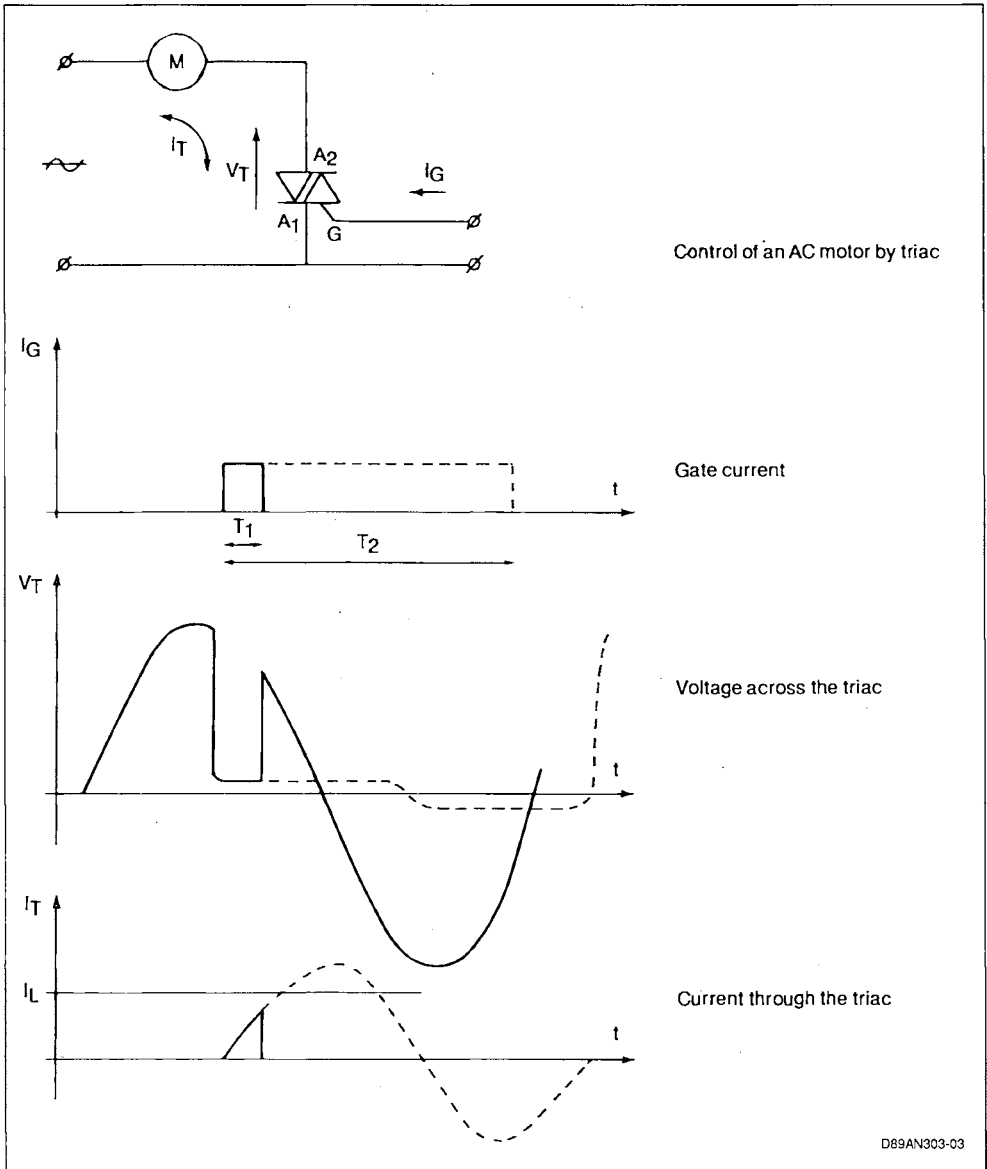

In continuous lines : short gate signal : the triac does not remain in the conducting state because the main current did not reach the value of the triac latching current before suppression of the gate current.

In dotted lines : long gate signal : the triac is fired and remains in the conducting state until its current falls below the holding current I_H after suppression of the gate current I_G .

On a highly inductive load, the inductance limits the current rise time to :

$$\frac{di_T}{dt} = \frac{V_a}{L}$$

(V_a : power supply voltage at the time the gate signal is applied ; L : load inductance).

Consider the operation on one full-wave of the power supply voltage. If the duration t_1 of the gate current pulse I_G is very small compared with a half-wave of the power supply voltage, the triac current cannot reach the triac latching current level in the firing mode considered (here the 1st quadrant). Thus firing will not take place and the voltage across the


triac increases. For triggering to be steady, the duration of pulse t_2 should be long when compared with a half-wave of the power supply voltage. The current set up in the triac is imposed by the load impedance. The triac remains in the conducting state until the current falls below the holding current I_H . It is blocked if the I_G current pulse has ended.

Another method consists of applying a train of closely spaced pulses to the triac gate instead of a square wave.

The SGS-THOMSON Microelectronics applications laboratories have developed a number of triac control circuits, specially designed to work on inductive loads (see bibliography, ref. N° 1).

Example 3 : Control by triac of a load whose power varies considerably.

Figure 4 : Control of an Arc Welding Set by Triac.

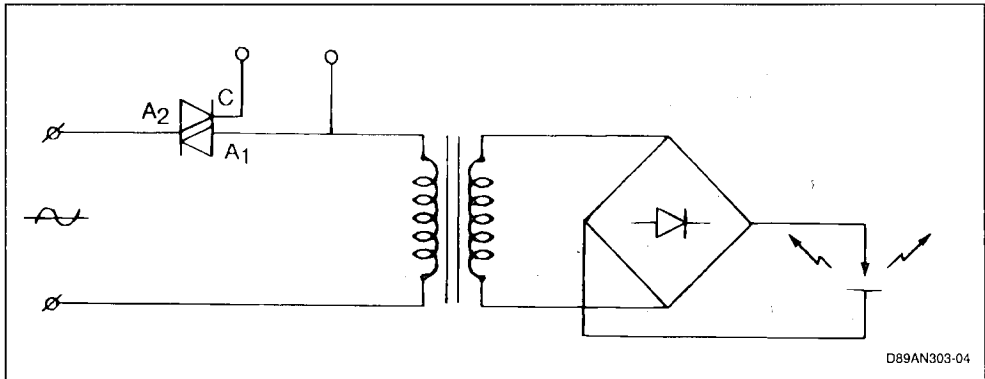

D89AN303-04

The designer of an arc welding set whose power is adjustable by triac, chooses a component capable of controlling high currents. For example, if the maximum current to be controlled is 40 A_{rms} , the designer, for safety, will choose a triac rated at 60 A_{rms} , thus a triac with a high latching current. Now, off-load, the transformer magnetizing current could be very low or even below the triac latching current I_L in one of the quadrants. This means that the triac could fire correctly in the first quadrant and then not fire if the next firing is to take place in the second quadrant where the I_L is much higher. A considerable unbalance then occurs, generating a DC current heating the transformer and preventing the equipment from operating correctly.

Since the latching current I_L increases with the size

of components, and thus with their rating, the user would thus be well advised not to select an excessively high rating for his triac in order to have the lowest possible latching current.

A.N : For this type of application, the SGS-THOMSON Microelectronics applications laboratories place at the disposal of designers a number of schematics meant for this type of circuit (see bibliography, ref. N°1).


These three examples illustrate the importance of the I_L parameter and the problems that it can cause in a circuit. To ensure stable firing of a triac or a thyristor, it is absolutely necessary for the circuit which is controlled to impose a current which is higher than its latching current.

FAVORABLE EFFECT OF AN RC CIRCUIT ON THE FIRING OF A THYRISTOR OR A TRIAC

In most inductive load applications of triacs or thyristors, the user connects an RC network between the anode and cathode of the device to eliminate the

risk of premature firing by transients or spontaneous firing by $(dv/dt)_c$ (case of triacs) (see figure 5). Capacitance C and the load impedance attenuate steep voltage transients transmitted by the mains or resulting from switching inductive loads.


Figure 5 : Reducing the Risk of Untimely Firing on Inductive Loads : the RC Circuit (called « Snubber »).

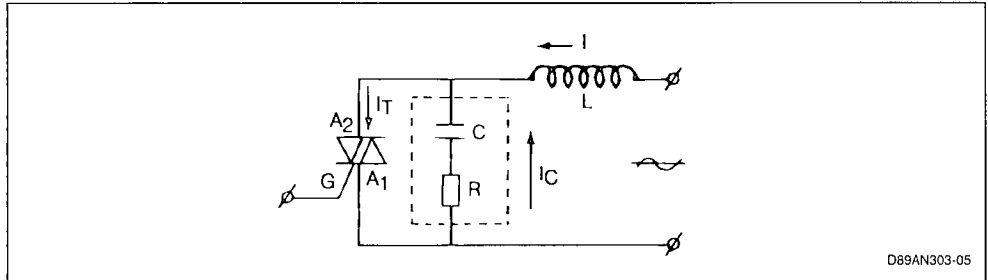

This RC network has also a second advantage. In fact, the energy accumulated in capacitor C after turning off is fed back to the triac when firing. The speed at which the current increases in the triac during discharge of the capacitor is then limited only by the peak charge voltage of the capacitor and the in-

ductance of the circuit connecting the SNUBBER to the triac. The current amplitude is the quotient of peak charge voltage of the capacitor by the series resistance R. This circuit thus helps the current to rise very quickly above the latching current I_L of the device (see figure 6).


Figure 6 : Favorable Effect of the RC Circuit for Firing on a Highly Inductive Load.

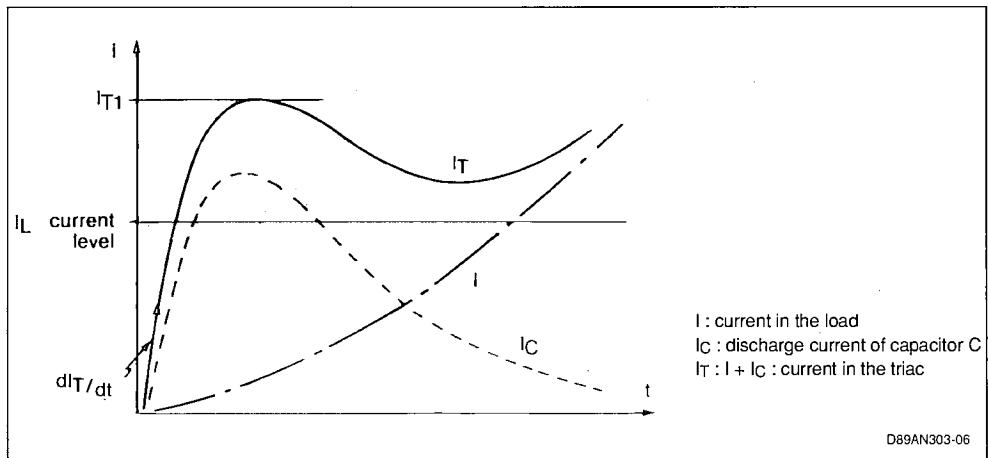

Note : When using an RC circuit, it is not advisable to work with a series resistance R which is too low. In fact, the combined effect during firing of I_T (figure 6) (equal to the quotient of the capacitor peak charge voltage and resistance R) and the current slope dI_T/dt (equal to the quotient of the capacitance charging voltage by the inductance of the connection between the triac and the RC circuit) could be dangerous for the triac. A value for R higher than 100 ohms is recommended.

LATCHING CURRENT (I_L) MEASUREMENT

Figure 7 : Latching Current (I_L) Measurement Circuit.

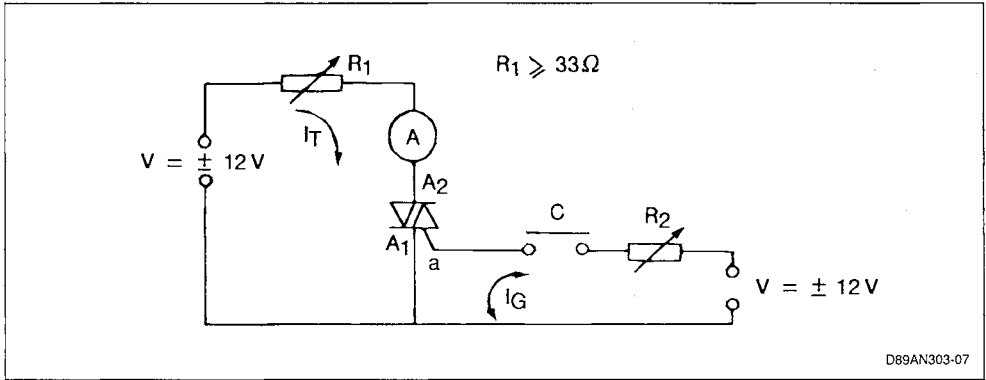

The closing of contact C enables passage of the gate current whose is selected higher than that of the triac firing current, I_{GT} to be measured. By gradually decreasing the value of resistance R_1 , while continuing to transmit pulses of gate current I_G , the main current I_T is increased. As long as the value of the I_T current is lower than that of the device latching current I_L , the device does not remain in the conducting state. The value of the latching current I_L is the value of the I_T current read as soon as the triac remains on, after suppressing the gate current I_G .

Only sensitive thyristors ($I_{GT} \leq 500 \mu A$) are measured with a $1 K\Omega$ resistor between gate and cathode.

Parameter I_L varies with the width of the gate current pulse I_{GT} and its level. For the measurement to be reproduced correctly, the following rules should thus be observed :

Fix a sufficiently wide control pulse I_G . The width of the pulse should be at least equal to 1 ms.

Impose a gate current I_G sufficiently high with respect to that of the triggering current I_{GT} of the device to be measured.

An $\frac{I_G}{I_{GT}}$ ratio higher than or equal to 1.2 is advisable.

Example : BTA 12.600 C
 $I_{GT \max (Q IV)} = 50 \text{ mA}$ therefore
 $I_G = 60 \text{ mA}$

In the case of a triac, there are four latching current I_L values that correspond to the four quadrants of triac operation :

- ($I_L + +$) when the electrodes A_2 and G are positive with respect to electrode A_1 .
- ($I_L + -$) when electrode A_2 is positive with respect to electrode A_1 and electrode G is negative with respect to electrode A_1 .
- ($I_L - -$) when electrodes A_2 and G are negative with respect to electrode A_1 .
- ($I_L - +$) when electrode A_2 is negative with respect to electrode A_1 and electrode G is positive with respect to electrode A_1 .

VARIATIONS OF LATCHING CURRENT I_L WITH THE UTILIZATION CONDITIONS

a) Variations of the I_L current with sensitivity of triacs and the various directions of conduction (typical values).

Figure 8 : Ratio of the Latching Current I_L in the Different Quadrants to the Triggering Current I_{GT} in the First Quadrant, for Sensitive and Standard Triacs (typical values).

	$\frac{I_L(QI)}{I_{GT}(QI)}$	$\frac{I_L(QII)}{I_{GT}(QI)}$	$\frac{I_L(QIII)}{I_{GT}(QI)}$	$\frac{I_L(QIV)}{I_{GT}(QI)}$
6 Arms Sensitive Triacs (T type)	3.5	15	5	3
12 Arms Standard Triacs (B type)	2	5	1.5	1.7

Example 1 :

BTA 06.600 T : if $I_{GT}(QI) = 1 \text{ mA}$
 then : $I_L(QI) \approx 3.5 \text{ mA}$;
 $I_L(QII) \approx 15 \text{ mA}$
 $I_L(QIII) \approx 5 \text{ mA}$;
 $I_L(QIV) \approx 3 \text{ mA}$

and BTA 12.600 B if $I_{GT}(QI) = 15 \text{ mA}$
 then : $I_L(QI) \approx 30 \text{ mA}$;
 $I_L(QII) \approx 75 \text{ mA}$
 $I_L(QIII) \approx 22 \text{ mA}$;
 $I_L(QIV) \approx 25 \text{ mA}$

In the case of triacs, as opposed to that of thyristors, note that : as underlined in the table of *figure 8*, the current $I_L + -$ (electrode A_2 positive with respect to electrode A_1 and electrode G negative with respect to electrode $A_1 - QII$) is much higher than the I_L current in the three other quadrants.

In the data sheets two values are specified : one value for quadrants I, III and IV and one value for quadrant II. In general these values are typical.

b) Relation between the latching current I_L and the holding current I_H

The holding current value I_H (see bibliography, note N° 2) is linked to the latching current value, I_L . By definition, the I_L current value will always be higher than the I_H current value.

The I_L / I_H ratio varies following the sensitivity of the triacs and their ratings (see figure 9).

Figure 9 : Ratio of the Latching Current I_L to the Holding Current I_H Depending on the Sensitivity and Ratings of the Devices (typical values).

	Sensitive Triacs and Thyristors $I_{RMS} \leq 6 \text{ A}$	Medium Power Thyristors and Triacs $6 \text{ A} \leq I_{RMS} \leq 60 \text{ A}$	High Power Thyristors and Triacs $60 \text{ A} \leq I_{RMS} \leq 300 \text{ A}$
I_L / I_H (1)	1.1 to 1.5	1.5 to 2	2 to 5

(1) 1 st quadrant in the case of triacs.

For the low power components (thyristors and triacs whose rated current is lower than 60A) the latching current I_L is dependent on the value of firing current I_{GT} (see *figure 8*).

Example 2 :

BTA 12.600 C : $I_L \text{ typ} = 40 \text{ mA}$ QI, III, IV
 $I_L \text{ typ} = 70 \text{ mA}$ QII

Depending on the production batches, parameter I_L shows dispersion. Shown below are approximate values :

sensitive triacs :

$I_{GT}(QI) \leq 5 \text{ mA}$ (type T):
 QI, III, IV : $2 \text{ mA} \leq I_L \leq 8 \text{ mA}$
 QII : $10 \text{ mA} \leq I_L \leq 40 \text{ mA}$

standard triacs :

$I_{GT}(QI) \leq 50 \text{ mA}$ (type B):
 QI, III, IV : $15 \text{ mA} \leq I_L \leq 50 \text{ mA}$
 QII : $50 \text{ mA} \leq I_L \leq 120 \text{ mA}$


c) Variations of the latching current I_L with the junction temperature.

The value of the latching current I_L is physically

linked that of the triggering current I_{GT} . These two parameters therefore vary analogously with the junction temperature (see figure 10).

Figure 10 : Relative variations of the latching current i_l versus the junction temperature t_j (typ. values).

1. Quadrant 2
2. Quadrants 1, 3 and 4.

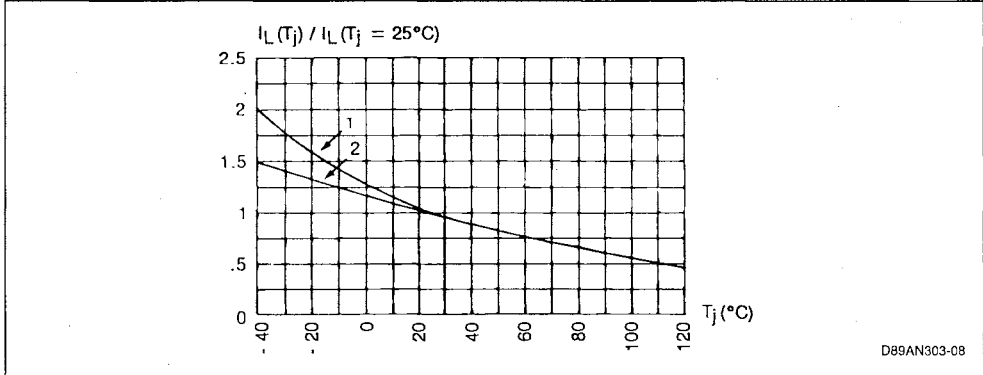

D89AN303-08

Example 3 : Triac TO 220, type BTA 12.600 C

If $I_L(QI) = 20$ mA at $T_j = 25$ °C, then $I_L(QI) = 30$ mA at $T_j = -40$ °C

This resistor affects the value of the latching current I_L in different proportions depending on its resistive value and the sensitivity of the component.


d) Influence of the external gate-cathode resistor R_{GC}

1. Sensitive thyristors ($I_{GT} < 500$ μ A)

When using sensitive thyristors, the designer could wire a resistor R_{GC} between cathode and gate to improve their voltage capability at high temperatures (shunting of leakage currents).

Resistor R_{GC} connected between gate and cathode (figure 11) has an important influence on the latching current I_L of sensitive thyristors. For some applications, the designer would be well advised to define a high impedance triggering circuit.

Figure 11 : Variation of the latching current I_L of a sensitive thyristor (e. g. TLS106-6) as a function of the gate-cathode resistance R_{GC} (typ. values).

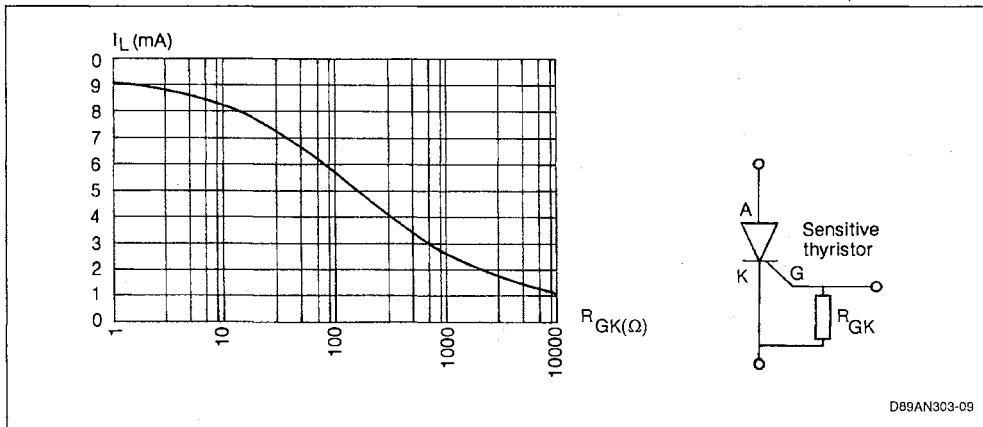

D89AN303-09

Note : The latching current of sensitive thyristors is always specified with a 1000-ohm gate-cathode resistor.


2. Standard thyristors, sensitive and standard triacs
 A resistor connected between the gate and cathode of one of these components does not have a significant influence on the value of its latching current I_L (on condition that its value is not too low $R_{GC} > 20$ ohms).

e) Variation of the latching current I_L with the control conditions

The latching current I_L of a triac or a thyristor rated at less than 60 A_{rms} varies with the amplitude and

the width of the triggering pulse I_G . With a constant pulse width ($< 50 \mu s$), an increase in the amplitude of I_G will lead to an increase in the latching current I_L and vice versa, if the amplitude of I_G is kept constant, a decrease in the width of the triggering pulse will lead to an increase in the latching current I_L that can even lead to an absence of firing of the device (figure 12).

Figure 12 : Variation of the Latching Current I_L versus the Width t_p and the Level of the Gate Current I_G (represented here as a multiple of the triggering current I_{GT} of the triac under consideration) Triac BTB 16.600 B (quadrant 1) (typical values).

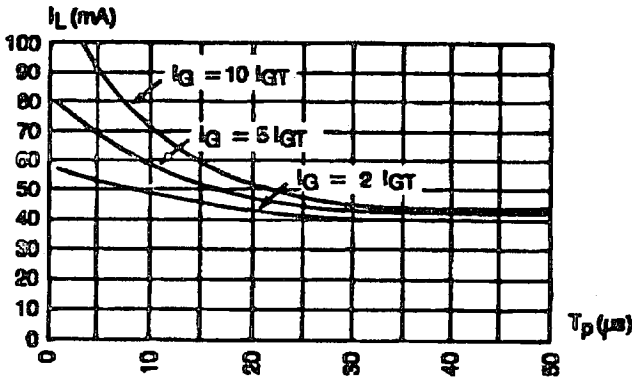


D89AN303-10

Negative biasing of the gate circuit (example : shape of the pulse in figure 13a) increases the latching current I_L in considerable proportions. If the decreasing speed dI_G/dt of the gate current is low


(example : pulse shape of figure 13 b) (less than 0.5 $A/\mu s$) the value of the latching current approaches the holding current I_H .

Figure 13a : Gate Current Pulse with Negative Current at the end of the Pulse : Increase of the Latching Current I_L .

Figure 13b : Gate Current Pulse (diac controlled type) with tailing and without Negative Current : decrease of the Latching Current I_L .

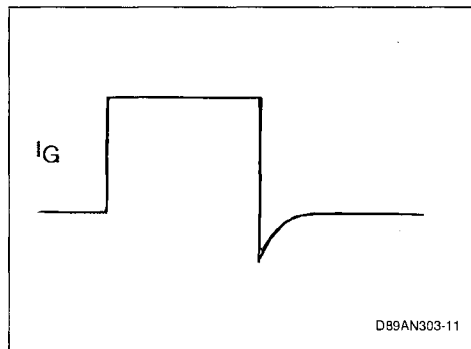

D89AN303-11

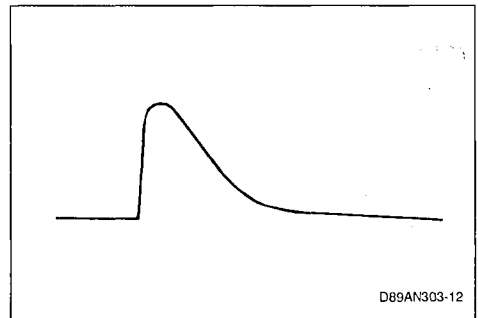

D89AN303-12

In order to obtain the lowest possible values for the latching current I_L , and thus ensure correct firing of the device, it is advisable to work with an amplitude of I_G equal to $1.2 I_{GT}$ and a width of the control current as high as possible. The firing technique using trains of closely spaced pulses ensures stable firing in total security. Control pulses with smooth tailing edges and without reverse current also reducing the latching current.

CONCLUSION

The choice of a thyristor or of a triac does not depend only on the rated current, voltage and sensitivity. Other parameters also play an important part in the correct operation of a circuit and should be taken into account. The latching current I_L is one of these. Its value varies with :

- the way in which the device is controlled (shape of the gate pulse)
- the temperature
- the trigger circuit (case of sensitive thyristors)
- the direction of the current.

Triac and thyristor applications involving highly inductive loads or loads with considerable variations of controlled power are the main applications where the latching current I_L plays a determining role.

Taking these elements into account will enable the designer to obtain satisfactory operation of his circuit in industrial applications.

BIBLIOGRAPHIE

- 1 - "Control of triacs for inductive loads" : technical information TI 36 / SGS THOMSON MICROELECTRONICS by X. DURBECQ.
- 2 - "Hypostatic current or holding current" by E. LEBLANC.