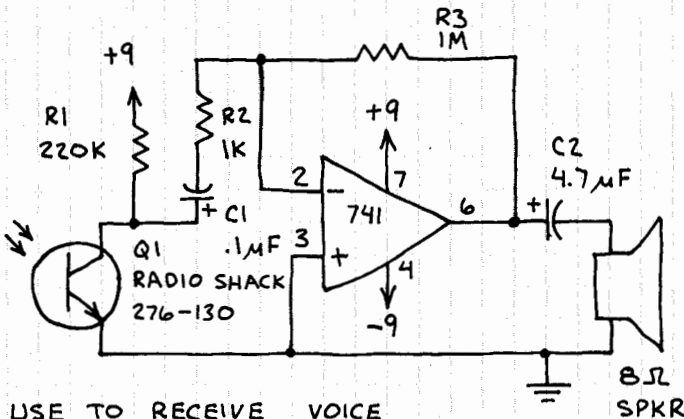


OPERATIONAL AMPLIFIER 741C

LIGHT WAVE RECEIVER



USE TO RECEIVE VOICE
MODULATED LIGHT WAVES. OK
TO USE SINGLE POLARITY POWER
SUPPLY FOR NON-VOICE RECEPTION.