



## Simple v.h.f. preamplifier

This preamplifier is suitable for portable use and operates between 85 and 95MHz. The components can be mounted on a board approximately one inch square. Gain is about 15dB but this can be increased with a small sacrifice in stability by using a BF185. All resistors are 1/4W metal oxide types and the capacitors are ceramic disc.

Ronald G. Young  
Peacehaven  
Sussex