
A Five-Component Wideband Amplifier for Your Receiver

Give your VHF receiver a boost!

by J.S. "Stu" Gurske K9EYY

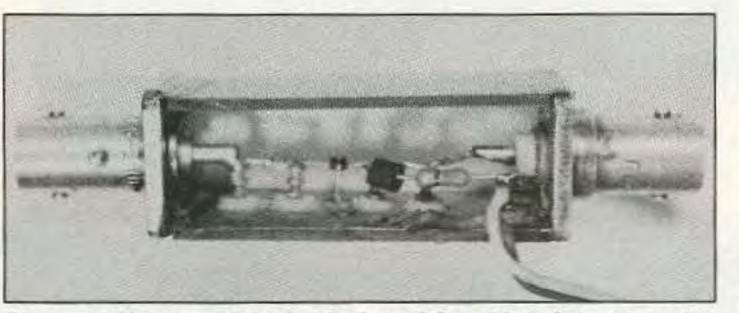

were now fully quiet. This amplifier makes a nice weekend project.

I magine a very wideband amplifier which covers a range of from about 100 MHz to 2,000 MHz, and requires only four other components to make it work. The Mini Circuits catalog lists just such a device, called a MAR-8. It is extremely small, measuring about 0.078 (5/64) inch in diameter by

about 0.62 (1/16) inch thick. It has a gain of about 33 dB at 100 MHz, pretty impressive for such a small device.

Getting It Together

I needed a preamplifier for one of my VHF

Photo A. Close-up of the finished amplifier: MAR-8 (center), chip caps, resistor, stand-off insulator bead on the resistor lead, BNC connectors and 12 volt wires.

receivers and decided to try this device. I obtained a MAR-8, two 100 pF chip capacitors, a 120 ohm 1/4 watt resistor, and a ferrite bead and hooked it all up. The amplifier worked very well. I heard signals which I had never heard before. The old marginal signals

The amplifier uses chip capacitors so, while some care must be taken when soldering them into the circuit, constructing the amplifier was easy. Here is how I did it.

It's easy to make a printed circuit board, but I chose to hard wire the

device instead. I mounted five small standoff insulators on a piece of copper-clad board (i.e. double-sided printed circuit board material) as shown in Figure 2. The circuit board material measured approximately 1/2" wide by 1-1/2" long. After mounting BNC connec-Continued on page 49

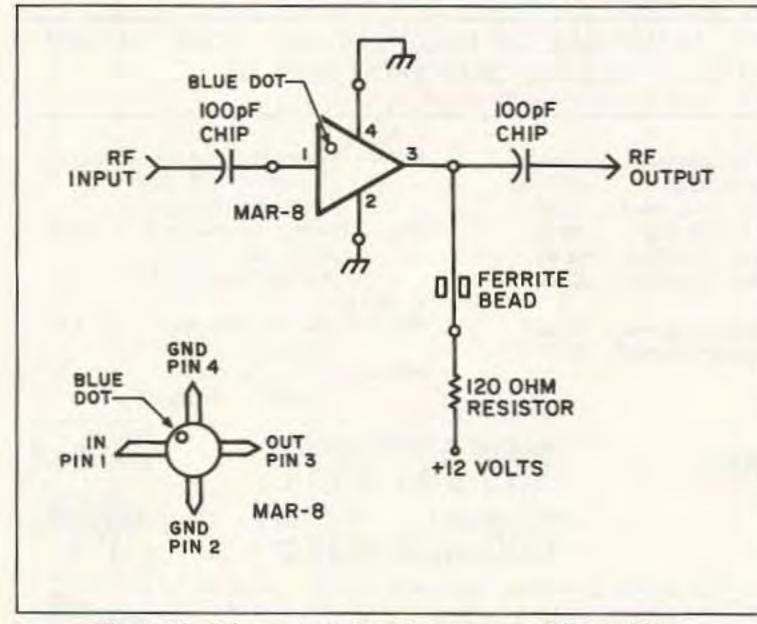


Figure 1. Schematic for the 5-component RF amplifier.

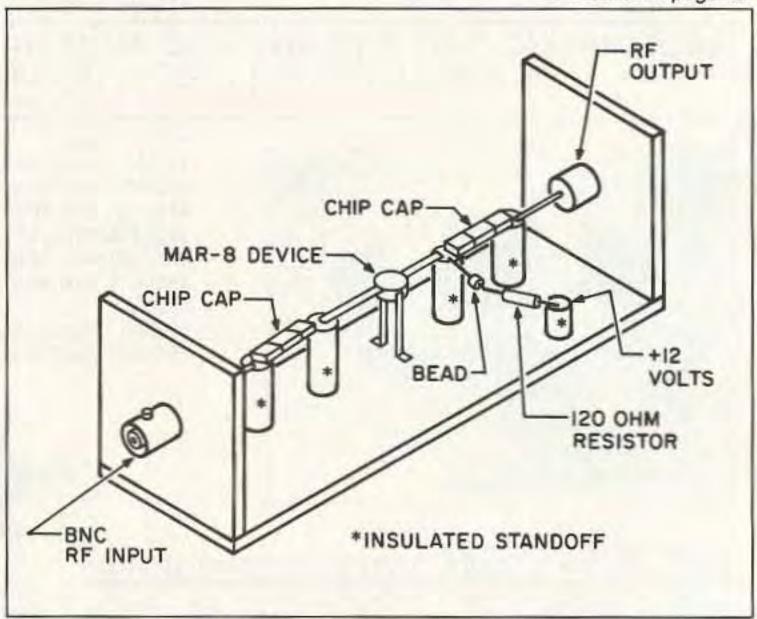


Figure 2. Parts placement for the RF amplifier assembly.

Five-component wideband amplifier

tors at each end of the board, I installed the standoff insulators. I then soldered the chip capacitors in place with great care—they are small.

Next, I mounted the MAR-8. First I bent pins 2 and 4 down so they touched the copperclad board (ground), then I soldered them to the board. Pins 1 and 3 were bent straight out to span between the standoff insulators which support the input and output capacitors. Then they were soldered in place.

After this, I slipped the ferrite (or powdered iron) bead over the resistor lead nearest to pin 3 of the MAR-8. I soldered this lead to the standoff insulator connected to pin 3 of the MAR-8. The other end of this resistor was connected to another standoff insulator and became the attachment point for the +12 volt supply. Incidentally, the size of the resistor is chosen to provide approximately 36 mA to the MAR-8. The data sheets recommend 111 ohms, but I used 120 ohms because that is what I had on hand. The data sheets also recommend a 1 µF capacitor from the +12 volt point to ground if erratic behavior is experienced. My amplifier did not need this capacitor.

Figure 1 shows the schematic for the amplifier. Figure 2 gives a pictorial representation of how the amplifier was assembled.

Photo A is a close-up picture of the device. The length of the little enclosure is about 1-1/2" inside of the box. It is about 1/2" wide and about 5/8" deep. In this view the sides of the box have been removed to show the components. MAR-8 can be seen in the center. After I tested the amplifier, I cut three more pieces of copper-clad board and enclosed the device by soldering the three pieces together to form a box. I have used the amplifier for about six months now with good results.

Continued from page 12

Parts List Qty. Device MAR-8 1 2 100 pF chip capacitors 1 120 ohm resistor 1 ferrite bead 2 chassis mount female BNC connectors insulated standoffs 5

Misc: Box (made out of PC board material).

Parts Sources

MAR-8: Mini-Circuits, Box 350166, Brooklyn NY 11235-0003; phone (718) 332-4661.

100 pF chip capacitors & resistor: Mini Circuits, or Digi-Key, 701 Brooks Ave. South, P.O. Box 677, Thief River Falls MN; (800) 344–4539.

RF Bead: Amidon Associates, P.O. Box 956, Torrance CA 90508; phone (213) 763–5770.

BNC connectors: Radio Shack stores.