

SUPER HOLD: A TELEPHONE PERIPHERAL

*Allows a hold function on any touch-tone phone
and has provisions for music during the hold*

By Thomas E. Black

IF YOU want to add a "hold" feature to your touch-tone phone, it means adding circuitry, or disassembling and modifying an existing phone. Most telephone companies object to this.

The Super Hold described here requires no modification of the telephone, can be connected anywhere on the telephone line, and can even be used to provide music to the person on hold. (As good as Super Hold is,

some telephone companies may require special compliance rulings for such a change, so be sure to check local ordinances with the telephone company before connecting anything to the telephone line.)

Super Hold is essentially a dual-tone decoder that monitors the telephone line and responds to the two frequencies that form the "*" signal (941 and 1209 Hz). Although it is necessary to use a touch-tone



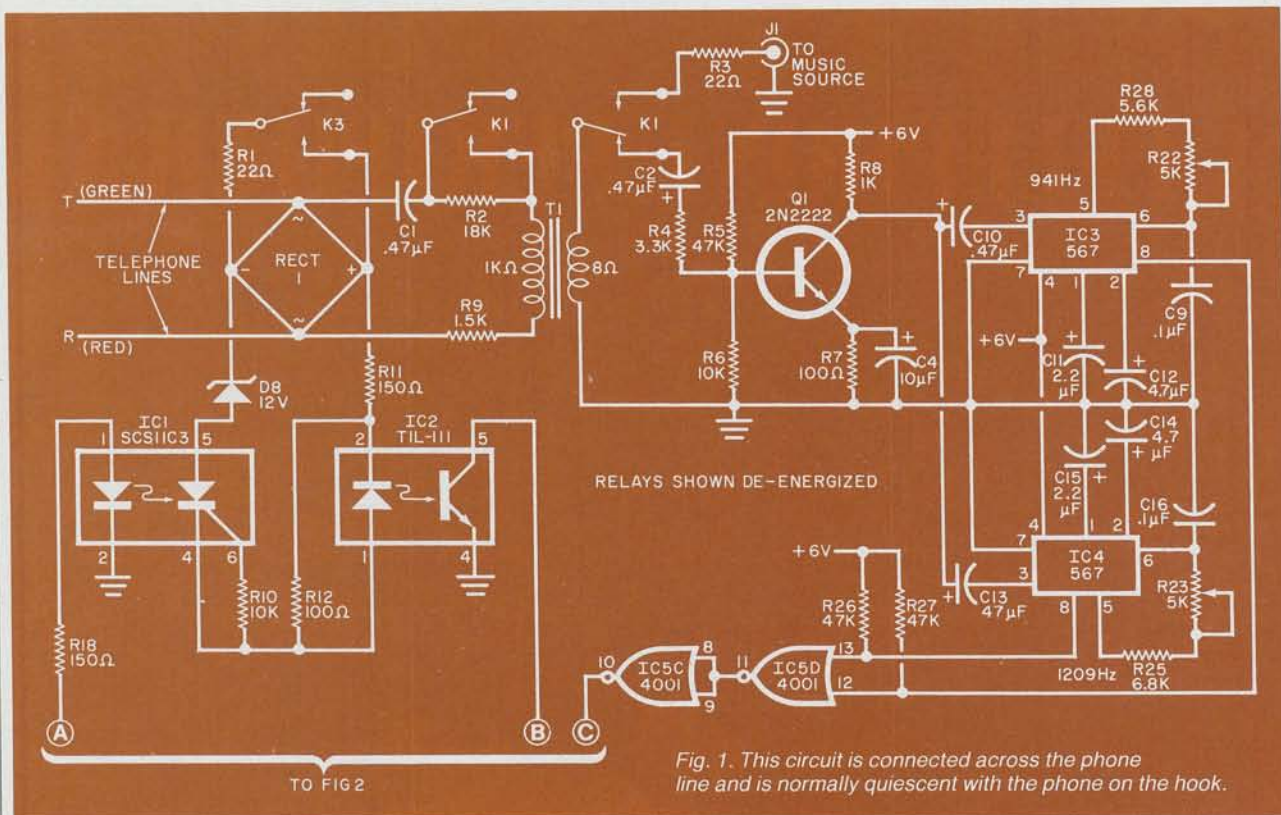


Fig. 1. This circuit is connected across the phone line and is normally quiescent with the phone on the hook.

phone to place a caller on hold, any type of phone can be used to return to the caller and remove the hold condition. Power is supplied by a conventional line-operated supply.

With Super Hold installed, to place someone on hold, simply depress the * pushbutton, then hang up immediately (within five seconds). To return to the holding party, just pick up any phone connected to the same circuit. The complete schematic is shown in Figs. 1 and 2.

Circuit Operation. Super Hold is wired in parallel with the telephone line via the connections marked "T" and "R" shown in Fig. 1. In the non-hold (illustrated) condition, relays K1, K2, and K3 are de-energized and the SCR in IC1 is nonconducting.

In this mode, no dc current flows through the circuit, so the line behaves as if Super Hold does not exist. With the telephone "on hook," the phone line has 48 volts dc provided by the telephone company's local office. When a phone is taken "off hook," this potential drops to

something less than 12 volts, but more than 4 volts. At this lower voltage, 12-volt zener diode D8 does not conduct. Therefore there is still no current path to Super Hold and the circuit is still "invisible." However, capacitor C1 provides enough ac coupling to pass all the audio from the telephone line to the primary of transformer T1. The contacts of de-energized relay K1 provide an audio path from the secondary of T1 to amplifier Q1, whose output is sufficient to drive parallel-connected tone decoders IC3 and IC4.

These two tone decoders are preset to respond to the frequencies associated with the two tones (941 Hz and 1209 Hz) generated when the * button is pushed, IC3 responds to 941 Hz, while IC4 responds to 1209 Hz. When these two tones (and only these two tones) are present at the inputs of the decoders, each output (pin 8) goes low. NOR gate IC5D has its two inputs pulled high via R26 and R27. Thus, its output at pin 11 will be low.

When the two inputs (from the

two tone decoders) go low at the same time, the output of IC5D goes high. After inversion by IC5C, the resulting low is applied to the trigger input (pin 2) of timer IC6, as shown in Fig 2. Upon receipt of the input trigger, pin 3 of IC6 goes high and remains high for the five-second interval determined by R20 and C8. The high on pin 3 performs two simultaneous functions—it drives Q4 to energize relay K3 and it enables IC1.

When relay K3 is activated, low-value resistor R1 is placed across the phone line through RECT1. This action greatly reduces the touch-tone level to prevent it from annoying a listener. At the same time, the high at IC6 pin 3 is applied to the anode of the LED within IC1 (Fig. 1), causing it to glow. The photosensitive SCR within IC1 does not latch since there is not enough voltage across the line to cause zener diode D8 to conduct. To make this zener conduct, the handset must be hung up, and five-second timer IC6 allowed to time out. When the phone is hung up, R1 is still across

...SUPER HOLD

the line. Hence, no current flows through *D8*. When *IC6* times out, relay *K3* de-energizes, removing the *R1* load from the line. Capacitor *C6* momentarily provides enough current to keep the LED within *IC1* glowing, while *K3* is de-energizing. This ensures that the SCR within *IC1* will latch when *D8* conducts. This latter event occurs as the line voltage increases when the load is removed. With *IC1* enabled, a current path exists across the line, and the incoming call is placed on hold.

With *IC1* latched, current also flows through the LED within optocoupler *IC2*. When this optocoupler latches on, it provides a low to *IC5A* via diode *D1*, and to *IC5B* via diode *D2*.

IC5A inverts the low to turn on *Q2* which, in turn, operates relay *K2*. The contacts of this relay can be used to turn on an (optional) tape recorder or radio to feed music to the line (via *J1*) while on hold. The low at *D2* cathode also discharges *C5* via *R16*. After the brief dis-

charge interval, *IC5B* pin 3 goes high, turning on *Q3* and energizing relay *K1*. The delay associated with *C5* and *R16* allows the optional tape deck to get up to speed before apply-

ing the tape-recorded music to the phone line. This prevents "slurred" music as the recorder reaches proper speed.

With *K1* energized, the music

PARTS LIST

C1—0.47- μ F, 200-V Mylar capacitor
 C2, C10, C13—0.47- μ F, 16-V electrolytic
 C3—Not used
 C4, C17—10- μ F, 16-volt electrolytic
 C5, C8—33- μ F, 16-V tantalum capacitor
 C6—220- μ F, 16-V electrolytic
 C7—22- μ F, 16-V electrolytic
 C9, C16—0.1- μ F, 16-V metal film
 C11, C15—2.2- μ F, 16-V electrolytic
 C12, C14—4.7- μ F, 16-V electrolytic
 C18—1000- μ F, 25-V electrolytic
 D1 through D4, D8, D9—1N914 or 1N4148
 D5 through D7—1N4001 diode
 D10—12 V, 1-W zener diode
 F1— $\frac{1}{2}$ -A fast-blow fuse
 IC1—SCS11C3 opto-coupler (Radio Shack 276-136)
 IC2—TIL-111 opto-coupler (Radio Shack 276-132)
 IC3, IC4—LM567 tone decoder
 IC5—4001 quad two-input NOR gate
 IC6—555 timer
 IC7—7805 5-V regulator
 J1, J2—Miniature phone connector
 K1—Dpdt subminiature relay, 5-V coil (Radio Shack 275-215)
 K2, K3—Spdt subminiature relay, 5-V coil (Radio Shack 275-216)

LED1—Red light emitting diode
 Q1 through Q4—2N2222 transistor
 The following are $\frac{1}{4}$ -W resistor unless otherwise noted:
 R1, R3—22 ohms, $\frac{1}{2}$ -W
 R2—18 kilohms
 R4—3.3 kilohms
 R5, R13, R16—47 kilohms
 R6, R10, R15—10 kilohms
 R7, R12—100 ohms
 R8, R21—1 kilohm
 R9, R14, R17—1.5 kilohms
 R11, R18, R24—150 ohms
 R19—180 kilohms
 R20—68 kilohms
 R22, R23—5 kilohm potentiometer (Radio Shack 273-1380)
 R25—6.8 kilohms
 R26, R27—47 kilohms
 R28—5.6 kilohms
 RECT1—200-V, 1-A diode bridge
 RECT2—50-V, 1-A diode bridge
 T1—Audio transformer, 1000:8 ohms, (Radio Shack 273-1380)
 T2—Power transformer, 12.6 V at 300 mA
 Misc.—Suitable enclosure, fuseholder, rubber grommets, music source, mounting hardware.

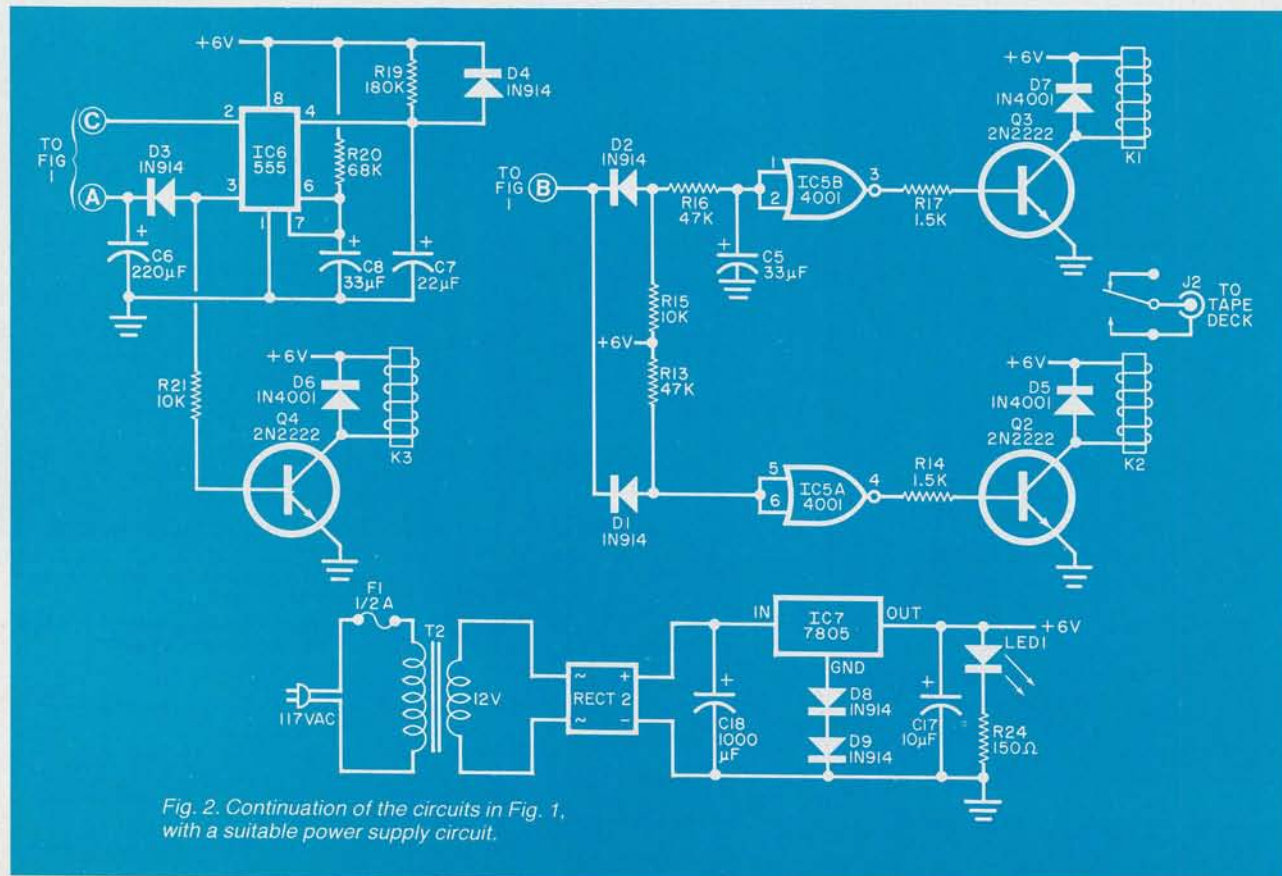


Fig. 2. Continuation of the circuits in Fig. 1, with a suitable power supply circuit.

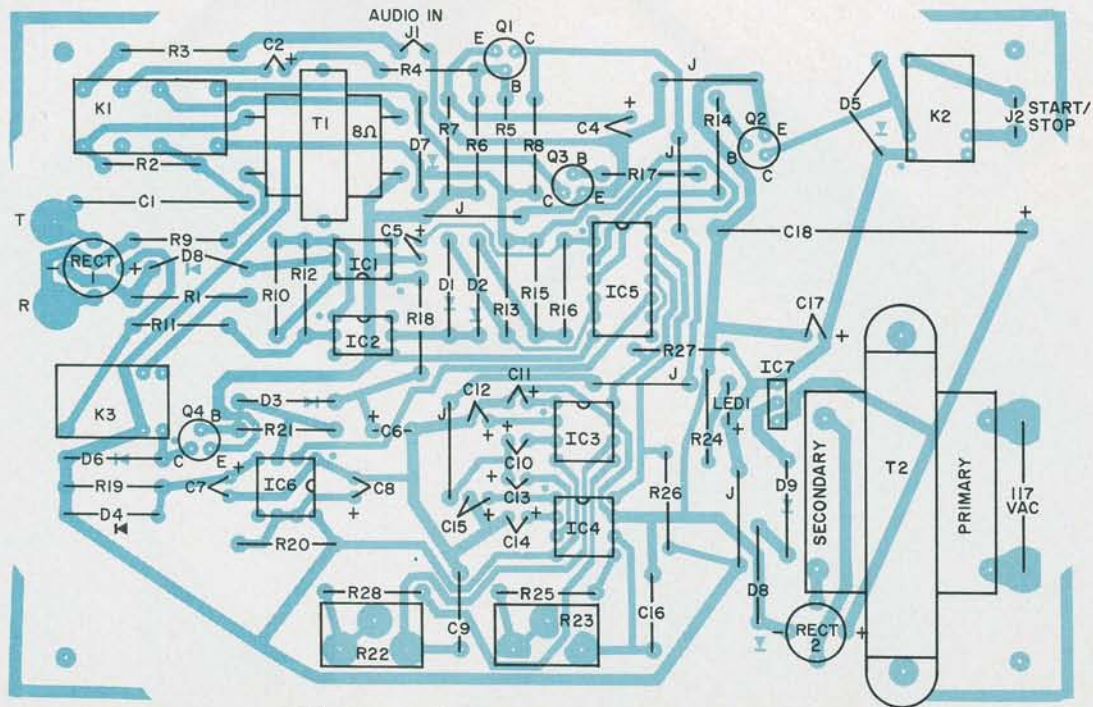
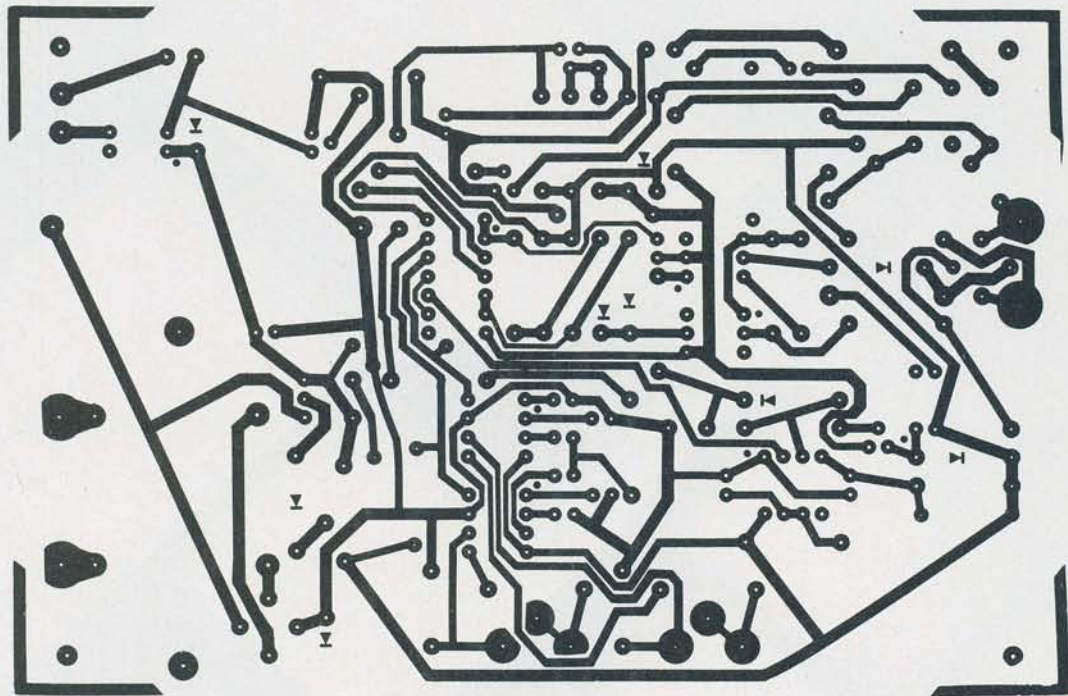


Fig. 3. Same-size foil pattern (top) and component layout for a printed circuit board for the Super Hold.

...SUPER HOLD

source is applied to *T1* via *R3*, while other contacts of *K1* short resistor *R2* to prevent attenuation of the music.

To exit the hold condition requires that the SCR within *IC1* have its current interrupted. This can be accomplished in two ways. When the handset is picked off the cradle, the reduced line voltage causes *D8* to stop conducting. This will unlatch the *IC1* SCR and remove power from the LED within *IC2*. Thus, the outputs of gates *IC5A* and *IC5B* go low, de-energizing *K1* and *K2*.

The other source of hold termination may not occur in all telephone districts. If available, the telephone company provides a momentary current interruption to the line when the holding party hangs up. This momentary interruption will reset the *IC1-IC2* loop. In some instances, the current interruption may not occur until a minute or so after hangup or may not occur at all. In any case, picking up the telephone handset will always reset the hold condition.

Construction. Although any form of construction can be used, a pc board using the foil pattern of Fig. 3 is recommended.

Using sockets for all ICs, install all components except *R1* (which will be installed after calibration). Use a heat sink on regulator *IC7*, and mount the fuseholder, jacks *J1* and *J2*, and power transformer *T2* in a suitable enclosure. Mount *LED1* in a grommetted hole, and provide grommetted holes for the power cord and telephone cable.

After temporarily mounting the board (remember that *R1* is missing), turn on the power and note that 6 to 7 volts dc exists across filter capacitor *C17*. Diodes *D6* and *D7* are used to modify the output of the 5-volt regulator to provide about 6 volts.

Calibration. The easiest way to calibrate *IC3* and *IC4* is to use a frequency counter. Connect the high-

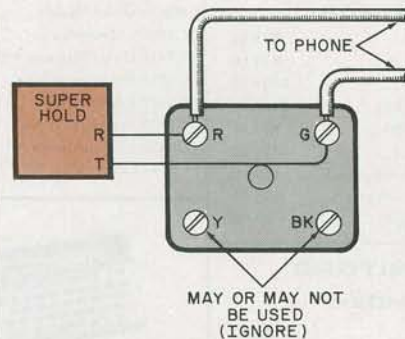


Fig. 4. Use this simple connection while calibrating the Super Hold circuit.

impedance probe to *IC3* pin 6 and adjust *R22* for 941 ± 10 Hz. Move the probe to *IC4* pin 6 and adjust *R23* for an indication of 1209 ± 10 Hz.

The other approach is to connect the Super Hold to the telephone line as shown in Fig. 4, call a friend on the phone and have him remain silent during the following calibration procedure.

Connect the positive lead of a dc voltmeter to *IC5* pin 13 and the negative lead to ground. The meter should indicate about 6 volts dc. Depress the * button on your phone and adjust *R23* until the meter indi-

cation drops to about 0.5 volt. Release the * key and note that the voltage increases. Depress the 7 key and note the voltage drop to about 0.5 volt. If not observed, return to the * key and adjust *R23* for a 0.5-volt indication. Depressing the 7 key should cause a drop from 6 to about 0.5 volt dc. This calibrates *IC4*, the 1209-Hz tone decoder.

To adjust *IC3*, the 941-Hz decoder, place the voltmeter positive lead at *IC5* pin 12, depress the * key, and note the voltage drop to about 0.5 V. Release the * key and depress the # key. The meter indication should drop to 0.5 V.

If not, depress the * key and adjust *R22* for a meter indication of about 0.5 V. Depressing the # key should also produce the voltage drop. This calibrates *IC3*, the 941-Hz tone decoder.

Connect the voltmeter to *IC5* pin 10 and note about 6 volts dc on this pin. Depress the * key and note that the voltage drops to about 0.5 V. No other key should produce this effect. If any does, then both *IC3* and *IC4* must be re-calibrated.

Terminate the phone call, remove all test equipment, and disconnect the power. Install *R1* in the circuit. Then connect the Super Hold back to the telephone line and turn on the power. Lift up the phone, depress the * key, and hang up the handset. Relay *K3* should have energized as soon as the * key was depressed. After about five seconds, *K3* should drop out and *K2* (if installed) should be energized. A couple of seconds later, *K1* will also be energized. Picking up the telephone handset should cause relays *K1* and *K2* to be de-energized.

When all works well, install the board in a suitable enclosure, connect *J2* to the tape-deck power on/off, and connect the audio output of the tape deck to *J1*.

Phone a friend, depress the * key to put him on hold, replace the phone in its cradle, and let him listen to the music for a few moments to check the volume. If necessary, re-adjust the volume. If desired, the tape deck components (*Q2* and its associated components) can be left off the circuit and a conventional line-powered radio used as the music source for *J1*. ◇

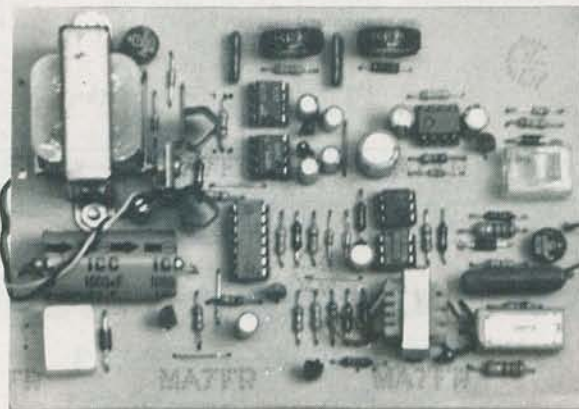


Photo showing layout of the printed circuit board in the author's prototype.

In "Super Hold: A Telephone Peripheral" (May 1983), the polarity of *RECT1* should be reversed on both the schematic and the component layout; on the schematic, *C13* should be 0.47 μ F and *R21* should be 1 kilohm; and on the component layout, *IC7* should be installed with its OUT terminal facing up.

July 1983