

# Practical

# RADIO COURSE

By ALFRED A. GHIRARDI

## Part 38. Covering the special oscillator pre-selector tracking problems that exist in multi-band, manually-tuned receivers, and methods employed in solving them.

QUITE a variety of oscillator tuning and band-switching circuit arrangements have been developed and used in multi-band manually-tuned receivers. Unfortunately, space restrictions make it impossible to present all of them here. However, descriptions of two general arrangements that have been widely used (with only slight modifications) in the receivers of various manufacturers—one mostly in 2-band receivers and one in 3-band receivers—will serve to outline the general way in which the oscillator tracking and band-switching problems have been solved for each tuning band.

Fig. 1 illustrates a popular oscillator tuning coil, band-switching, and oscillator-preselector tracking arrangement that has been used in many 2-band receivers employing a tapped-coil system for multi-waveband coverage. For reception on the 540 to 1720 kc. broadcast-band tuning range provided in this particular receiver, the four band switches shown are thrown over to the "B" contact. This places

Fig. 1. Band-switching, tuning, high-frequency trimmers, and low-frequency padder arrangements employed in oscillator of a two-band receiver using tapped coil system (Philco model 42-322).

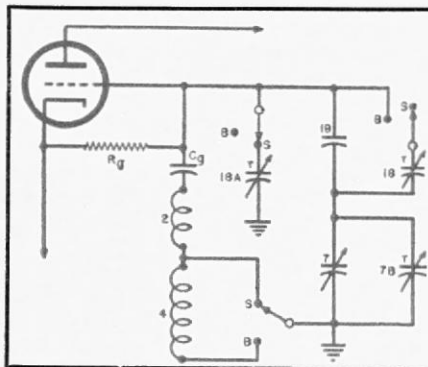
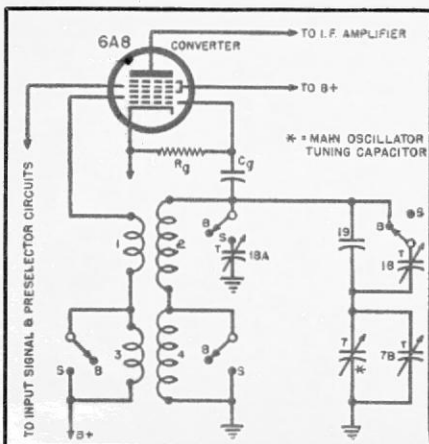


Fig. 2. Leaving portion 4 of the tuning coil open, as shown, when the short-wave band is being used has disadvantages over that of shorting the coil, illustrated in Fig. 1, as discussed in the text.

the full tickler winding (1 + 3) in the plate circuit (the second grid acts here as the plate of a triode oscillator), and the full secondary winding (2 + 4) in the tuning circuit. The full secondary is tuned by a combination made up of fixed low-frequency padder 19 shunted by adjustable broadcast-band padder 18, all in series with main oscillator tuning capacitor 7 shunted by its broadcast-band, high-frequency trimmer 7B. (Notice the similarity between this circuit arrangement and that of the fundamental "padder" circuit illustrated in Fig. 3 in the installment of this series that appeared in the September 1945 issue of RADIO NEWS.)

The manufacturer's aligning and tracking instructions specify that broadcast-band, high-frequency trimmer 7B and the similar one on the preselector tuning capacitor section (not shown) are to be adjusted at a preselector frequency of 1500 kc. to obtain correct oscillator-preselector tracking at the high-frequency end of the broadcast-band. The broadcast-band, low-frequency adjustable padder 18 must be adjusted at a preselector

frequency of 580 kc. in order to correctly tie down the oscillator tracking at the low-frequency end. Tracking will then be close and satisfactory all over the broadcast band.

For reception on the 8.7 to 15.5 mc. short-wave band provided in this receiver, the four band-switches shown are thrown over to the "S" contact. This shorts out portion 3 of the tickler coil and portion 4 of the secondary, leaving only portion 1 of the tickler and portion 2 of the secondary in the circuit. Padder 18 is now out of the circuit and adjustable short-wave high-frequency trimmer capacitor 18A is shunted across the tuning coil 2. Fixed series padder 19 still remains in series with the main tuning capacitor 7 that is shunted by its broadcast-band trimmer 7B. Short-wave high-frequency trimmer 18A, and a similar one across the short-wave preselector tuning coil (not shown), are to be adjusted for correct tracking at a preselector frequency of 15 mc. No means for adjustment of the padder capacitance is provided or necessary for the short-wave band.

A somewhat similar band-switching and oscillator tracking arrangement is used on many 3-band receivers that employ the tapped-coil system for multi-waveband coverage.

### Why Unused Portions of Tapped Tuning Coils are Shorted by Band-Switch

We will digress from our discussion of oscillator tracking for a moment, to consider an important detail in connection with the use of tapped tuning coils in multi-band receivers. It will be noticed that the lower portion, 3, of the full oscillator tuning coil is shorted out by the ganged waveband switch when it is set for short-wave operation, as is also the lower portion, 3, of the plate tickler coil. The tuning coil might have been tapped, of course, and its lower end left ungrounded; then the lower terminal of main tuning capacitor, 7, could have been arranged to be switched either to the lower end of tuning coil 4 for broadcast-band reception, or to the tap for short-wave reception, thus leaving the unused portion of the tuning coil open as shown in Fig. 2.

At first thought it would appear that leaving the unused portion of the tuning coil open would be better than shorting it, since experience has taught us that even one or two shorted turns in a tuning coil are undesirable. However, there is good reason for shorting coil 4, as we shall see. If an appreciable part of the coil is left open, the capacitance (both distributed and due to circuit wiring, shields, etc.) across this portion of the coil is likely to resonate it to a frequency in or near the desired short-wave band. If this occurred, it would greatly reduce both the sensitivity and selectivity over part of the short-wave band. In addition, coil 3 would most likely resonate at one frequency and coil 4 at a different frequency. This would throw the oscillator so badly out of track with the preselector circuits that it is doubtful if any signal at all would be received at certain frequencies. Spiling the oscillator tracking is much more serious than spiling the alignment of the preselector tuned circuits with each other. Another important thing to consider is that if the resonant frequency of the unused open portion of the oscillator coil happened to fall in the desired short-wave band, it is probable that the energy absorption would be so great that the oscillations would stop entirely. Now, if one unused turn of a coil is shorted it is very serious, for a comparatively large current will flow in the shorted turn and this will absorb power from the remainder of the coil and also seriously alter its effective resistance and inductance. If two unused turns are shorted, the effect is less serious because while the total voltage induced in the two turns is almost twice as great, the inductance of these two turns is four times as great as for one turn (inductance is nearly proportion-

al to the square of the number of turns). Consequently the inductive reactance and impedance will be proportionately greater, and the current flowing in the two shorted turns is only half what it was in one turn. Accordingly, when there are a large number of unused turns on a coil, the effect of shorting them, as was done in the circuit of Fig. 1, is usually negligible, so the band-switch circuit in multi-band receivers employing tapped coils is always designed to short all unused turns on the coils.

Fig. 3 illustrates the tapped-coil system employed in the preselector and oscillator of the 3-band *Stromberg-Carlson* 58 receiver. Note that the waveband switches are of the "shorting" type, designed to short out all unused coils when in either of the short-wave band positions,  $S_1$  or  $S_2$ .

#### Oscillator Tracking and Band-Switching in Multi-Band Receivers Employing Separate Coils for Each Band

Most multi-band capacitor-tuned receivers, especially those designed to provide reception on 3 or more frequency bands, employ an individual preselector and oscillator tuning coil for each band, as illustrated in Fig. 4. In some of these, the secondary of each individual preselector and oscillator tuning coil is shunted with its own individual adjustable high-frequency shunt trimmer capacitor, and the tuning circuit of each oscillator coil has, in addition, both a fixed and an adjustable low-frequency series padder (the adjustable padder is usually omitted from the tuning coil for the highest-frequency waveband). For each waveband, the circuits and ganged waveband switches are arranged to switch the proper preselector and oscillator tuning coils and individual trimmer

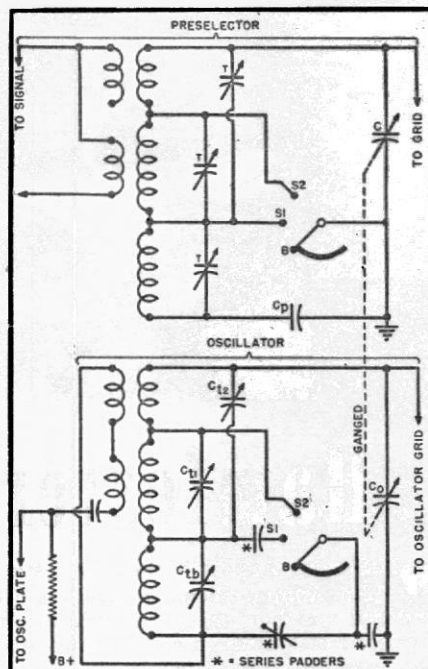



Fig. 3. Preselector and oscillator circuit arrangement employed in 3-band receiver, using tapped-coil system with coil-shortening type band switches (Stromberg-Carlson 58).

and padder capacitors into the circuits as units.

Fig. 4 illustrates a typical preselector and oscillator tuning and switching arrangement of this type, as used in the *Fada* model 290 series receivers which provide reception on the regular broadcast band and on two short-wave bands. Capacitors  $C_p$  and  $C_o$  are the main preselector and oscillator tuning capacitors, respectively, and are ganged together for single tuning control.

$B$  is the broadcast-band position of (Continued on page 158)

Fig. 4. Tracking arrangement provided in typical 3-band receiver (*Fada* model 290 series), employing individual tuning coils, high-frequency trimmers, and low-frequency padders for each of the three bands.

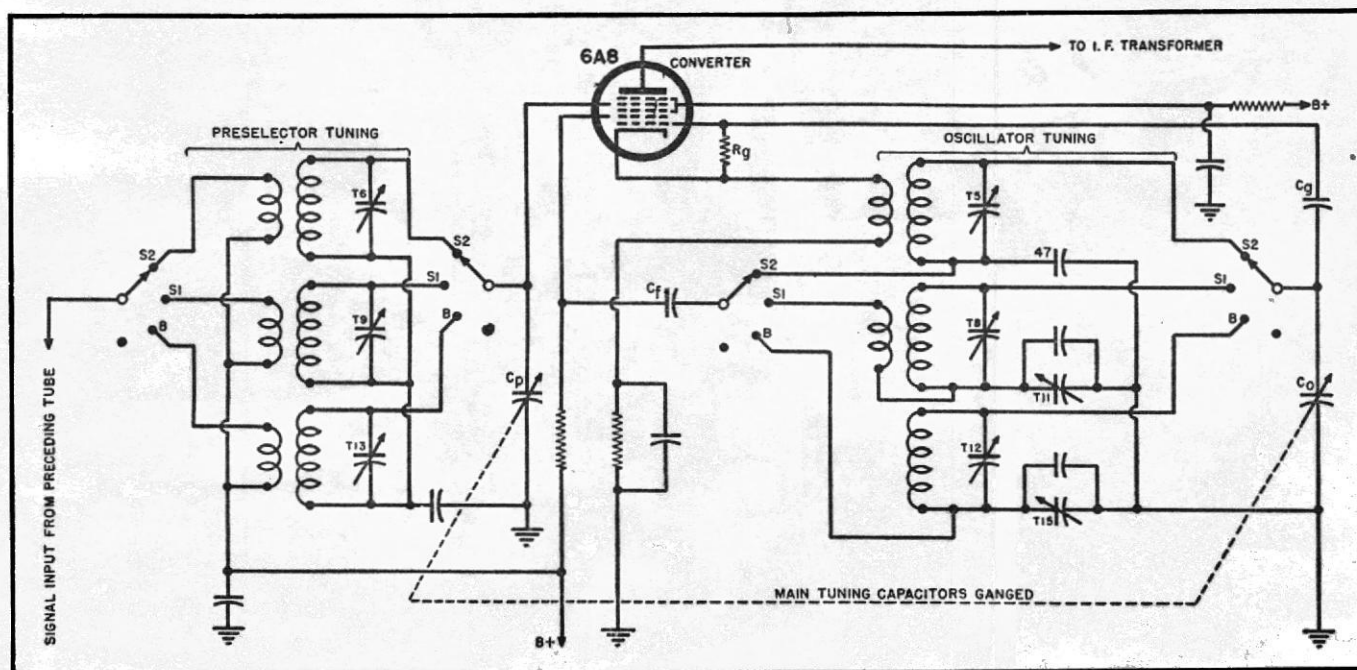



**★ INDUSTRIAL ★  
MAN-POWER BUREAU**

Continued

**ENGINEERS  
FOR DESIGN WORK  
ON RADIO RECEIVERS,  
AUDIO AMPLIFIERS,  
TELEVISION**

Men with substantial experience wanted, preferably those having Degrees in Electrical or Communications Engineering. Write, giving details of experience and salary expected, to:

**FREED RADIO  
CORPORATION**

**Makers of the Famous Freed-Eisemann Radio-Phonograph**

**200 Hudson Street  
New York 13, N. Y.**

**RADIO  
ENGINEERS  
DRAFTSMEN  
WANTED**

For development and design of marine radio telephone, telegraph and navigational equipment.

Permanent positions available with pioneer company.

write

**Mackay Radio and Telegraph Co., Inc.  
MARINE DIVISION**

111 Eighth Avenue New York 11, N. Y.

**RADIO MECHANICS**

We have a number of openings for skilled mechanics, particularly with A & E licenses. We have a smaller number of openings for unlicensed mechanics, radio operators, skilled aviation personnel of all types. These are excellent paying positions. Contact us shortly before you are discharged giving both Army and Civilian addresses, giving full information. Main Office: AIR PERSONNEL & SALES, INC. First National Bank Building, Urbana, Illinois. Branch Office: P.O. Box 1895, Pittsburgh, Pa.

**Practical Radio Course**

(Continued from page 51)

each band switch. Capacitors  $T_{13}$  and  $T_{12}$  are the broadcast-band preselector and oscillator high-frequency trimmers respectively, which are to be adjusted for proper high-frequency tracking at a preselector frequency of 1500 kc. Capacitor  $T_{16}$  is the adjustable unit of the broadcast-band low-frequency padder, and is to be adjusted for proper low-frequency tracking at 600 kc.

$S_1$  is the first short-wave band position of each band switch. Capacitors  $T_9$  and  $T_8$  are the high-frequency trimmers for this band, and are to be adjusted for correct high-frequency tracking at a preselector frequency of 4.5 mc. Capacitor  $T_{11}$  is the low-frequency padder for this band, and is to be adjusted for proper low-frequency tracking at a preselector frequency of 1.8 mc.

$S_2$  is the higher-frequency short-wave band position of each band switch. Capacitors  $T_6$  and  $T_7$  are the high-frequency trimmers for this band, and are to be adjusted for correct high-frequency tracking at a preselector frequency of 15 mc. No low-frequency adjustable padder is provided for this band—the fixed low-frequency padder 47 sufficing for correct tracking here.

To insure perfect tracking the ganged main oscillator tuning capacitor should be "rocked" while adjusting the low-frequency padders, so that the maximum signal output will be followed.

**Interlocking Trimmers**

Inspection of the separate-coil multi-band oscillator circuit in Fig. 4 reveals that a separate coil and oscillator high-frequency trimmer is used for each band. The trimmer is connected across the coil for that particular band and utilized only when that coil is in the circuit. Hence, the adjustment of a trimmer on one band is entirely independent of the trimmer adjustments on any other band so it does not matter which band is first adjusted for correct high-frequency tracking.

Many multi-band receivers that use a tapped-coil tuning system instead, employ trimmers that are in the circuit on more than one band. For example, for the broadcast band in the oscillator of the *Stromberg-Carlson* 58 receiver (see Fig. 3), all three trimmers are in series across the full tuning coil. Therefore, the oscillator tracking at the high-frequency end of the bands must be adjusted on the highest-frequency band first, when the lower two portions of the tuning coil, and their trimmers, are shorted out by the waveband switch. Then the adjustment is made on the medium-frequency band, and finally the broadcast-band. If the tracking adjustment were made on the broadcast-band first, the subsequent tracking adjustments made on the other two bands would

**Classified**

Rate 20c per word, Minimum, 10 words

**WANTED**

RADIO Tubes 2B6 wanted. Jarvis, 27 Boulevard, New Rochelle, N. Y.

ENGINEERS interested in becoming associated with national engineering organization as Consultants. Write United Engineers, Box 1065-D, Los Angeles 28, Calif.

**RADIO ENGINEERING**

INTENSIVE radio operator courses (Marine, Broadcast, Aviation) prepare for FCC examinations. Co-ed. Days—evenings. Western Radio Communications Institute, Dept. "R," 106 West Third St., Los Angeles 13, Calif.

RADIO Engineering, Broadcasting, Aviation and Police Radio, Servicing, Marine Operating and Electronics taught thoroughly. Expenses low. Write for catalog. Valparaiso Technical Institute, Dept. N, Valparaiso, Ind.

**RADIO EQUIPMENT**

RADIO Service men and experimenters send for our giant radio catalogue. Save dollars. United Radio Co., (1000M) Newark, N. J.

**CORRESPONDENCE COURSES**

USED Correspondence courses, Educational and Technical Books, bought, sold, rented. Catalog Free. Educational Exchange, Henagar, Ala.

USED Correspondence Courses and Educational Books sold or rented. Inexpensive. Money-back guarantee. Write for Free Catalog listing 4000 bargains.—(Courses Bought.)—Lee Mountain, Pisgah, Ala.

CORRESPONDENCE Courses and self-instruction books, slightly used. Sold. Rented. Exchanged. All subjects. Satisfaction guaranteed. Cash paid for used courses. Complete information and 92-page illustrated bargain catalog FREE. Write Nelson Company, Dept. 2-59, Chicago 4.

**FOR SALE**

BARGAINS—Tubes, Parts, etc. Write—J. C. Thimijan, Lake City, Minn.

SELSYNS, Autosyns, Synchro-Units—war surplus aircraft type instruments for indicating position of remotely located rotary antenna. Applicable in remote control circuits. \$15.00 pair without priority. Wiring instructions included. Discount to dealers. D. O'Connor, 7 Winthrop Terrace, East Orange, N. J.

GET LIST. Surplus tubes, capacitors, meters, electronic instruments. Fraction original cost. Quest, 395, Great Neck 3, N. Y.

RECTIFIERS—Halfwave, 5 Amperes, \$4.50; 2.2 Amperes, \$2.25; 1.5 Amperes, \$1.85. Fullwave, 1 Ampere, \$2.50; .5 Ampere, \$1.85. Maximum 18 volts input. List free. Milton Bursma, Route 5, Grand Rapids, Mich.

BUZZER Code Practice set complete with key, battery and instructions. Sends real wireless signals. Only \$1.65. Two sets \$3.00. Guaranteed. Rathert Electric, Dent, N. Cresco, Iowa.

HOOK-UP Wire: Rubber and Aircraft Covering. 3 lbs., \$1.00. Postpaid 1000 miles; over 25c. Satisfaction guaranteed. Coaxial and multi-conductor available. Aldred Salvage Supply, 2515 Boulevard, Jacksonville 6, Florida.

LEADING radio retailers, buy our hobby, sporting, toy, game, other fast-selling merchandise. Boost radio business. Riolen, Riolen Bldg., New Rochelle, N. Y.

BUILD radio complete with tubes \$10.95, details. Radio, 9418a Avenue "A", Brooklyn, N. Y.

LOWEST Prices. Radio Tubes, parts. Bargain lists 3c. Potter, 1314 McGee, Kansas City 6, Mo.

**MISCELLANEOUS**

AIRCRAFT Radio-Army radio transmitters and receivers converted. All types aircraft radio serviced and installed. Work done by FCC licensed mechanics. Prompt service-satisfaction guaranteed. Backed by 15 years experience. Airway Radio-Sales and Service, 10636 S. Spaulding Ave., Chicago 43, Ill.

ADMINISTRATIVE—Returning Veterans with Navy Radio Technician training and experience, also 20 years of Banking and Accounting experience, including 7 years as a Bank Examiner before entering the service. Looking for a permanent administrative position, preferably Treasurer or Comptroller, with a Broadcasting System or Radio and Electronic Manufacturer. Wallace T. Miller, 1322-32 St., Des Moines 11, Iowa.

I AM SEEKING a line of Radio, etc. I can offer intelligent representation as distributor or agent. Clifford, 7 Irvington St., Boston.

**LEARN radio easier—faster!** "The Mystery of Radio (How it Works)" illustrates, explains radio principles, wiring circuits, connections, etc. in easy-to-understand terms. Only 50c. Details free. Scientific Radio Service, Box 1285, Sioux City 7, Iowa.

**RADIO Books**—We have hundreds of the best Radio and Television books. Send for free book lists. Vaughan's, 4524 Spruce St., Philadelphia, Pa.

### PATENT ATTORNEYS

**INVENTORS**—Before disclosing your invention to anyone, send for Form "Evidence of Conception"; "Schedule of Government and Attorneys' Fees" and instructions. Sent free. Lancaster, Allwine & Rommel, 414 Bowen Building, Washington 5, D. C.

**RANDOLPH & Beavers**: Registered Patent Attorneys, 331-E Columbian Building, Washington, D. C. In order to protect your invention and reap the reward that should be yours, Patent your invention without delay, and at the same time have Rights to sell as Manufacturers convert to Civilian Production. Write for Information and Record Form Today.

**PATENTS SECURED.** Two valuable booklets sent free. Write immediately. Victor J. Evans & Co., 948-K Merlin Bldg., Washington 6, D. C.

## ELECTRICIANS! RADIO MEN!

Earn More Money!

Get this new  
**GIANT SIZE**

**ELECTRICAL and RADIO TROUBLE SHOOTING MANUAL**  
GUARANTEED BY COYNE

*Yours 10 Days Free*

**OVER 500**  
Large Size  
Electrical and Radio  
Shop Prints  
How to read  
and use them

Needed by war workers, maintenance men, beginners, old timers! Nothing else like it. Saves time, helps boost your pay... **4 GREAT BOOKS IN ONE!**  
1. New Step-by-Step Trouble Shooting Course, 2. 500 Shop Prints, 3. Elec. Radio Dictionary, 4. Spare Time Jobs.

**FREE!** 1 yr. Technical Counsel by mail from COYNE staff, on trouble-shooting problems.

**SEND NO MONEY!** See offer below. Satisfaction guaranteed by famous COYNE "Learn-by-Doing" Electrical School. Rush coupon now!

**H. C. LEWIS, President, Dept. 78-72**  
**COYNE ELECTRICAL SCHOOL**  
500 S. Paulina St., Chicago 12, Ill.  
Send, with all shipping charges paid, your new COYNE Electrical and Radio Trouble Shooting Manual. Within 10 days after getting it I'll either return it or send \$3, then \$5 monthly until total of \$8.56 is paid. [ ] Cash price \$8.00—you save over 10%—Same 10-day free trial and return privilege.

NAME \_\_\_\_\_ Age \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ Zone \_\_\_\_\_ STATE \_\_\_\_\_



### Learn modern watch and clock repairing

At home, spare time. Good field now... security and contentment in future. Start part-time business and earn while you learn. Hologology is precision instrument work, a great and growing field, sensational opportunities. Easy self-instruction course. Low price. Money-back guarantee. Write now for Free Success-Catalog. **NELSON CO., 321 S. Wabash Ave., Dept. 3138, Chicago 4, Illinois**

**RCA Institutes, Inc.**  
Offer thorough training courses in all technical phases of Radio and Television  
**WEEKLY RATES** **DAYS—EVENINGS**  
**VETERANS:** RCA Institutes is approved under G. I. Bill of Rights  
For Free Catalog write Dept. RN-45  
**RCA INSTITUTES, Inc.**  
A Service of Radio Corporation of America  
75 Varick St., New York 13, N. Y.

**Specify SAUERISEN**  
**ACIDPROOF CEMENTS—COMPOUNDS FOR**  
Tanks, Sewers, Stacks, Floors  
Technical cements for all purposes.  
Send sketches or samples  
Sauereisen Cements Company • Pittsburgh 15, Penna.

nullify the settings on the broadcast-band because the trimmer capacitors for the two short-wave bands also have a tuning effect on the full tuning coil when it is used for broadcast-band reception. Similarly, adjustment of trimmer  $C_{12}$  affects the tuning of the portion of the coil used for the medium-frequency band, so, unless the highest frequency band is tracked before the medium-frequency band, it will nullify the settings on the latter.

### Fixed Tracking Padders

In the oscillators of some multi-band receivers there is only an adjustable type series-padding capacitor for the broadcast-band, the series padder for the medium- and short-wave bands being in the form of fixed capacitors (see Fig. 3). In others, all bands but the highest-frequency band are provided with adjustable padders, the latter requiring only a fixed padder of the proper capacitance value (see Figs. 1 and 4).

It is interesting to note that if the receiver is designed to have the oscillator operating at a lower frequency than the signal, the low-frequency pad or pads are placed in the preselector tuning circuits. Using a "low side" oscillator is advantageous in ultra-high frequency receivers, since the oscillator has greater output and stability when operating at a lower frequency. Let us see the reason for this. The difference between "low side" (or lower-frequency) oscillator operation and "high side" (or higher-frequency) oscillator operation amounts to twice the intermediate frequency. Therefore, in a standard broadcast-band receiver employing the usual 455 kc. i.f., the frequency advantage gained by low-side oscillator operation would be only  $455 \times 2 = 910$  kc. The benefits of such operation would be negligible! The difference in efficiency also would be negligible. On the other hand, in a u.h.f. receiver employing a much higher i.f., say 5 megacycles, the difference of  $5 \times 2 = 10$  mc. between the two methods of oscillator operation could result in a considerable improvement in oscillator performance if the "low-side" mode of operation is employed.

The special oscillator-preselector tracking problems encountered in receivers that employ push-button station selection will be explained in the next article of this series.


(To be continued)

### Photo Credits

Page	Credit
25, 26 (top, bottom right), 27 (center), 28 (center, bottom left), 29 (top, bottom right), 30... U. S. Navy	
26 (center, bottom left and center), 27 (top, bottom), 29 (bottom left)	U. S. Army Air Forces
31	Supreme Instruments Co.
41, 42, 43	G. Haug
58	General Electric Co.
92	Paul Guillemette, Inc. (CNS)
96	U. S. Army Signal Corps
114	RCA Victor Division, RCA
120	Westinghouse Electric Corp.
146	Maguire Industries, Inc.

# RADOLEK


## Radio-Electronic Service Parts

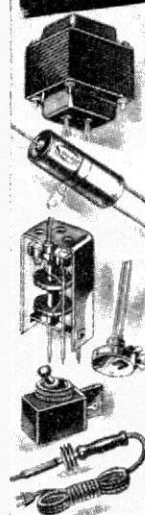

Large stocks assure the finest and most complete selections of all available items at lowest prevailing prices. Thousands of active buyers depend on us for their entire Radio repair and replacement requirements. Because we understand service problems, every order is expedited for delivery in double quick time. Everything we do is planned for convenience and satisfaction to our customers. You will find it profitable to make Radolek your buying headquarters.
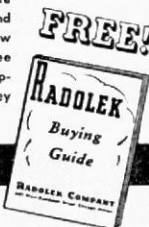
### FREE BUYING GUIDES

Because of existing conditions we keep our customers right up to the minute on available merchandise by releasing supplements frequently instead of sending our regular Big Profit Guide once a year. Send the coupon now to get these Free Buying Guide Supplements as they are issued.




### FAST SERVICE!

**RADOLEK CO., Dept. B-107**  
601 W. Randolph St., Chicago 6, Ill.  
Please send FREE Buying Guide Supplements

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_

### ORDER FROM RADOLEK
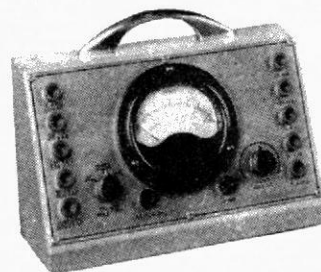
## THIS MULTITESTER IN STOCK IMMEDIATE DELIVERY



**YOUR COST ONLY**

**\$18.75**

Less Test Leads

Model No. MT 100

### UNCONDITIONALLY GUARANTEED SATISFACTION OR MONEY BACK

Latest meter design in all metal case; compact-rugged; the answer to your need for an all purpose, accurate Multitester. Case measures 3 1/2" x 8" x 5". Complete with self-contained batteries.

## RADIO REPAIR MEN ORDER THIS TESTER TODAY

**OMAHA RADIO PRODUCTS CO.**  
300 Saunders-Kennedy Bldg.  
Omaha, Nebraska

Enclosed is full remittance of \$18.75, or my Deposit of \$..... and ship Multitester #MT 100 C.O.D. for balance.

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_